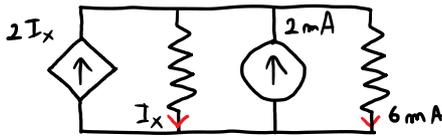



P 2.1



$$2I_x - I_x + 2\text{mA} - 6\text{mA} = 0 \Leftrightarrow$$

$$\Leftrightarrow I_x = 4\text{mA}$$

P 2.2

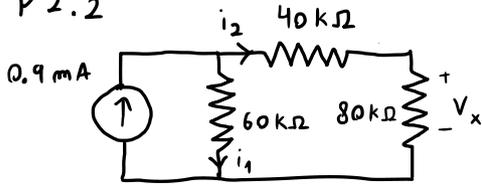

$$I_{\text{suma}}; 0.9\text{mA} = i_2 + i_1$$


$$E; i_2(40\text{k}\Omega + 80\text{k}\Omega) = i_1 \cdot 60\text{k}\Omega$$

$$\text{Logo } i_1 = 0,6\text{mA}$$

$$i_2 = 0,3\text{mA}$$


$$V_x = i_2 \cdot 80\text{k}\Omega = 24\text{V}$$

P 2.3

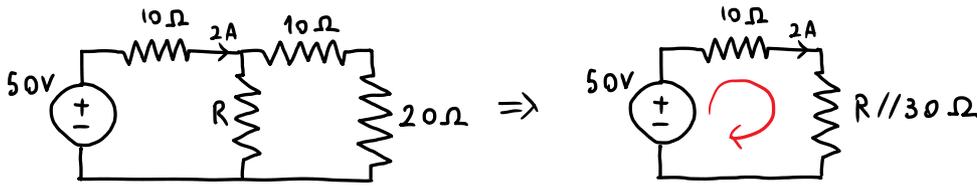

$$50\text{V} = 10\Omega \cdot 2\text{A} + (R // 30\Omega) \cdot 2\text{A} \Leftrightarrow 15 = \left(\frac{1}{R} + \frac{1}{30}\right)^{-1} \Leftrightarrow \frac{1}{15} - \frac{1}{30} = \frac{1}{R} \Leftrightarrow R = 30\Omega$$


P 2.4

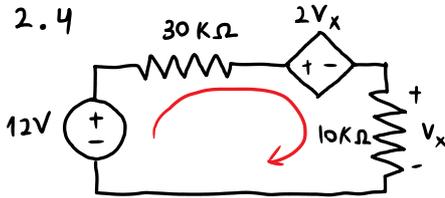

$$\begin{cases} 12\text{V} = 30\text{k}\Omega \cdot I + 2V_x + V_x \\ I = \frac{V_x}{10\text{k}\Omega} \end{cases} \Rightarrow \begin{cases} V_x = 2\text{V} \\ I = 0,2\text{mA} \end{cases}$$

$$P = V \cdot I = R \cdot I^2 = 1,2\text{mW}$$

P 2.5

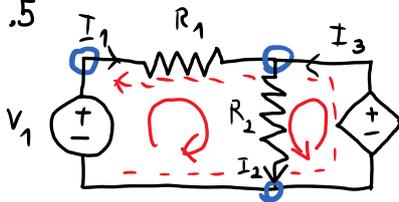

$$V_1 = 10\text{V}$$

a) m<sup>o</sup>: 3 —

$$R_1 = 100\Omega$$

malha: 3 - - - + -

$$R_2 = 200\Omega$$

malha elementar: 2 - -

$$K = 300\Omega$$

b)

$$\begin{cases} R_2 I_2 = V_3 \\ V_1 = R_1 I_1 + R_2 I_2 \\ I_1 + I_3 = I_2 \\ V_3 = K I_1 \end{cases} \Leftrightarrow \begin{cases} \frac{2}{3} I_2 = I_1 \\ I_3 = \frac{1}{3} I_2 \\ 10 = \left(\frac{200}{3} + 200\right) I_2 \\ - \end{cases} \Leftrightarrow \begin{cases} I_1 = 25\text{mA} \\ I_2 = 37,5\text{mA} \\ I_3 = 12,5\text{mA} \\ V_3 = 7,5\text{V} \end{cases}$$

P 2.6

