
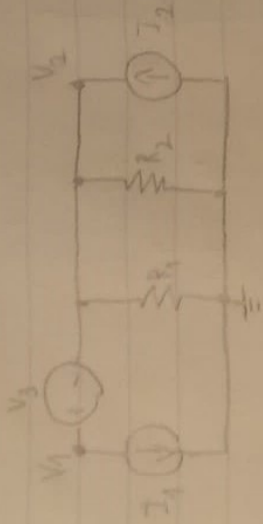

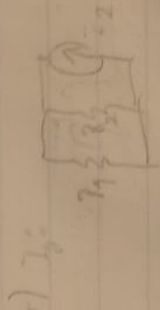
$$\begin{aligned}
 I_1 &= 750 \mu\text{A} \\
 R_1 &= 30 \text{ k}\Omega \\
 R_2 &= 68 \text{ k}\Omega \\
 I_2 &= 460 \mu\text{A} \\
 V_3 &= 1,2 \text{ V}
 \end{aligned}$$




$$\begin{aligned}
 V_a - V_b &= 1,2 \text{ V} \\
 I_1 + \frac{V_b}{R_1} + \frac{V_b}{R_2} - I_2 &= 0 \\
 V_a = V_b &= -5,0444 \text{ V} \\
 V_b = V_2 &= -6,2444 \text{ V}
 \end{aligned}$$




$$V + V'' + V''' = -6,2444 \text{ V}$$
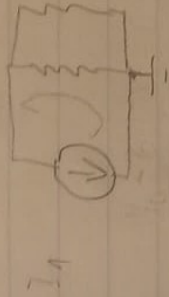
$$V' = \left(\frac{1}{R_1} + \frac{1}{R_2}\right) \cdot I_1 = 9,36735 \text{ V}$$




$$V'' = -15,61224 \text{ V}$$

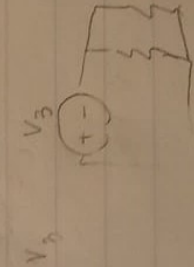


$$V''' = 0 \text{ V}$$

$$V_3 + I_2 (R_1 // R_2)$$

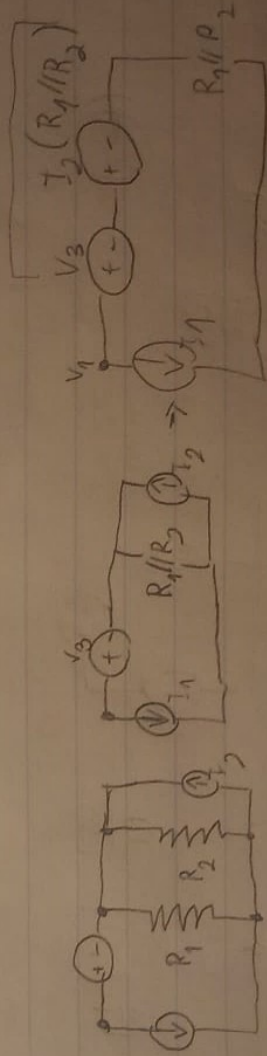
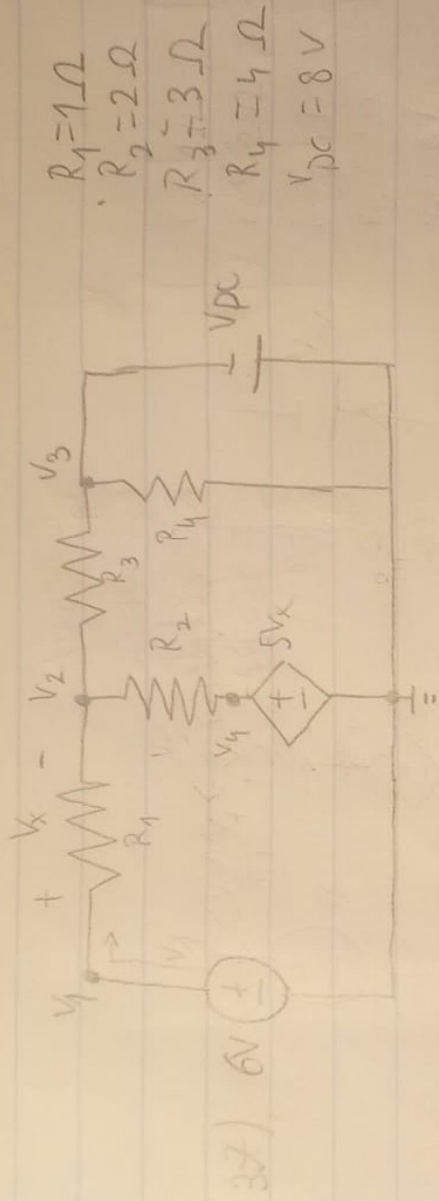
$$\begin{aligned}
 \frac{V_3 + I_2 (R_1 // R_2)}{R_1 // R_2} &= I_1 + \frac{V_a}{R_1 // R_2} \\
 \hookrightarrow V_a &= 5,044 \text{ V}
 \end{aligned}$$



$$R_1 = 1 \Omega$$

$$R_2 = 2 \Omega$$

$$R_3 = 3 \Omega$$

$$R_4 = 4 \Omega$$

$$V_{DC} = 8V$$

a) $V_3 = -8V$

$V_1 = 6V$

$V_4 = 5V_s = (V_1 - V_2) \cdot 5$

$\frac{(V_2 - V_1)}{R_1} + \frac{V_2 - V_4}{R_2} + \frac{V_2 - V_3}{R_3} = 0$

$V_3 = -8V$


$V_1 = 6V$

$V_2 = 1.23V$

$V_4 = 8.8V$

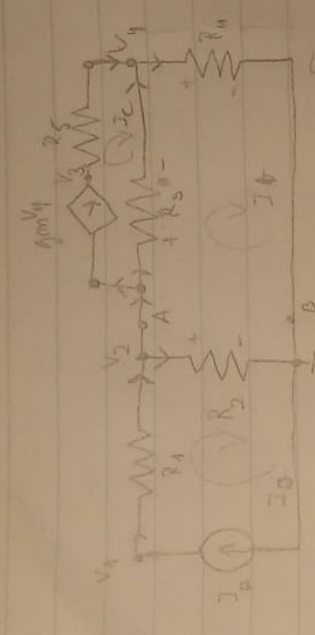c) $P_{V_6} = 6 \cdot (-1.77) = -10.62W$

$R_1 = 2\Omega$
 $R_2 = 5\Omega$
 $R_3 = R_{Th} = 2\Omega$
 $R_5 = 10\Omega$
 $I_0 = 1A$
 $g_m = 2S$




6

$$\begin{bmatrix} 1/R_1 & -1/R_1 & 0 & 0 \\ 1/R_1 & -(1/R_1 + 1/R_2) & 0 & 1/R_3 - g_m \\ 0 & 0 & 1/R_2 & -g_m \\ 0 & 1/R_3 & 1/R_5 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} I_0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$I_0 = \frac{1}{R_1}(v_1 - v_2)$
 $\frac{1}{R_1}(v_1 - v_2) = \frac{1}{R_1}v_1 - \frac{1}{R_1}(v_2 - v_1)$
 $g_m v_4 = \frac{1}{R_2}(v_3 - v_4)$
 $\frac{1}{R_3}(v_3 - v_4) + \frac{1}{R_5}(v_3 - v_4) = \frac{1}{R_4}(v_4)$
 $I_0 = I_A$
 $-(R_2 I_A - I_0) + R_2 (I_A - I_C) + R_4 I_C = 0$
 $I_C = g_m v_4 \Leftrightarrow I_C - g_m I_C \cdot R_4 = 0$

c) $I_A = 1A$ $v_{R_5} = R_5 \cdot I_C \Leftrightarrow v_{R_5} = 10 \cdot 10 = 100V$
 $I_B = 6A$
 $I_C = 20A$

$R = \frac{-20}{-5} = 4\Omega$

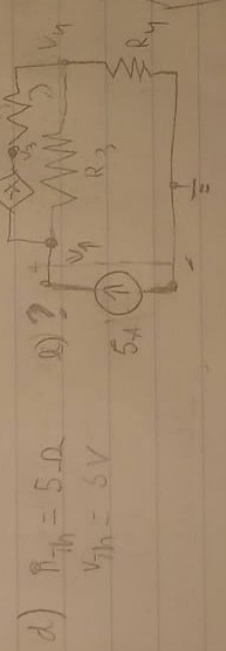

d) $R_{Th} = 5\Omega$
 $v_{Th} = 5V$
 $v_{Th} = 0V$

$$-g_m v_4 + \frac{v_2 - v_4}{R_5} = 0$$

$$-5 + g_m v_4 + \frac{v_1 - v_4}{R_3} = 0$$


$$\frac{v_1}{R_4} + \frac{v_1 - v_4}{R_3} + \frac{v_4 - v_3}{R_5}$$

1.0 (only R_{Th} and R_5) ($R_{Th}, I_N, R_1, R_2, R_3, R_4$)

2.0 (only R_{Th} and R_5) (R_{Th} and I_N)

3.0 (only R_{Th} and R_5) (use no v_{Th} and I_N)

4. R_5 ($v_{Th} = 0$ and $I_N = 0$)

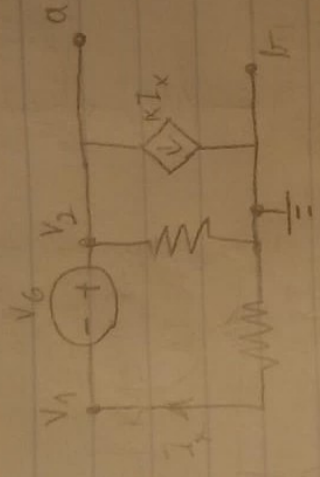

$V_6 = 20V$
 $R = 6k\Omega$
 $k = 1/2$

a)

$$V_2 - V_1 = 20V \quad V_6 = 10V = V_{Th} = V_{a,b}$$

$$\frac{V_1}{R} + \frac{V_2}{R} + (-\frac{1}{2} \frac{V_1}{R}) = 0 \quad V_1 = 20V$$




$$I_2 = I_1 + kI_x \quad I_2 + I_1 + \frac{1}{2} I_x \quad \left| \quad \frac{1}{2} I_x = I_1 \right.$$

$$R(I_2 - I_3) = 0 \quad \Rightarrow \quad \begin{cases} I_2 = I_3 \\ I_3 = I_x \end{cases} \quad \left| \quad -V_6 \cdot R(I_3 - I_2) + R(I_3) = 0 \right.$$

$$I_3 = I_x$$


$$I_1 = I = I_{ab} = I_{cc} = 2.5 \text{ mA}$$

b)

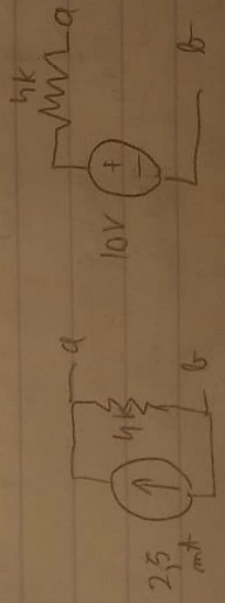

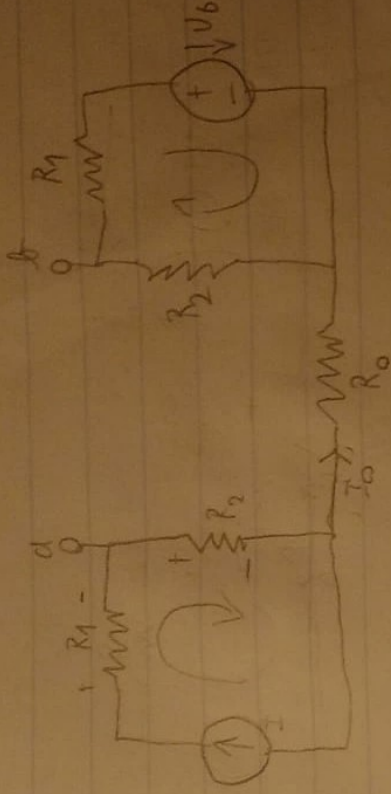3.4


- $V_6 = 20V$
- $I = 20mA$
- $R_0 = 125\Omega$
- $R_1 = 15k\Omega$
- $R_2 = 500\Omega$




a) $I - I = 78 \Rightarrow I_0 = 0$

b) $-V_{ab} + R_2 I + 0 - V_6 \frac{R_2}{R_1 + R_2} = 0 \Rightarrow V_{ab} = 5V$

c) $V_{Th} = 5V$

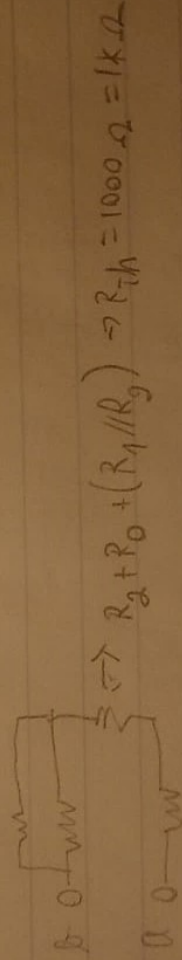




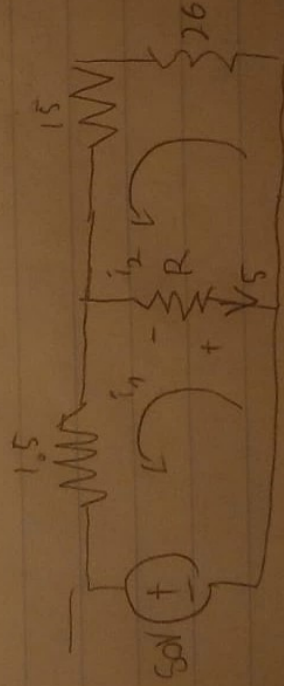
d) $i_{cc} = i_{abr} = \frac{V_{oc}}{R_{Th}} = \frac{5}{1} = 5mA$




$$50 + i_1 \cdot 1.5 - 5R = 0$$

$$5R + 15i_2 + 26i_2 = 0$$

$$i_2 = i_1 + 5$$

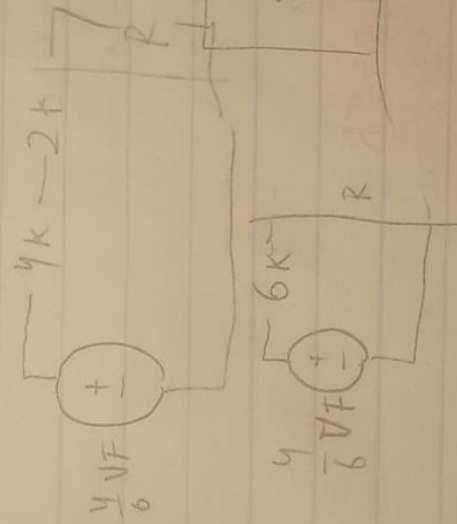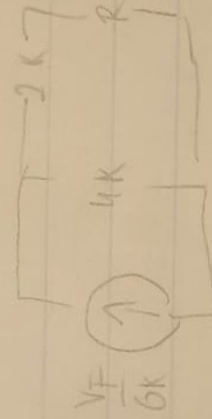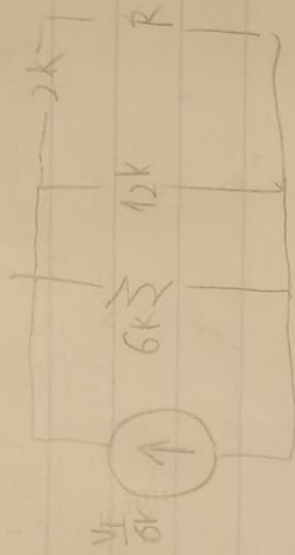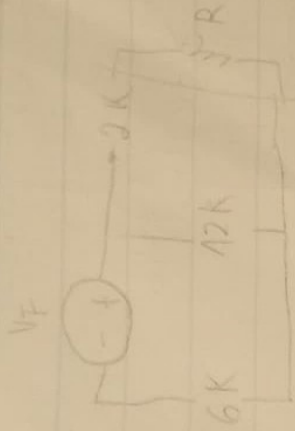

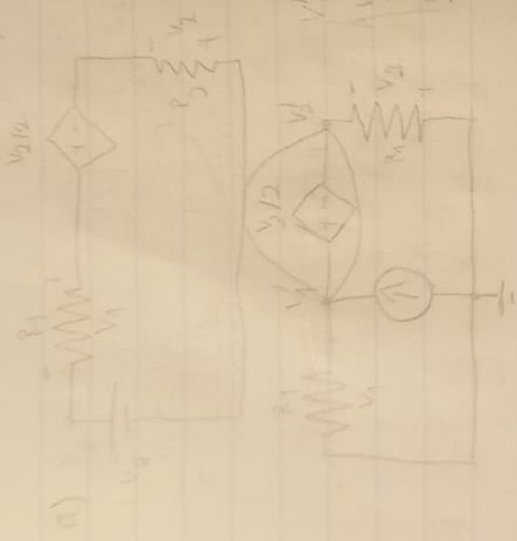3.2 $I_A = 4 \text{ mA}$
 $V_B = 1 \text{ V}$
 $R_1 = 1 \text{ k}\Omega$
 $R_2 = 5 \text{ k}\Omega$



$$v_B + R_2 \cdot I = 0 - \frac{v_2}{2} + R_2 \cdot I$$

$$v_2 = R_2 \cdot I$$

$$I = -0,4$$

$$v_1' = -1,2$$

$$v_2' = -0,4$$

$$v_1 - v_2 = \frac{v_1}{2}$$

$$v_1 = 2v_2$$

$$v_2 = -0,4$$

$$\frac{v_1 - 4 \cdot \frac{v_1}{2}}{1} = 0$$

$$v_1 = 1,4 \text{ V}$$

$$v_2 = 43 \text{ V}$$

$$v_3 = -78 \text{ V}$$

$$v_1 = v_1' + v_2' = -6 \text{ V}$$


$$v_1 = v_1' + v_2' = 2,4 - 0,4 = 2 \text{ V}$$



$$v_B + R_1 \cdot I_1 - \frac{R_2 \cdot I_2}{2} + R_2 \cdot I_2 = 0 \quad I_1 = 2 \text{ mA}$$

$$I_1 = -I_2 + I_A$$

$$I_2 = -2 \text{ mA}$$

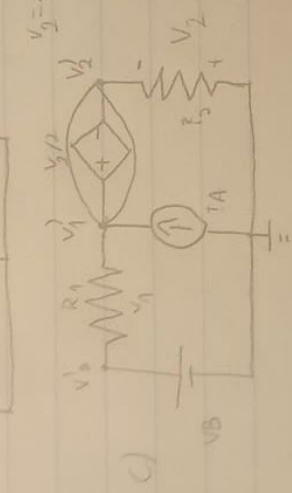

$$v_2 = R_2 \cdot I_2 = 3 \cdot 2 = -6 \text{ V} \quad v_1 = 2 \text{ V}$$

$$-I_A + \frac{v_1 - v_3}{R_1} + \frac{v_2}{R_2}$$

$$v_3 = v_B$$

$$v_1 - v_2 = \frac{v_2}{2}$$

$$v_2 = -v_2$$

$$v_1 = 3$$

$$v_2 = 6$$

$$v_3 = 4$$

$$v_2 = -6$$

$$v_1 = v_3 - v_2 = 2 \text{ V}$$

$$v_2 = -6 \text{ V}$$

d) $P_{v_B} = 2 \cdot 1 = 2 \text{ mW}$


$P_{R_1} = 2 \cdot 2 = 4 \text{ mW}$

$P_{R_2} = -2 \cdot -6 = 12 \text{ mW}$

$P_{I_A} = -3 \cdot 4 = -12 \text{ mW}$

$P_{v_3/2} = -3 \cdot 2 = -6 \text{ mW}$

✓ 3.1

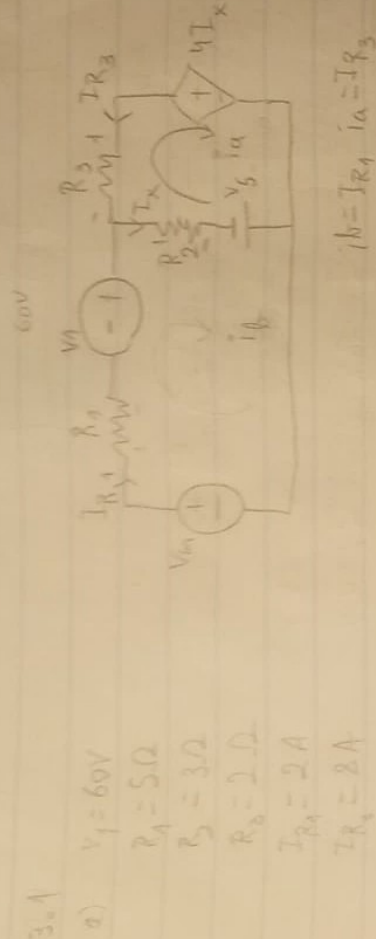

$R_1 = 5\Omega$ $R_2 = 3\Omega$ $R_3 = 2\Omega$
 $I_{R_1} = 2A$ $I_{R_2} = 2A$ $I_{R_3} = 10A$
 $V_{R_1} = 10V$ $V_{R_2} = 6V$ $V_{R_3} = 20V$

$\Leftrightarrow \begin{cases} -V_{im} + 10 - 60 + 3 \cdot 10 - V_S = 0 \\ V_S - 3(10) - 16 + 4 \cdot 10 = 0 \end{cases} \Leftrightarrow \begin{cases} V_{im} = -26 \\ V_S = 6 \end{cases}$

b) $P = 4I_x \cdot (-R_3) = 4 \cdot 10 \cdot -8 = -320W$

c) Satz von Millman

$V_1 = \frac{60}{3} = 20A$

$V_{im} = \frac{-36}{3} = -12A$


$V_S = \frac{5}{3} = 2A$

Nö: $I_x = I_{R_1} + I_{R_3} \Leftrightarrow I_x = 10A$

Millman: $V_S - 3(I_b - I_a) - V_{R_3} + 4I_x = 10A$

d) $V_{TH} = V_4$
 $R_{TH} = 13/4 \Omega$
 $I_N = \frac{V_4}{R_1}$

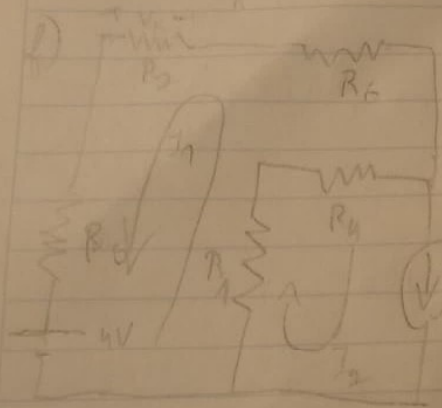1) $I_N = I_E$
 $V_{TH} = V_5$
 $R_{TH} = \frac{V_5}{I_E}$




$I_2 = \frac{V_5}{400}$

$R_1(I_1 + I_2) + R_4(I_1 + I_2) + R_6(I_1) + R_2(I_1) + R_5(I_1) + 4 = 0$

$I_1 + I_2 = -V_x$

$V_x = \frac{2}{5}$

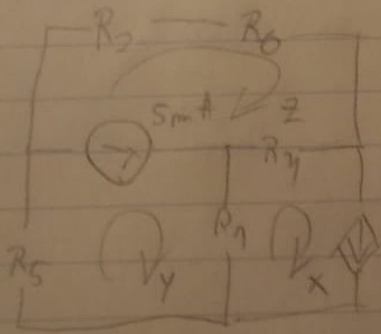

$I_x = \frac{V_x}{400}$

$I_y = 5mA + I_x$

$R_1(I_y - I_x) + R_5(I_y) + R_2(I_y) + R_6(I_x) + R_4(I - I_x) = 0$

$V_x = R_2 \cdot I_x$

$V_x = \frac{3}{4}$

$V_x = \frac{3}{4} + \frac{2}{5} = -0.35V$

3.9 $v_x = 2000 \cdot I_T$

a)

$I_D = \frac{v_x}{4000} \Rightarrow I_D = \frac{2000 \cdot I_T}{4000} \Rightarrow I_D = \frac{1}{2} I_T \Rightarrow I_D - \frac{1}{2} I_T = 0$

b)

$-4 + R_5 I_E + R_2 I_T + R_6 I_T + R_4 (I_T - I_D) + R_1 (I_E - I_D) = 0$

$I_E = I_T + 5$

$I_E = \frac{13}{4000}$

$$\begin{bmatrix} 1 & 0 & -1 \\ 0 & 1 & -\frac{1}{2} \\ R_5 + R_1 & -R_1 - R_4 & R_2 + R_6 + R_4 \end{bmatrix} \cdot \begin{bmatrix} I_E \\ I_D \\ I_T \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 4 \end{bmatrix}$$

$I_D = \frac{7}{8000}$

$I_T = \frac{7}{1000}$

b) $v_x = 4V$ $\frac{v_x}{R_5} + 5 + \frac{(v_1 - v_2)}{R_2} = 0$

$(v_1 - v_2) + 5 + \frac{(v_1 - v_2)}{R_2} = 0$

$\frac{v_2 - v_1}{R_2} + \frac{v_2 - v_1}{R_6} = 0$

$v_1 = \frac{19}{8} V$

$v_2 = \frac{109}{40} V$

$v_3 = \frac{33}{6} V$

$v_4 = \frac{151}{400} V$

$v_5 = 4$

$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix} = \begin{bmatrix} 4 \\ -5 \\ 0 \\ 5 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 0 & 0 & 0 & 1 & 0 \\ \frac{1}{R_5} + \frac{1}{R_2} & -\frac{1}{R_2} & 0 & 0 & -\frac{1}{R_5} \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_6} & 0 & -\frac{1}{R_6} & 0 \\ 0 & 0 & \frac{1}{R_4} + \frac{1}{R_1} & -\frac{1}{R_1} & 0 \\ -\frac{1}{400} & -\frac{1}{400} & -\frac{1}{R_6} & \frac{1}{R_4} & \frac{1}{R_6} + \frac{1}{R_4} \end{bmatrix} \cdot \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

c) $I_D \cdot v_x = \frac{151}{40} \cdot \frac{7}{1000} = -0.0033 W = -3.3 mW$