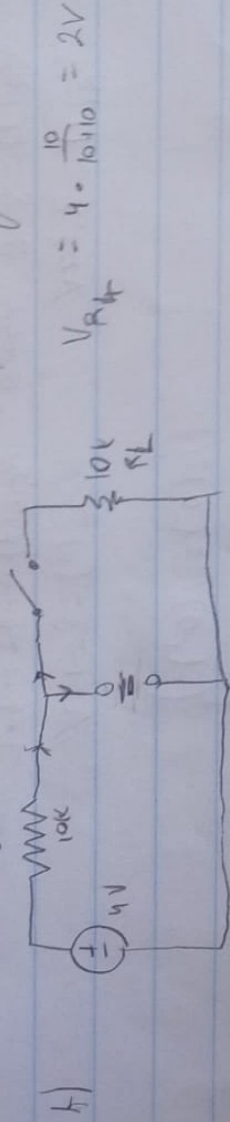


$$4.1) \left(\frac{1}{\frac{1}{4+4} + \frac{1}{6}} + 2 \right)^{-1} = 2,85 \mu F$$

$$b) \left(\frac{1}{\left(\frac{1}{4} + \frac{1}{12}\right)^{-1} + 3} + \frac{1}{4+2} \right)^{-1} + 1 + 2 = 6 \text{ mH}$$

4.2)

$$d) W = \frac{1}{2} C V^2 = \frac{1}{2} \cdot 100 \cdot 4^2 \times 10^{-6} = 0,0008 \text{ J} = 0,8 \text{ mJ}$$



$$V_{R4} = 4 \cdot \frac{10}{10+10} = 2V$$

c)


$$V_C(t) = K_1 + K_2 e^{-t/\tau}$$

$$V_C(\infty) = 2 + 2 e^{-\frac{t}{0,5}}$$


$$V_C(0) = K_1 + K_2 = 4V \Leftrightarrow \begin{cases} K_1 = 2 \\ K_2 = 2 \end{cases}$$

$$V_C(\infty) = 2V = K_1$$
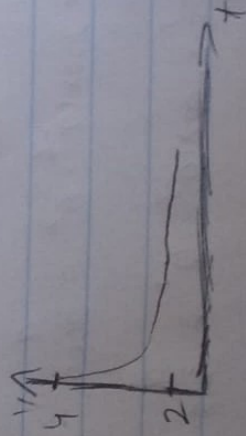
$$\tau = R_{Th} C = 100 \times 10^{-3} \times 100 \times 10^{-6} = 0,01$$




4.3) $V_C(0^-) = V_C(0^+) = 10V$

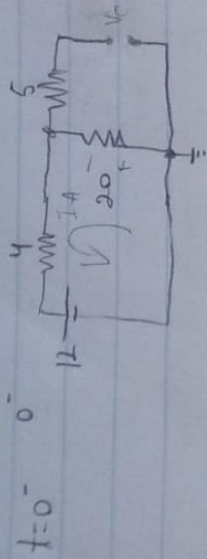

$I_A = -0.5A$

$20 \cdot 0.5 = 10V$

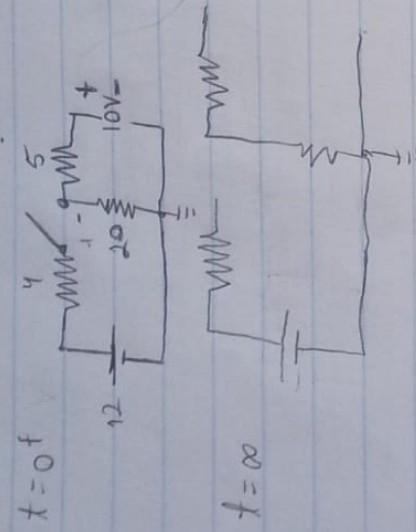$\tau = R_{Th} \cdot C = 80m \cdot 25 = 2000 \times 10^{-3}$



$V_C(0^+) = 10V$
 $V_R(0^+) = 10 \cdot \frac{20}{5+20} = 8V \rightarrow K_1 \cdot K_2$
 $V_{SW}(0^+) = 12 - 8 = 4$

$V_C(\infty) = 0V$
 $V_R(\infty) = 0V$
 $V_{SW}(\infty) = 12V$

$V_C(t) = 10e^{-\frac{t}{2000 \times 10^{-3}}}$
 $V_R(t) = 8 \cdot e^{-\frac{t}{2000 \times 10^{-3}}}$
 $V_{SW}(t) = 12 - 8 \cdot e^{-\frac{t}{2000 \times 10^{-3}}}$
 $V_C(1) = 4.499V$
 $V_R(1) = 3.59V$
 $V_{SW}(1) = 8.41V$

$(i_L(0^-) = i_L(0^+))$
 $(V_C(0^-) = V_C(0^+))$

4.4) $i_L(0) = \frac{10}{2} = 5A$
 $V_L(0) = 0$
 $V_C(0) = \frac{12}{20} \cdot 10 = 6V$

$i_L(\infty) = \frac{20}{8} = 2.5A$
 $V_L(\infty) = 0$
 $V_C(\infty) = \frac{12}{20} \cdot 20 = 12V$

$W_L(0) = \frac{1}{2} \cdot 3 \cdot 10^{-3} \cdot 5^2 = \frac{3}{80} J$
 $W_L(\infty) = \frac{1}{2} \cdot 3 \cdot 10^{-3} \cdot 2.5^2 = \frac{3}{200} J$
 $W_C(0) = \frac{1}{2} \cdot 200 \times 10^{-6} \cdot 6^2 = \frac{d}{2600} = 3.6 \mu W$

$W_L(\infty) = \frac{1}{2} \cdot 3 \cdot 10^{-3} \cdot 10^2 = \frac{3}{200} J$
 $W_C(\infty) = \frac{1}{2} \cdot 200 \times 10^{-6} \cdot 12^2 = \frac{d}{625} = 14.4 \mu W$


$0^+ \rightarrow$

$i_L(0^+) = 5A$ (lego)

$V_C(0^+) = 6V$

$V_L(0^+) = 8.3V$

$i_C(0^+) = 12.5A$

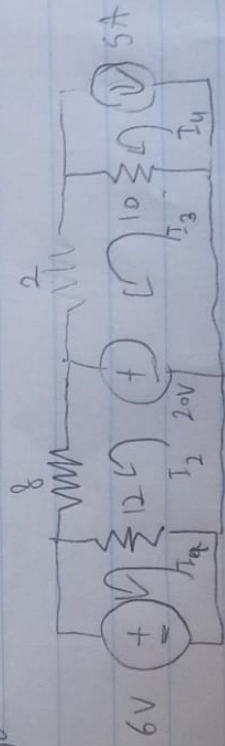

$I_4 = 5A$

$W_L(0^+) = W_L(\infty)$

$W_C(0^+) = W_C(\infty)$

$I_3: 10(I_3 - I_4) + 20V = 0$

$I_2: -20 + 8(I_2) + 12(I_2 - I_1) = 0$


$I_1: 12(I_1 - I_2) + 6 = 0$

$I_4 = -5$


$I_3 = -5.8(3)$

$I_2 = 1.75$

$I_1 = 1.25$

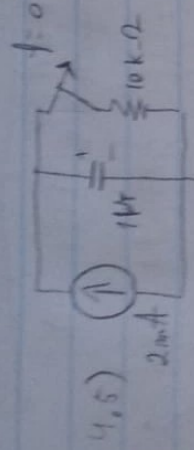


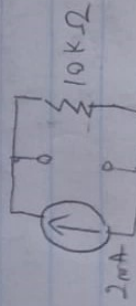a) $w_c = \frac{1}{2} \cdot C \cdot V^2 =$
 $= \frac{1}{2} \cdot 1 \cdot 10^{-6} \cdot 20^2 =$
 $= 2 \cdot 10^{-4} \text{ J}$



$V = 2 \cdot 10^{-3} \cdot 10 \cdot 10^3 = 20 \text{ V}$

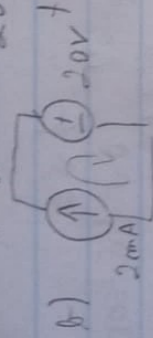$P = 2 \cdot 10^{-3} \cdot 20 = 0.04 \text{ W}$



$10000 \text{ J/m}^2 \text{ rad}$

$2 \cdot 10^{-3} = 1000 \frac{dV}{dt} \Rightarrow \frac{dV}{dt} = 2000 \Rightarrow V = 2000t + K$


$V = 2000t + 20$

$t_1 = t = 15 \text{ ms}$

$V_c(t_1) = 50 \text{ V}$

c) $V_c(t_1) = 50 \text{ V}$

$V_c(\infty) = 20 \text{ V}$

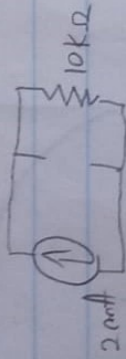

$K_1 + K_2 = 50$
 $K_1 = 20$

$V(t) = K_1 + K_2 e^{-t/\tau}$




$\frac{t - 15 \text{ ms}}{10 \cdot 10^{-3}}$

$V(t) = 20 + 30 e^{-\frac{t - 15 \text{ ms}}{10 \cdot 10^{-3}}}$

$t = t_2 = 30 \text{ ms}$

$V(t_2) = 20 + 30 e^{-\frac{15 \text{ ms}}{10 \cdot 10^{-3}}} \approx 26.69$


$i_c = \frac{dV_c}{dt}$

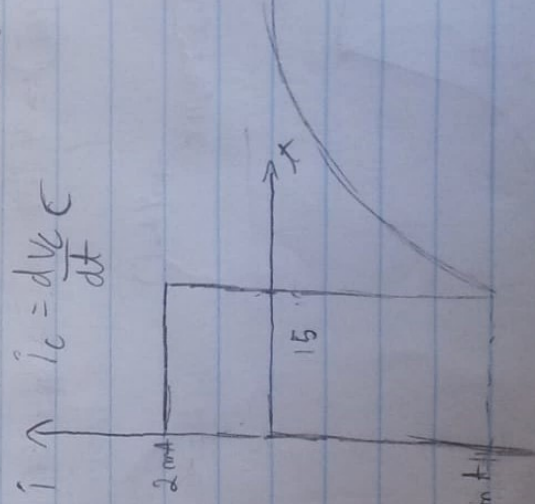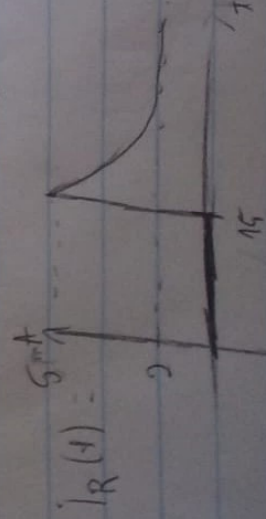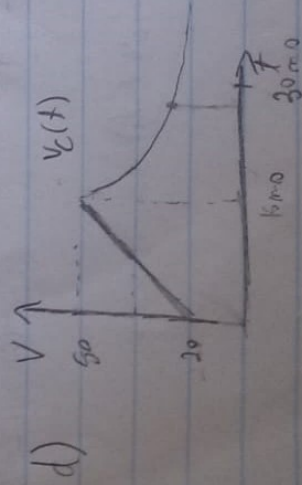

$$d) P_F = i(t) \cdot v(t) = 2 \times 10^{-3} \cdot v_c(t) = 2 \times 10^{-3} \cdot \begin{cases} 2000t + 120 & 0 \leq t < 15 \text{ ms} \\ 20 + 30e^{-\frac{t-15}{10}} & t = 15 \text{ ms} \end{cases}$$


$$W_F = \int_0^{30} P_F dt = \int_0^{15} 2 \times 10^{-3} (2000t + 120) dt + \int_{15}^{30} 2 \times 10^{-3} (20 + 30e^{-\frac{t-15}{10}}) dt = 0.15 = 150 \mu\text{J}$$
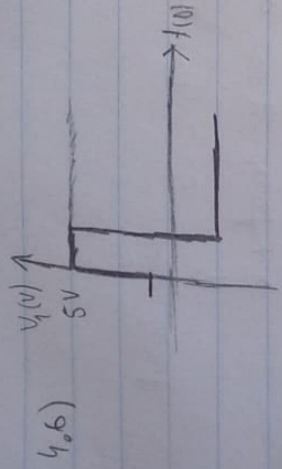
$$W_R = \frac{21}{20000} (6e^{\frac{3}{2}} - 3) = 2.116 \text{ mJ}$$



$$v_c(t) = \begin{cases} 5 - 4e^{-10^4 t} & 0 \leq t < 150 \mu\text{s} \\ -2 + 4.11e^{-10^4(t-t_1)} & t > 150 \mu\text{s} \end{cases}$$
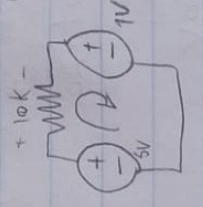
$$v_R(t) = \begin{cases} 0 & t \leq 0 \\ 4e^{-10^4 t} & 0 \leq t < 150 \mu\text{s} \\ -6.11e^{-10^4(t-t_1)} & t > 150 \mu\text{s} \end{cases}$$



da 5 pinnen = 2

$$v_c(0^-) = v_c(0^+) = 1V$$

$$v_R(0^-) = v_R(0^+) = 4V$$

$$v_c(\infty) = 5V = k_1$$

$$v_R(\infty) = 0$$

$$k_1 = 5V \quad k_2 = -4V \quad \tau = 10 \cdot 10^{-3} \cdot 10 \cdot 10^{-9} = 10^{-4}$$

$$v_c(t) = 5 - 4e^{-10^4 t} \quad v_R(t) = 4e^{-10^4 t}$$



da 5 pinnen = 2

$$v_c(150 \mu\text{s}^+) = v_c(150 \mu\text{s}^-) = 4.11V$$

$$v_c(\infty) = -2$$

$$k_1 = -2 \quad v_c(t) = -2 + 4.11e^{-10^4(t-t_1)}$$

$$k_2 = 4.11$$

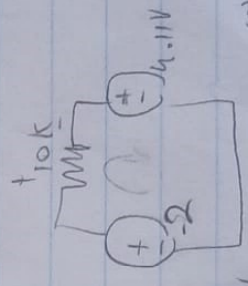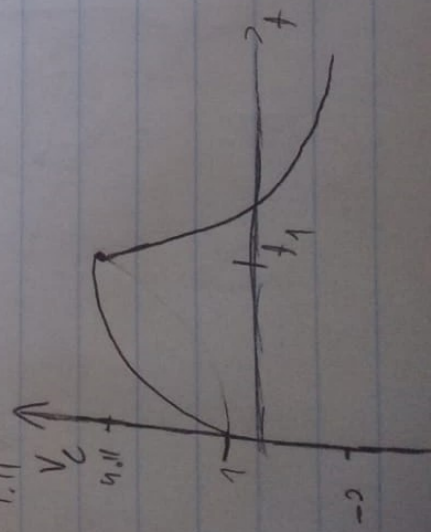


$$v_R(150 \mu\text{s}^+) = 6.11V$$

$$v_R(\infty) = 0$$

$$v_R(t) = -6.11e^{-10^4(t-t_1)}$$

$$-(2) \cdot 4.11 = -1/R$$

4.7

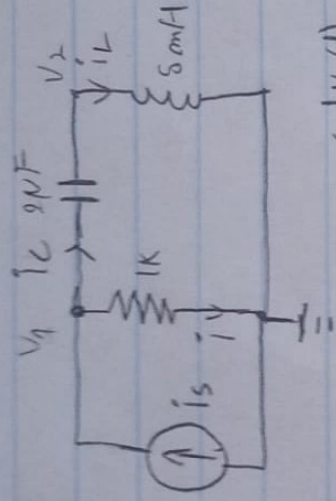

a)

$$\begin{cases} i_s = i_c + i_l & \Leftrightarrow i_s = \frac{v_1(t)}{R} + C \left(\frac{dv_2(t)}{dt} - \frac{dv_3(t)}{dt} \right) \\ i_l = i_c & \Leftrightarrow C \left(\frac{dv_2(t)}{dt} - \frac{dv_3(t)}{dt} \right) = \frac{1}{L} \int_0^t v_2(x) dx + i_l(0) \end{cases}$$

b)

$$\int \frac{1}{C} \int_0^t i_c(x) dx + R(i_c(t) - i_s(t)) + L \frac{di_c(t)}{dt} + v_c(0) = 0$$