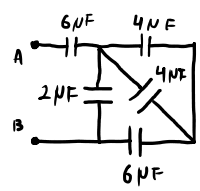
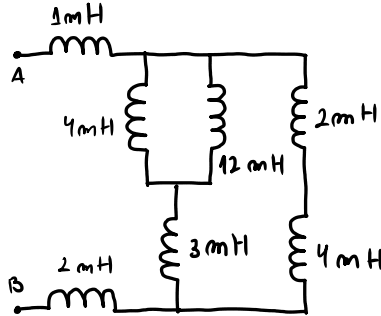


4.1) a) 
$$\left(\left[(4\mu F // 4\mu F) + 6\mu F \right] // 2\mu F \right) + 6\mu F = \left(\frac{1}{\left(\frac{1}{4+4} + \frac{1}{6} \right)^{-1} + 2} + \frac{1}{6} \right)^{-1} = 2,85\mu F$$

 // - Paralelo
 + - Série

b) 
$$(2\text{ mH} + 4\text{ mH}) // \left[(4\text{ mH} // 12\text{ mH}) + 3\text{ mH} \right] + 1\text{ mH} + 2\text{ mH} = 6\text{ mH}$$

4.2) a) $W_C = \frac{1}{2} \cdot C \cdot V_C^2 = \frac{1}{2} \cdot 100 \cdot 10^{-6} \cdot 4^2 = 0,8\text{ mJ}$
 $C = 100 \times 10^{-6}\text{ F}$
 $V_C = 4\text{ V}$

b) Em $t = \infty$:

$$V_C = 4 \cdot \frac{10}{10+10} = 2\text{ V}$$

$$V_{R_L} = V_C \Rightarrow V_{R_L} = 2\text{ V}$$

c) $V_C(t) = k_1 + k_2 e^{-t/\tau}$ (solução tipo)


$$\begin{cases} V_C(0) = k_1 + k_2 \\ V_C(\infty) = k_1 \end{cases} \text{ temos tambem que } \begin{cases} V_C(0) = 4\text{ V} \\ V_C(\infty) = 2\text{ V} \end{cases}$$

$$\tau = R_{Th} \cdot C = 5 \times 10^3 \times 100 \times 10^{-6} = 0,5$$

Logo $k_1 = 2$
 $k_2 = 2$

Temos então: $V_C(t) = 2 + 2e^{-\frac{t}{0,5}}$

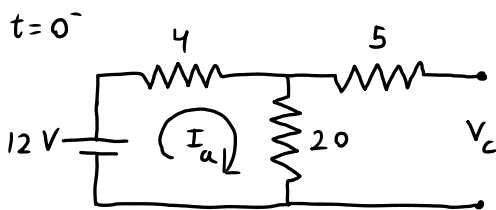4.3) a) $V_C(0^-) = V_C(0^+) = 10\text{ V}!$



$$I_a = \frac{12}{20+4} = 0,5\text{ A}$$

$$V_C = 20 \cdot 0,5 = 10\text{ V}$$


$$\tau = R_{Th} \cdot C = 25 \cdot 50\text{ ms} = 1,25$$

Pelo método de k_1 e k_2 : $V_C(t) = 10 e^{-\frac{t}{1,25}}$

$$V_C(1) = 4,49\text{ V}$$

$$V_R(t) = 8 \cdot e^{-\frac{t}{1,25}}$$


$$V_R(1) = 3,59\text{ V}$$

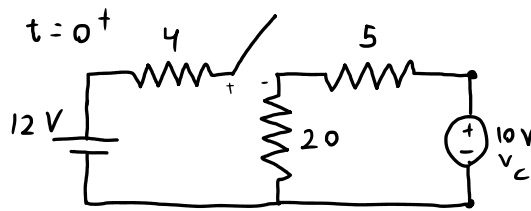

$$V_C(0^+) = 10\text{ V}$$

$$V_R(0^+) = 10 \cdot \frac{20}{20+5} = 8\text{ V}$$

$$V_{Sw}(0^+) = 12 - 8 = 4\text{ V}$$

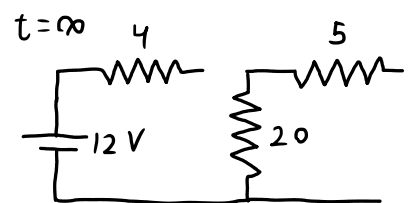

$$V_C(\infty) = 0$$


$$V_R(\infty) = 0$$

$$V_{Sw}(\infty) = 12\text{ V}$$


$$V_{Sw}(t) = 12 - 8 e^{-\frac{t}{1,25}}$$

$$V_{Sw}(1) = 8,41\text{ V}$$

4.4) Em $t=0$:

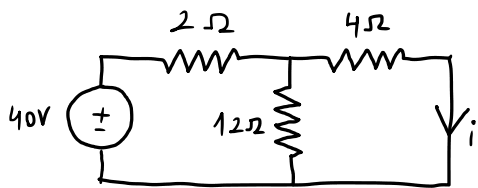

Em $t=\infty$:

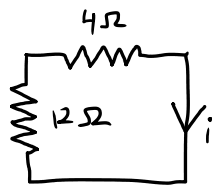

$$i(0) = 6 \text{ A} \quad Z = \frac{R}{L} = \frac{8}{2} = 4$$

$$i(\infty) = 0 \text{ A}$$


$$i(t) = k_1 + k_2 e^{-\frac{t}{Z}}$$

$$i(t) = 6 e^{-\frac{t}{4}}$$

4.5) a) $W_c = \frac{1}{2} \cdot C \cdot V^2 = \frac{1}{2} \cdot (1 \cdot 10^{-6}) \cdot (2 \cdot 10^{-3} \cdot 10 \cdot 10^3)^2 = 2 \times 10^{-4} \text{ J}$

$P = I \cdot V = 2 \cdot 10^{-3} \cdot (-20) = -0.04 \text{ W}$

b)

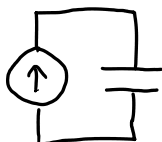

$$i = C \frac{dV}{dt} \Leftrightarrow \frac{i}{C} = \frac{dV}{dt} \Leftrightarrow \frac{dV}{dt} = 2000 \Leftrightarrow V = 2000t + k$$

↑ tensão inicial

$V(t) = 2000t + 20$

$V(t_1) = 2000(15 \text{ ms}) + 20 = 50 \text{ V}$

c) $V_c(t_1) = 50 \text{ V} \quad V(t) = k_1 + k_2 e^{-\frac{t-15 \text{ ms}}{\tau}}$

$V_c(\infty) = 20 \text{ V} \quad k_1 + k_2 = 50$


$k_1 = 20$

$Z = 10 \cdot 10^3 \cdot 1 \cdot 10^{-6} = 10 \cdot 10^{-3}$


Logo $V(t) = 20 + 30 e^{-\frac{t-15 \text{ ms}}{10 \cdot 10^{-3}}}$

$V(t_2) = V(30 \text{ ms}) = 26.69 \text{ V}$


d)

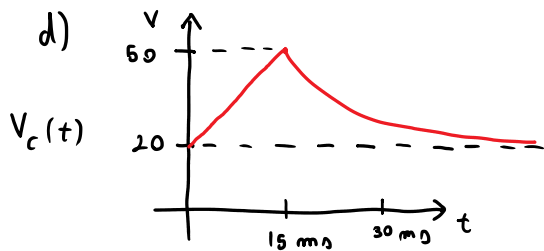

$$i_c = \frac{dV_c}{dt} \cdot C$$

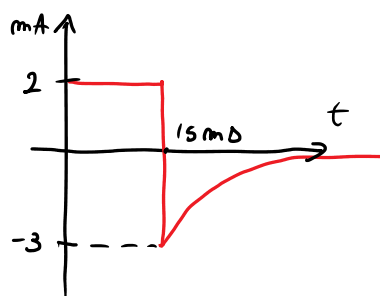

$i_R(t)$

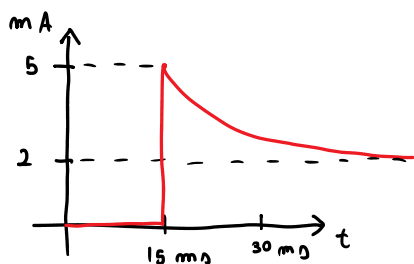

4.6) De 1 para 5:

$$V_C(0^-) = V_C(0^+) = 1$$

$$V_C(\infty) = 5V$$

$$Z = R \cdot C = 10^{-4}$$

$$\text{Logo } V_C(t) = 5 - 4e^{-10^4 t}$$

$$V_R(0^+) = 4V$$

$$V_R(\infty) = 0$$

$$V_R(t) = 4e^{-10^4 t}$$

De 5 para -2:

$$V_C(150\mu s) = 4.11V$$

$$V_C(\infty) = -2$$

$$Z = 10^{-4}$$

$$\text{Logo } V_C(t) = -2 + 6.11e^{-10^4(t-t_1)}$$

$$V_R(150\mu s) = -6.11V$$

$$V_R(\infty) = 0$$

$$V_R(t) = -6.11e^{-10^4(t-t_1)}$$

$$V_C = \begin{cases} 1 & , t \leq 0 \\ 5 - 4e^{-10^4 t} & , 0 \leq t \leq t_1 \\ -2 + 6.11e^{-10^4(t-t_1)} & , t \geq t_1 \end{cases}$$

$$V_R = \begin{cases} 0 & , t \leq 0 \\ 4e^{-10^4 t} & , 0 \leq t \leq t_1 \\ -6.11e^{-10^4(t-t_1)} & , t \geq t_1 \end{cases}$$

