

5.1)

$$Z_L = \frac{V_L}{I_L}$$

d)

$$Z_L = j\omega L$$

$$Z_R = R$$

$$I_L = I_S \cdot \frac{R}{j\omega L + R}$$

$$V_L = Z_L \cdot I_L = V_0$$

$$V_0 = I_S \cdot \frac{R}{j\omega L + R} \cdot j\omega L = I_S \cdot \frac{j\omega L R}{R + j\omega L}$$

$$b) \left| \frac{V_0}{I_S} \right| = \left| \frac{j\omega L R}{R + j\omega L} \right| = \frac{\omega L R}{\sqrt{R^2 + \omega^2 L^2}}$$

$$\frac{\omega}{\sqrt{(1 \times 10^3)^2 + \omega^2 (1 \times 10^{-3})^2}} = 0,707 \Rightarrow \omega = 0,707 \sqrt{10^6 + \omega^2 \cdot 10^{-6}} = 0$$

$$\sqrt{\Rightarrow \omega = 707}$$

$$f = \frac{\omega}{2\pi} = \frac{707}{2\pi} = 112,5 \text{ Hz}$$

So2) a) máo!

Divisor

$$\text{de corrente } I_{AB} = I_S \cdot \frac{R_1}{R_1 + \frac{1}{C_2 j\omega} + R_2} = I_S \cdot \frac{C_2 j\omega R_1}{C_2 j\omega (R_1 + R_2) + 1}$$


$$V_{AB} = R_2 \cdot I_{AB} = I_S \cdot \frac{C_2 j\omega R_1 R_2}{C_2 j\omega (R_1 + R_2) + 1}$$

$$Z_{ab} = (Z_{C_2} + Z_{R_1}) \parallel Z_{R_2} = \left(\frac{1}{C_2 j\omega} + R_1 \right) \parallel R_2 = \frac{1 + R_1 C_2 j\omega}{C_2 j\omega} \parallel R_2 =$$

$$\left(\frac{C_2 j\omega}{1 + R_1 C_2 j\omega} + \frac{1}{R_2} \right)^{-1} = \frac{R_2 (1 + R_1 C_2 j\omega)}{1 + R_1 C_2 j\omega + R_2 C_2 j\omega} \parallel R_2 = \frac{R_2 (1 + R_1 C_2 j\omega)}{1 + (R_1 + R_2) j\omega C_2} \parallel R_2$$

b) $V_{oc} = V_{ab}$

$Z_{Th} = \frac{V_{oc}}{I_{cc}}$

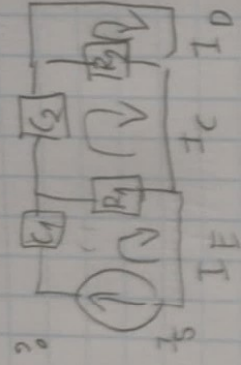

$I_{cc} = ?$

$I_E = I_S$

$R_1(I_C - I_E) + \frac{1}{C_2 j\omega}(I_C) + R_2(I_C - I_D) = 0$

$I_D = I_{cc}$

$R_2(I_D - I_C) = 0$

$I_E = I_S$

$I_D = I_C$

$R_1 I_C - R_1 I_S + \frac{1}{C_2 j\omega} I_C = 0 \Rightarrow I_C (R_1 + \frac{1}{C_2 j\omega}) = R_1 I_S \Leftrightarrow$

$\Rightarrow I_C = I_D = I_{cc} = \frac{R_1 I_S}{R_1 + \frac{1}{C_2 j\omega}} = \frac{R_1 C_2 j\omega I_S}{R_1 C_2 j\omega + 1}$

$\frac{V_{AB}}{I_{cc}} = \frac{j\omega C_2 R_1 R_2 I_S}{1 + j\omega C_2 (R_1 + R_2)} \cdot \frac{R_1 C_2 j\omega + 1}{R_1 R_2 j\omega I_S} = \frac{R_2 R_1 C_2 j\omega + R_2}{1 + j\omega C_2 (R_1 + R_2)} = Z_{Th}$

S.3) 1) (Vou apleas maai asociatim)

$= (L_2 j\omega + \frac{1}{C_2 j\omega}) // \frac{1}{C_1 j\omega} + L_1 j\omega = \frac{1 - L_2 C_2 \omega^2}{C_2 \omega j} // \frac{1}{C_1 j\omega} + L_1 j\omega =$

$= \left(\frac{C_2 \omega j}{1 - L_2 C_2 \omega^2} + C_1 j\omega \right)^{-1} + L_1 \omega j = \frac{C_2 \omega j + C_1 j\omega (1 - L_2 C_2 \omega^2)}{1 - L_2 C_2 \omega^2} + L_1 \omega j =$

$= j\omega L_1 + \frac{1 - L_2 C_2 \omega^2}{C_2 \omega j + C_1 j\omega (1 - L_2 C_2 \omega^2)}$

$= j \left(\omega L_1 + \frac{1 - L_2 C_2 \omega^2}{1 + \frac{C_2}{C_1} - \omega^2 C_2 L_2} \cdot \frac{1}{\omega C_1} \right)$


$$\begin{aligned}
 2) \quad Z &= (Z_{C_2} + Z_{L_2}) \parallel Z_{L_1} + Z_{C_1} = \\
 &= \left(\frac{1}{C_2 j\omega} + L_2 j\omega \right) \parallel L_1 j\omega + \frac{1}{C_1 j\omega} = \\
 &= \frac{1 - L_2 C_2 \omega^2}{C_2 j\omega} \parallel L_1 j\omega + \frac{1}{C_1 j\omega} = \\
 &= \left(\frac{C_2 j\omega}{1 - L_2 C_2 \omega^2} + L_1 j\omega \right)^{-1} + \frac{1}{C_1 j\omega} = \\
 &= \left(\frac{C_2 j\omega L_1 j\omega - L_2 C_2 \omega^2 + 1}{L_1 j\omega (1 - L_2 C_2 \omega^2)} \right)^{-1} + \frac{1}{C_1 j\omega} = \\
 &= j \left(\frac{\omega L_1 (1 - L_2 C_2 \omega^2)}{1 - \omega^2 C_2 (L_1 + L_2)} \right) - \frac{1}{C_1 j\omega}
 \end{aligned}$$

5.4)

$$i_G(t) = 5 \cos(1000t + \frac{\pi}{4})$$

a) $i_G(t) = 5 e^{j\pi/4}$

b) $V_C(t) = R$

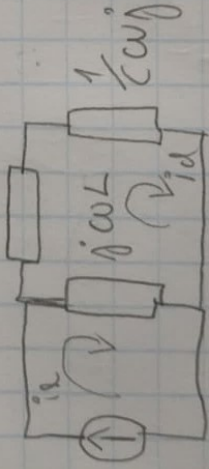

$$i_x = i_g$$

$$j\omega L (i_d - i_x) + R i_d + \frac{1}{C\omega j} i_d = 0 \Leftrightarrow \frac{j\omega L i_x = i_d}{j\omega L + R + \frac{1}{C\omega j}}$$

$$V_C = \frac{1}{C\omega j} \cdot \frac{j\omega L i_g}{j\omega L + R + \frac{1}{C\omega j}}$$


$$F = \frac{j\omega L}{C\omega j (j\omega L + R + \frac{1}{C\omega j})} = \frac{j\omega L}{1 - \omega^2 C L + j\omega C R}$$

$$c) v_C = i_C \cdot \left[\frac{j \omega L}{1 - \omega^2 LC + j \omega RC} \right]$$

↓ Calculadora
 1/2 substitui valores

$$v_C = \frac{1}{2} \cdot i_C = \frac{1}{2} \cdot 5 \cdot e^{j(4t - \frac{\pi}{4})} = 2.5 e^{j(4t - \frac{\pi}{4})}$$
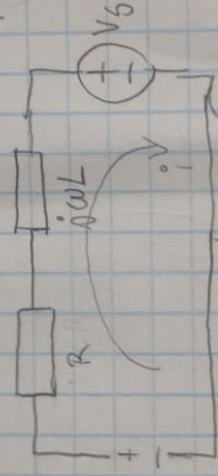
$$v_C(t) = 2.5 \cos(1000t + \frac{\pi}{4})$$



5.5)

$$i(t) = 0.8 \cos(20t) = 0.8 \cos(20t - \frac{\pi}{2}) = 0.8 e^{j(20t - \frac{\pi}{2})}$$

$$iR + j\omega L + v_C + v_{im} = 0$$

$$\rightarrow 0.8 e^{-j\frac{\pi}{2}} \cdot 100 + 0.8 e^{-j\frac{\pi}{2}} \cdot j \cdot 20 \cdot 10 + 60 e^{-j\frac{\pi}{2}} = v_{im}$$

Calculadora
 para
 resolver

$$\approx 120 - 110j = v_{im} \quad j \cdot 19 - \left(\frac{-110}{120}\right)$$


$$\sqrt{120^2 + (-110)^2} e^{j(19 - \frac{-110}{120})} \rightarrow 162 \cos(20t - 0.741)$$

$$-0.741 = -42.05 \cdot \frac{\pi}{180}$$

5.6)

$\omega = 500$

a)

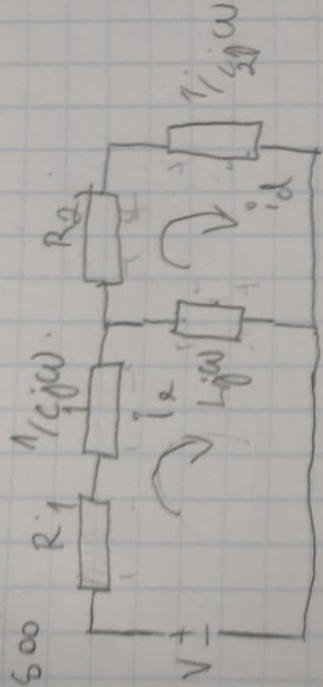

$i_d = i_e$

$$R_1 i_e + \frac{1}{C_1 j\omega} (i_e) + L j\omega (i_e - i_d) - V = 0$$

$$L j\omega (i_d - i_e) + R_2 (i_d) + \frac{1}{C_2 j\omega} (i_d) = 0$$

$\Rightarrow V = 230.24 + 18.92 \angle 18.42^\circ$

$\hookrightarrow 29.96 e^{i(-0.68)}$

$\hookrightarrow 29.96 \angle -39.2^\circ$

$\hookrightarrow 29.96 \cos(500t - \frac{39.2}{180} \pi)$

b) $(R_2 + \frac{1}{C_2 j\omega}) \parallel (L j\omega) + R_1 + \frac{1}{C_1 j\omega} = \frac{97}{13} + \frac{61}{10} j$

$\hookrightarrow 8.81 e^{i0.561375}$

$\hookrightarrow 8.81 \angle 32.2^\circ$