

5.1) a) $Z_R = R$ $V_L = Z_L \cdot I_L = V_0$
 $Z_L = j\omega L$ $I_L = I_S \cdot \frac{R}{j\omega L + R} \Rightarrow V_0 = I_S \cdot \frac{j\omega L R}{j\omega L + R}$

b) $\left| \frac{V_0}{I_S} \right| = \left| \frac{j\omega L R}{j\omega L + R} \right| = \frac{\omega L R}{\sqrt{R^2 + \omega^2 L^2}}$

$\frac{\omega L R}{\sqrt{R^2 + \omega^2 L^2}} = 0,707$ Com $R = 1k\Omega$ Logo $\omega = 707$ e $f = \frac{\omega}{2\pi} = 112,5 \text{ Hz}$
 $L = 1 \text{ mH}$

5.2) a) $V_{AB} = R_2 \cdot I_{AB}$

Temos um divisor de corrente logo:

$I_{AB} = I_S \cdot \frac{R_1}{R_1 + R_2 + \frac{1}{j\omega C_2}} = I_S \cdot \frac{C_2 j\omega R_1}{C_2 j\omega (R_1 + R_2) + 1}$

Logo $V_{AB} = I_S \cdot \frac{C_2 j\omega R_1 R_2}{C_2 j\omega (R_1 + R_2) + 1}$

$Z_{AB} = (Z_{C_2} + Z_{R_1}) // Z_{R_2} = \left(\frac{1}{C_2 j\omega} + R_1 \right) // R_2 =$
 $= \left(\frac{C_2 j\omega}{1 + R_1 C_2 j\omega} + \frac{1}{R_2} \right)^{-1} = \frac{R_2 (1 + R_1 C_2 j\omega)}{1 + R_1 C_2 j\omega + R_2 C_2 j\omega}$

$Z_{AB} = \frac{R_2 + R_1 R_2 C_2 j\omega}{1 + (R_1 + R_2) j\omega C_2}$

5.3) a)

$Z_T = (Z_{C_2} + Z_{L_2}) // Z_{L_1} + Z_{C_1} = \left(L_2 j\omega + \frac{1}{C_2 j\omega} \right) // L_1 j\omega + \frac{1}{C_1 j\omega} = \left(\frac{C_2 j\omega}{1 - L_2 C_2 \omega^2} + \frac{1}{L_1 j\omega} \right)^{-1} + \frac{1}{C_1 j\omega} =$
 $= j \left(\frac{\omega L_1 (1 - \omega^2 L_2 C_2)}{1 - \omega^2 C_2 (L_1 + L_2)} - \frac{1}{\omega C_1} \right)$

b) $Z_C = (Z_{C_2} + Z_{L_2}) // Z_{C_1} + Z_{L_1} = \left(L_2 j\omega + \frac{1}{C_2 j\omega} \right) // \frac{1}{C_1 j\omega} + L_1 j\omega = \left(\frac{C_2 j\omega}{1 - L_2 C_2 \omega^2} + C_1 j\omega \right)^{-1} + L_1 j\omega =$
 $= j \left(\omega L_1 - \frac{1 - L_2 C_2 \omega^2}{1 + \frac{C_2}{C_1} - \omega^2 C_2 L_2} \cdot \frac{1}{\omega C_1} \right)$

5.4) a) $I_S = 5 e^{j\frac{\pi}{4}} \text{ A}$

b) $V_C(j\omega) = \frac{1}{C\omega j} \cdot \frac{j\omega L \cdot i_G}{j\omega L + R + \frac{1}{j\omega C}} \rightarrow$ Divisor de corrente!

$F(j\omega) = \frac{j\omega L}{C\omega j (j\omega L + R + \frac{1}{j\omega C})} = \frac{j\omega L}{1 - \omega^2 CL + j\omega CR} \Omega$

c) $V_C(j\omega) = \frac{j\omega L}{1 - \omega^2 CL + j\omega CR} \cdot i_G = \frac{1}{2} \cdot i_G \Rightarrow V_C(t) = 2,5 \cos(1000t + \frac{\pi}{4})$
 $\bar{V}_C = 2,5 e^{j\frac{\pi}{4}}$

$R = 200 \Omega$
 $C = 100 \text{ nF}$ Calculadora
 $L = 10 \text{ mH}$
 $\omega = 1000$

$$5.5) i(t) = 0.8 \sin(20t) = 0.8 \cos(20t - \frac{\pi}{2}) = 0.8 e^{-\frac{\pi}{2}j}$$

$$v_s(t) = 50 \cos(20t - 53^\circ \cdot \frac{\pi}{180^\circ}) = 50 e^{-53^\circ j}$$

Pela malha:

$$Ri + j\omega Li + v_s - v_{im} = 0 \Leftrightarrow 100 \cdot 0.8 e^{-\frac{\pi}{2}j} + j \cdot 20 \cdot 10 \cdot e^{-\frac{\pi}{2}j} + 50 e^{-53^\circ j} = v_{im}$$

calculadora:

$$v_{im} = 244.76 e^{-0.562844j} = 244.76 \cos(20t - 0.562844)$$

\downarrow
 $32.2^\circ \cdot \frac{\pi}{180^\circ}$

5.6) a)

$$R_1 = 4 \Omega$$

$$R_2 = 10 \Omega$$

$$C_1 = 1 \text{ mF}$$


$$C_2 = 0.25 \text{ mF}$$

$$L_1 = 12 \text{ mH}$$

$$(R_2 + \frac{1}{j\omega C_2}) // j\omega L_1 + R_1 + \frac{1}{j\omega C_1} \Rightarrow \text{calculadora} \Rightarrow 8.81 e^{0.561375j}$$

$$\bar{Z}_t = 8.81 e^{32.2^\circ \cdot \frac{\pi}{180^\circ} j} \Omega$$

b) Equações das malhas:

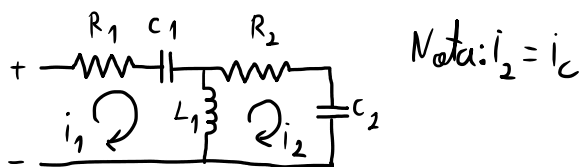

$$\begin{cases} R_1 i_1 + \frac{1}{j\omega C_1} i_1 + j\omega L_1 (i_1 - i_2) - V = 0 & \text{com } i_2 = 2 e^{j\frac{\pi}{6}} \\ j\omega L_1 (i_1 - i_2) + R_2 i_2 + \frac{1}{j\omega C_2} i_2 = 0 \end{cases}$$

$$\hookrightarrow \text{calculadora} \rightarrow V = 29.96 e^{-39.1^\circ \cdot \frac{\pi}{180^\circ} j}$$

$$v(t) = 29.96 \cos(500t - \frac{39.1^\circ}{180^\circ} \pi)$$