
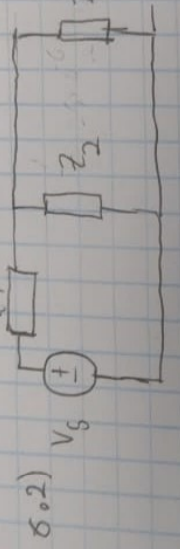


6.1)

$$\frac{V_1}{V_S} = \frac{V_L}{V_S} = \frac{2}{\sqrt{13}} = 0.5547$$

$$\frac{V_2}{V_S} = 0.6202$$

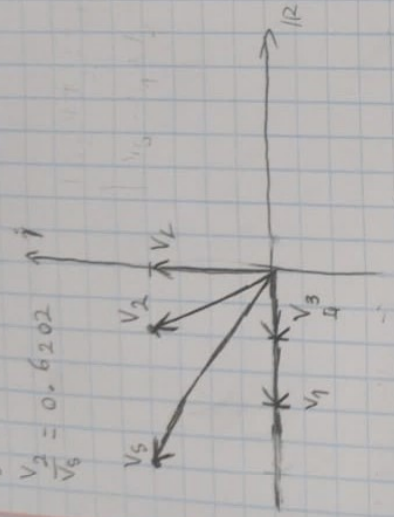

6.2)

$$V_0 = V_S \cdot \frac{Z_2 \parallel Z_3}{Z_1 + Z_2 \parallel Z_3}$$

$$F(\omega) = \left| \frac{V_2 \parallel Z_3}{Z_1 + Z_2 \parallel Z_3} \right| = \left| \frac{j\omega C + \frac{1}{R}}{j\omega L + (j\omega C + \frac{1}{R})} \right| = \frac{1}{\sqrt{(1 - \omega^2 LC)^2 + (\frac{\omega L}{R})^2}}$$

$$L = 2 \times 10^{-3} \text{ H}$$

$$C = 10 \times 10^{-6} \text{ F}$$

$$R = 4 \Omega$$

6.1)

$$I_L = 0$$

$$V_L = I_L \cdot Z_L = 2j$$

$$V_3 = I_L \cdot Z_3 = -1$$

$$V_2 = V_3 + V_L$$

$$V_1 = I_1 + I_2 \Leftrightarrow$$

$$I_1 = j + \frac{V_2}{Z_2} \Leftrightarrow I_1 = -2$$

$$V_1 = Z_1 \cdot I_1 = -2 \cdot 1 = -2$$

$$V_S = V_1 + V_2 = -1 + 2j = \sqrt{5}$$


$$Z_1 = j\omega L$$

$$Z_2 = \frac{1}{j\omega C}$$

$$Z_3 = R$$

$$F(\omega) = \left| \frac{1}{(j\omega C + \frac{1}{R})} \right| = \frac{1}{\sqrt{(1 - \omega^2 LC)^2 + (\frac{\omega L}{R})^2}}$$

6.3) $V_{OC} = V_{xy}$
 $I_{CC} =$

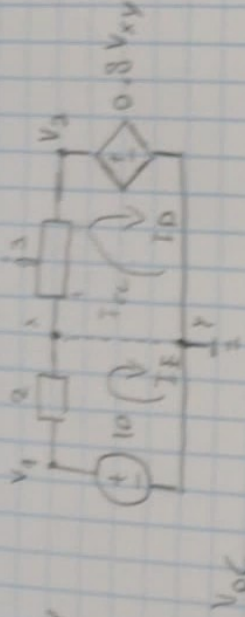

$V_1 = 10$

$V_x:$

$$\frac{V_x - V_1}{2} + \frac{V_x - V_2}{3} = 0$$

$V_2 = 0.8V_x$

$V_3 = 10$

$V_2 = 7.86 + 1.08I$

$V_x = 9.825 + 1.310I$


$I_{CC} = I_E'$

$I_E = I_{CC} = 5$

$-10 + 2 \cdot I_E = 0$

$0.93(I_D) = 0$

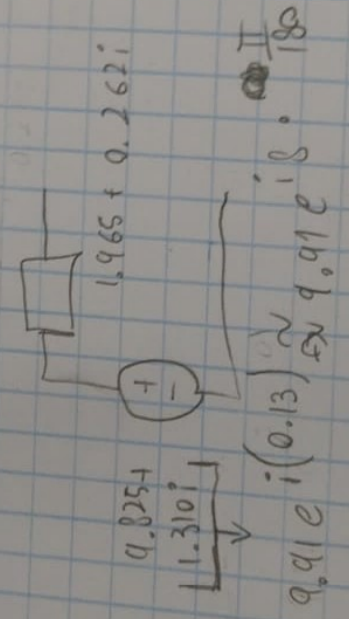$Z_{Th} = \frac{V_{OC}}{I_{CC}} = \frac{9.825 + 1.310I}{5} = 1.965 + 0.262I$



6.4)

a) $V_2 = 0$

$V_+ = V_-$

$V_- : \frac{V_+}{R_3} + \frac{V_- - V_0}{R_4} \Leftrightarrow \frac{V_+}{R_3} + \frac{V_+}{R_4} = V_0$

$V_+ : \frac{V_+}{R_2} + \frac{V_+ - V_1}{R_1} = 0 \Leftrightarrow V_+ \left(\frac{1}{R_2} + \frac{1}{R_1} \right) = \frac{V_1}{R_1} \Leftrightarrow \left(\frac{R_1 \left(\frac{1}{R_2} + \frac{1}{R_1} \right)}{V_1} \right)^{-1} = V_+$

$\frac{V_1 \left(\frac{1}{R_2} + \frac{1}{R_1} \right)}{R_1 \left(\frac{1}{R_2} + \frac{1}{R_1} \right)} = V_+ \rightarrow R_4 \left(V_+ \left(\frac{1}{R_3} + \frac{1}{R_4} \right) \right) = V_0$

$R_4 \left(\frac{V_1 \left(\frac{1}{R_2} + \frac{1}{R_1} \right)}{R_1 \left(\frac{1}{R_2} + \frac{1}{R_1} \right)} \right) = V_0$

$\frac{V_1 R_4 \left(\frac{1}{R_2} + \frac{1}{R_1} \right)}{R_1 \left(\frac{1}{R_2} + \frac{1}{R_1} \right)} = V_0 \Leftrightarrow V_1 \frac{R_3 + R_4}{R_3} \frac{R_2}{R_1 + R_2} = V_0$

b) $V_4 = 0$

$V_- = V_+ = 0$

$\frac{V_- - V_2}{R_3} + \frac{V_- - V_0}{R_4} = 0 \Leftrightarrow V_0 = -\frac{R_4}{R_3} V_2$

c) Dado en una aproximación de Norton Imagenes $V_0 = -\frac{R_4}{R_3} V_2 + V_1 \frac{R_3 + R_4}{R_3} \frac{R_2}{R_1 + R_2}$

d) $\frac{R_4}{R_3} = 2$ $\Leftrightarrow \frac{R_2}{R_1 + R_2} = \frac{2}{3} \Leftrightarrow R_2 = 2R_1$
 $\frac{R_3 + R_4}{R_3} \cdot \frac{R_2}{R_1 + R_2} = 2$ $\Leftrightarrow \frac{R_4}{R_3} = 2R_3$
 $\frac{R_2}{R_1 + R_2} = \frac{2}{3} \Leftrightarrow R_2 = 2R_1$

6.6)

$$V_1 = V$$

$$V = \frac{V_1 - V_0}{R_1} + \frac{V_0 - V_0}{R_2} = 0 \Leftrightarrow V = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V_0 = \frac{V_0}{R_1} + \frac{V_0}{R_2} \Leftrightarrow V = \left(\frac{R_2 + R_1}{R_1 R_2} \right) \left(\frac{R_1 R_2}{R_1 + R_2} \right)$$

$$V_0 = \frac{V_1}{R_1} + \frac{V_0 - V_0}{R_2} = -I_L \Leftrightarrow$$

$$\Leftrightarrow I_L = \frac{V_0}{R_1} - V_0 \left(\frac{1}{R_2} + \frac{1}{R_4} \right)$$

$$I_L = \frac{V_0}{R_1} - \left(\frac{V_0}{R_2} + \frac{V_0}{R_4} \right) = \left(\frac{R_2 + R_4}{R_1 R_2 R_4} \right) \left(\frac{R_1 R_2 R_4}{R_2 + R_4} \right)$$

$$V_0 \left(\frac{1}{R_1} - \frac{1}{R_2} - \frac{1}{R_4} \right) \left(\frac{R_2 R_4}{R_2 + R_4} \right) =$$

$$\frac{1}{R_1} - \frac{1}{R_2} - \frac{1}{R_4} = \frac{R_2 R_4 + R_1 R_4 - R_1 R_2 - R_1 R_2}{R_1 R_2 R_4} = \frac{R_2 R_4 - R_1 R_2}{R_1 R_2 R_4}$$

$$\left(\frac{1}{R_1} - \frac{R_2 (R_1 + R_2)}{R_1 R_2 (R_1 + R_2)} \right)$$

$$V_0 = 0$$

$$I_L = -\frac{V_0}{R_1} \left(\frac{R_2 + R_4}{R_1 R_2} \right) = -\frac{V_0}{R_1 R_2} \left(\frac{R_2 + R_4}{R_1} \right)$$

$$I_L = -\frac{V_0}{R_1} //$$

$$\frac{R_1 R_2}{R_2 R_3 + R_2 R_4} = -V_0 = \frac{R_1 (R_1 R_2)}{R_1 (R_1 R_2) R_2}$$

$$\frac{R_2}{R_1} = \frac{R_1 R_2}{R_2 R_3 + R_2 R_4}$$

$$R_2 R_3 = R_1 R_4$$