

a)

$$\bar{I}_L = j$$

$$\bar{V}_L = \bar{I}_L \cdot \bar{Z}_L = 2j \text{ V}$$

$$\bar{V}_3 = \bar{I}_L \cdot \bar{Z}_3 = -1 \text{ V}$$


$$\bar{V}_2 = \bar{V}_3 + \bar{V}_L$$

$$\bar{V}_2 = -1 + 2j \text{ V}$$

$$\bar{I}_1 = \bar{I}_L + \bar{I}_2 \Leftrightarrow \bar{I}_1 = j + \frac{\bar{V}_2}{\bar{Z}_2} = -2 \text{ A}$$

$$\bar{V}_1 = \bar{Z}_1 \cdot \bar{I}_1 = -2 \text{ V}$$
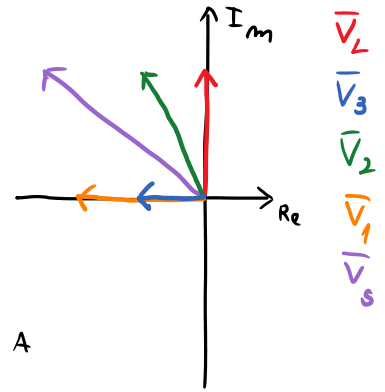
$$\bar{V}_s = \bar{V}_1 + \bar{V}_2 = -3 + 2j \text{ V}$$



b)

$$|\bar{V}_L| = 2 \quad |\bar{V}_2| = \sqrt{5}$$

$$|\bar{V}_3| = 1 \quad |\bar{V}_1| = 2 \quad |\bar{V}_s| = \sqrt{13}$$

i)

$$\frac{|\bar{V}_1|}{|\bar{V}_s|} = \frac{2}{\sqrt{13}} \approx 0.55$$

ii)

$$\frac{|\bar{V}_2|}{|\bar{V}_s|} = \frac{\sqrt{5}}{\sqrt{13}} \approx 0.62$$

iii)

$$\frac{|\bar{V}_L|}{|\bar{V}_s|} = \frac{2}{\sqrt{13}} \approx 0.55$$

calculadora

c)

$$V_2 = \frac{(2+j) // (-j)}{(2+j) // (-j) + 1} \cdot v_s \quad I_L = \frac{V_2}{2+j} \rightarrow I_L = 277,35 \cos(10t - 56.3047^\circ \cdot \frac{\pi}{180}) \text{ mA}$$

6.2) $v_s(t) = 20 \cos(10t + \frac{\pi}{5}) \text{ V} = 20 e^{j\frac{\pi}{5}}$

a)

$$v_s = 1 \cdot \bar{I}_E - j(\bar{I}_E - \bar{I}_0)$$

$$0 = j \cdot \bar{I}_0 + 2 \cdot \bar{I}_0 + j(\bar{I}_E - \bar{I}_0)$$

$$\Rightarrow \begin{bmatrix} 1-j & j \\ j & 2 \end{bmatrix} \cdot \begin{bmatrix} \bar{I}_E \\ \bar{I}_0 \end{bmatrix} = \begin{bmatrix} 20 e^{j\frac{\pi}{5}} \\ 0 \end{bmatrix} \Rightarrow \begin{cases} \bar{I}_E = 11.1 e^{j67.7^\circ} \text{ A} \\ \bar{I}_0 = 5.5 e^{-j20.3^\circ} \text{ A} \end{cases}$$

b)

$$\bar{V}_a = v_s$$

$$\bar{V}_a - \bar{V}_b - j\bar{V}_c = 0$$

$$-j\bar{V}_b - \frac{\bar{V}_c}{2} + j\bar{V}_c = 0$$

$$\Rightarrow \begin{bmatrix} 1 & 0 & 0 \\ 1 & -1 & -j \\ 0 & -j & -\frac{1}{2} + j \end{bmatrix} \cdot \begin{bmatrix} \bar{V}_a \\ \bar{V}_b \\ \bar{V}_c \end{bmatrix} = \begin{bmatrix} 20 e^{j\frac{\pi}{5}} \\ 0 \\ 0 \end{bmatrix} \Rightarrow \begin{cases} \bar{V}_a = 20 e^{j\frac{\pi}{5}} \text{ V} \\ \bar{V}_b = 12.4 e^{j6.3^\circ} \text{ V} \\ \bar{V}_c = 11.1 e^{-j20.3^\circ} \text{ V} \end{cases}$$

c)

$$\bar{I}_L = \bar{I}_0 = 5.5 e^{-j20.3^\circ} \text{ A}$$

$$\bar{V}_2 = \bar{V}_b = 12.4 e^{j6.3^\circ} \text{ V}$$


$$\bar{V}_1 = \bar{I}_E \cdot 1 = 11.1 e^{j67.7^\circ} \text{ V}$$

d)

$$i_L(t) = 5.5 \cos(10t - 20.3^\circ) \text{ A}$$

$$v_1(t) = 11.1 \cos(10t + 67.7^\circ) \text{ V}$$
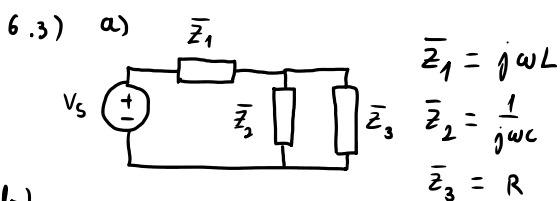
$$v_2(t) = 12.4 \cos(10t + 6.3^\circ) \text{ V}$$



$$\bar{Z}_1 = j\omega L$$

$$\bar{Z}_2 = \frac{1}{j\omega C}$$



$$\bar{Z}_3 = R$$

$$V_0 = v_s \cdot \frac{\bar{Z}_2 // \bar{Z}_3}{\bar{Z}_1 + \bar{Z}_2 // \bar{Z}_3}$$

$$F(\omega) = \left| \frac{\bar{Z}_2 // \bar{Z}_3}{\bar{Z}_1 + \bar{Z}_2 // \bar{Z}_3} \right| = \left| \frac{(j\omega C + \frac{1}{R})^{-1}}{j\omega L + (j\omega C + \frac{1}{R})^{-1}} \right| = \left| \frac{1}{(j\omega C + \frac{1}{R})j\omega L + 1} \right| =$$

Wolfram

$$= \left| \frac{1}{1 - \omega^2 LC + \frac{j\omega L}{R}} \right| = \frac{1}{\sqrt{(1 - \omega^2 LC)^2 + \left(\frac{\omega L}{R}\right)^2}}$$

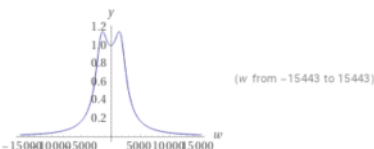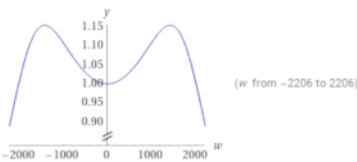


6.4) $V_S = j\omega L \cdot \bar{I}_E + \frac{1}{j\omega C} \cdot (\bar{I}_E - \bar{I}_D)$
 a) $0 = -\frac{1}{j\omega C} (\bar{I}_E - \bar{I}_D) + R \bar{I}_D \Rightarrow \begin{bmatrix} (\omega L - \frac{1}{\omega C})j & \frac{1}{\omega C} j \\ \frac{1}{\omega C} j & R - \frac{1}{\omega C} j \end{bmatrix} \begin{bmatrix} \bar{I}_E \\ \bar{I}_D \end{bmatrix} = \begin{bmatrix} 6e^{j\frac{\pi}{4}} \\ 0 \end{bmatrix}$

$\bar{I}_E = 1.515 e^{j44.9^\circ} \text{ A}$
 $\bar{I}_D = 1.507 e^{j39.2^\circ} \text{ A}$
 $\bar{V}_0 = R \bar{I}_D = 6.028 e^{j39.2^\circ} \text{ V}$

$V_S = 6 e^{j\frac{\pi}{4}}$
 $\omega = 200$

b) $\frac{\bar{V}_S - \bar{V}_0}{\bar{Z}_L} = \frac{\bar{V}_0}{\bar{Z}_C} + \frac{\bar{V}_0}{\bar{Z}_R} \Leftrightarrow \frac{\bar{V}_S}{\bar{Z}_L} \cdot \left(\frac{1}{\bar{Z}_L} + \frac{1}{\bar{Z}_C} + \frac{1}{\bar{Z}_R}\right)^{-1} = \bar{V}_0 = 6.03 e^{j39.2^\circ} \text{ V}$


c) $v_0(t) = 6.03 \cos(200t + 39.2^\circ) \text{ V}$

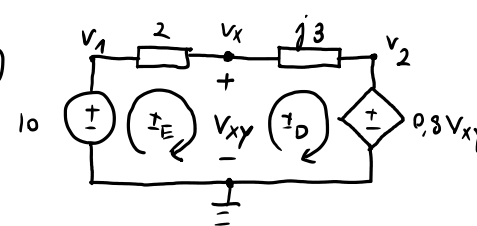6.5) 

$V_{oc} : \begin{cases} v_1 = 10 \\ \frac{v_x - v_1}{2} + \frac{v_x - v_2}{3j} = 0 \\ v_2 = 0.8v_x \end{cases} \Rightarrow \begin{cases} v_1 = 10 \\ v_2 = 7.86 + 1.08j \\ v_x = 9.825 + 1.31j \end{cases}$

$Z_{th} = \frac{V_{oc}}{I_{cc}} = \frac{9.825 + 1.31j}{5} = 1.965 + 0.262j \Omega$

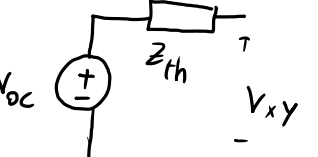$I_{cc} : \begin{cases} I_D = 2I_E \\ j3I_D = 0 \end{cases} \Rightarrow \begin{cases} I_E = 5 \text{ A} \\ I_D = 0 \end{cases} \quad I_{cc} = I_E - I_D = 5 \text{ A}$



$Z_{th} = 1.965 + 0.262j \Omega$
 $V_{oc} = 9.825 + 1.31j \text{ V} = 9.91 e^{j7.6^\circ} \text{ V}$

6.6) a) $V_{xy}(t) = 9.91 \cos(100\pi t + 7.6^\circ) \text{ V}$

b) $j3 = j\omega L \Leftrightarrow L = \frac{3}{100\pi} = 9.55 \text{ mH}$

c) $\bar{V}_L = \bar{V}_x - \bar{V}_2 = 1.965 + 0.23j = 1.98 e^{j7.6^\circ} \rightarrow 1.98 \cos(100\pi t + 7.6^\circ) \text{ V}$

$\bar{I}_L = \frac{\bar{V}_L}{j3} = 0.66 e^{-j82.4^\circ} \rightarrow 0.66 \cos(100\pi t - 82.4^\circ) \text{ A}$

d) $p_L(t) = 0.6534 \cos(200\pi t - 74.8^\circ) \text{ W}$

e) i) $S_L = \frac{\bar{V}_L \cdot \bar{I}_L^*}{2} = 0.6534 e^{j\frac{\pi}{2}} \text{ VA} \rightarrow 0 + j0.6534 \text{ [W | VAR]}$

$P_L = R_e \{ S_L \} = 0 \text{ W} \quad Q_L = I_m \{ S_L \} = 0.6534 \text{ VAR}$

ii) $S_R = \frac{\bar{V}_R \cdot \bar{I}_R^*}{2} = \frac{(\bar{V}_1 - \bar{V}_x) \cdot \left[\frac{(\bar{V}_1 - \bar{V}_x)}{2}\right]^*}{2} = 436.7 e^{j0} \text{ mVA} \rightarrow 436.7 + j0 \text{ [mW | VAR]}$

$P_R = R_e \{ S_R \} = 436.7 \text{ mW} \quad Q_R = I_m \{ S_R \} = 0 \text{ VAR}$

Gerador independente:

$$S_I = \frac{\bar{V}_I \cdot \bar{I}_I^*}{2} = \frac{\bar{V}_I \cdot (-\bar{I}_R^*)}{2} = -3.304 e^{j82.39^\circ} \text{ VA} \rightarrow -437.5 - j3.275 \text{ [mW | VAR]}$$

$$P_I = \text{Re}\{S_I\} = -437.5 \text{ mW} \quad Q_I = \text{Im}\{S_I\} = -3.275 \text{ VAR}$$

Gerador dependente:

$$S_D = \frac{\bar{V}_D \cdot \bar{I}_D^*}{2} = \frac{0.8 \bar{V}_X \cdot \bar{I}_L^*}{2} = 2.62 e^{j\frac{\pi}{2}} \text{ VA} \rightarrow 0 + j2.62 \text{ [W | VAR]}$$

$$P_D = \text{Re}\{S_D\} = 0 \text{ W} \quad Q_D = \text{Im}\{S_D\} = 2.62 \text{ VAR}$$

S - complexa

|S| - aparente

Q - reativa

P - ativa

$$\text{iii) } \sum P = P_L + P_R + P_I + P_D = 437.5 - 437.5 = 0$$

$$\sum Q = Q_L + Q_R + Q_I + Q_D = 0.6534 + 0 - 3.275 + 2.62 = 0$$

$$6.7) \bar{V}_C = \bar{V}_R = \bar{V}_O = 6.02442 e^{j39.232^\circ} \text{ V}$$

$$\bar{V}_L = \bar{V}_S - \bar{V}_O = 0.606 e^{j134.442^\circ} \text{ V}$$

$$\bar{V}_S = 6 e^{j\frac{\pi}{4}} \text{ V}$$

$$C: S_C = \frac{\bar{V}_C \cdot \bar{I}_C^*}{2} = \frac{\bar{V}_C \cdot \left(\frac{\bar{V}_C}{\bar{Z}_C}\right)^*}{2} = 0.4545 e^{-j\frac{\pi}{2}} \text{ VA} \rightarrow 0 - j0.4545 \text{ [W | VAR]}$$

$$P_C = \text{Re}\{S_C\} = 0 \quad Q_C = \text{Im}\{S_C\} = -0.4545 \text{ VAR} \quad |S| = 0.4545 \text{ VA}$$

$$R: S_R = \frac{\bar{V}_R \cdot \bar{I}_R^*}{2} = \frac{\bar{V}_R \cdot \left(\frac{\bar{V}_R}{\bar{Z}_R}\right)^*}{2} = 4.545 e^{j0} \text{ VA} \rightarrow 4.545 + j0 \text{ [W | VAR]}$$

$$P_R = \text{Re}\{S_R\} = 4.545 \text{ W} \quad Q_R = \text{Im}\{S_R\} = 0 \text{ VAR} \quad |S| = 4.545 \text{ VA}$$

$$L: S_L = \frac{\bar{V}_L \cdot \bar{I}_L^*}{2} = \frac{\bar{V}_L \cdot \left(\frac{\bar{V}_L}{\bar{Z}_L}\right)^*}{2} = 0.459 e^{j\frac{\pi}{2}} \text{ VA} \rightarrow 0 + j0.459 \text{ [W | VAR]}$$

$$P_L = \text{Re}\{S_L\} = 0 \text{ W} \quad Q_L = \text{Im}\{S_L\} = 0.459 \text{ VAR} \quad |S| = 0.459 \text{ VA}$$

$$V_S: S_V = \frac{\bar{V}_V \cdot \bar{I}_V^*}{2} = \frac{\bar{V}_V \cdot (-\bar{I}_L^*)}{2} = -4.545 e^{j0.0576^\circ} \text{ VA} \rightarrow -4.545 - j4.6 \text{ [W | mVAR]}$$

$$P_V = \text{Re}\{S_V\} = -4.545 \text{ W} \quad Q_V = \text{Im}\{S_V\} = -4.6 \text{ mVAR} \quad |S| = 4.545 \text{ VA}$$

$$\sum P = P_C + P_R + P_L + P_V = 0 + 4.545 + 0 - 4.545 = 0$$

$$\sum Q = Q_C + Q_R + Q_L + Q_V = -0.4545 + 0 + 0.459 - 4.6 \times 10^{-3} = 0$$

$$\sum |S| = |S_C| + |S_R| + |S_L| + |S_V| = 4.545 + 454.5 \times 10^{-3} + 459.1 \times 10^{-3} + 4.545 = 10 \text{ VA}$$