

7.1) $V_+ = V_- = 0$

$$\frac{V_2 - V_-}{R_1} + \frac{V_- - V_2}{R_2} = 0$$


$$\frac{V_2 - V_-}{R_2} + \frac{V_2 - V_0}{R_3} + \frac{V_2}{R_4} = 0$$

$$-\frac{V_1}{R_1} = \frac{V_2}{R_2}$$

$$\frac{V_2}{R_2} + \frac{V_2}{R_3} + \frac{V_2}{R_4} = \frac{V_0}{R_3}$$

$$V_2 = \frac{V_0}{R_3 \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)}$$

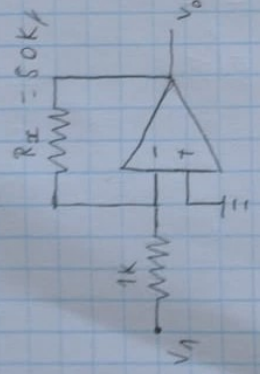
$$V_1 = -\frac{R_1}{R_2} V_2 \rightarrow V_1 = -\frac{R_1}{R_2} \cdot \frac{V_0}{R_3 \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)} \Leftrightarrow \frac{V_0}{V_1} = -\frac{R_2 R_3 \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)}{R_1}$$



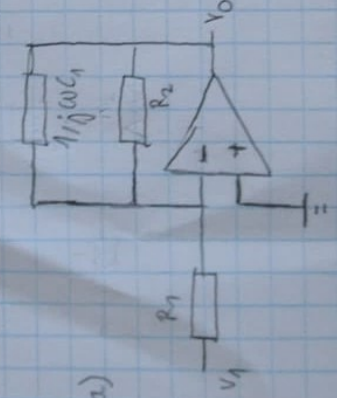7.2) $\frac{V_0}{V_1} = -50$

$R_f = 50k$

$$V_+ = V_- = 0 \quad \frac{V_- - V_1}{1k} + \frac{V_- - V_0}{R_{oc}} = 0 \Leftrightarrow -\frac{R_{oc}}{1k} = \frac{V_0}{V_1} \Leftrightarrow -\frac{R_{oc}}{1k} = -50 \Leftrightarrow R_{oc} = 50k$$




$$V_+ = V_- = V_0$$

$$\frac{V_- - V_1}{R_1} + \frac{V_- - V_0}{Z_T} = 0 \Leftrightarrow -\frac{V_1}{R_1} Z_T = V_0 \Leftrightarrow Z_T = -\frac{R_1 V_0}{V_1}$$

$$Z_T = \frac{1}{j\omega C_1} \parallel R_2 = \left(\frac{1}{j\omega C_1} + \frac{1}{R_2} \right)^{-1} = \frac{R_2}{j\omega C_1 R_2 + 1}$$


Com R_2 tem um ganho limitado a $-\frac{R_2}{R_1}$

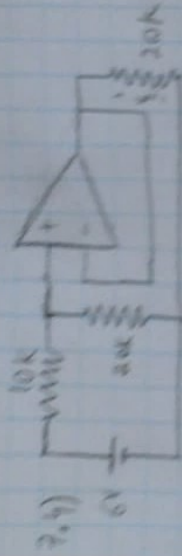1) Sem R_2 $-\frac{V_1}{R_1} = j\omega C_1 V_0 \Leftrightarrow \frac{V_0}{V_1} = -\frac{1}{j\omega C_1 R_1}$



$$V_+ = V_- = V_0 = V_2$$
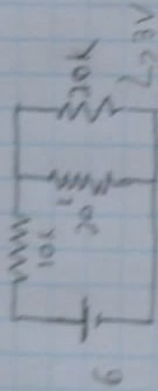
$$V_+ = \frac{6}{10} + \frac{V_0}{20} \Leftrightarrow V_+ = 4V = V_2$$




2.5) $V_2 = 1V$

a)

$$V_3 = 0$$

$$V_4 = V_0 \text{ (out)}$$

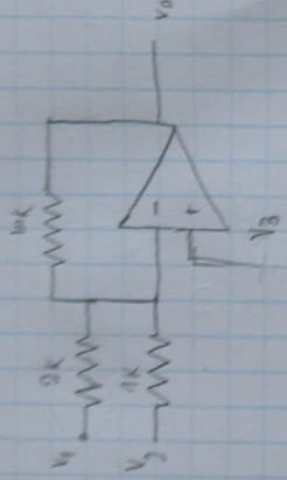

$V_4 = V_- = 0$

$$\frac{V_- - V_3}{1k} + \frac{V_- - V_0}{10k} = 0 \Leftrightarrow -\frac{1}{1k} - \frac{V_0}{10k} = 0 \Leftrightarrow V_0 = -\frac{1}{1k}, 10k \Leftrightarrow V_0 = -10V$$

V_1 :

$$\frac{V_- - V_1}{2k} + \frac{V_- - 10}{10k} = 0 \Leftrightarrow -\frac{V_1}{2k} = \frac{V_0}{10k} \Leftrightarrow V_0 = -5V_1(t)$$

$$V_0 = -10 - 5V_1(t)$$

$$V_1(m) = 1.2 \quad (-16V = V_0)$$

b) $V_3 = V_+ = V_-$

$$\frac{V_1 - V_-}{2k} + \frac{V_2 - V_-}{1k} + \frac{V_0 - V_-}{10k} = 0 \Leftrightarrow -\frac{V_3}{2k} + \frac{V_3}{1k} + \frac{V_0}{10k} - \frac{V_3}{10k} = 0 \Leftrightarrow V_0 = 16V_3$$

$$V_0(t) = \begin{cases} -16V & V_3 \leq -1V \\ 16V_3(t) & -1V \leq V_3(t) \leq 1V \\ 16V & 1V \leq V_3(t) \end{cases}$$