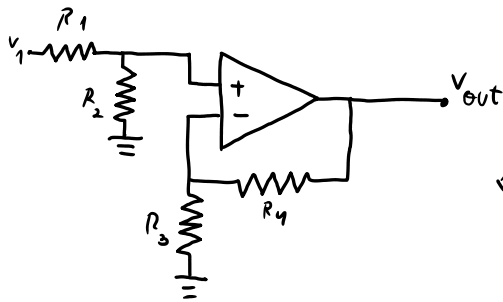



7.1) a)  $V_2 = 0$



$$V_- = V_+ \quad i_- = i_+ = 0 \quad V_+ = V_1 \cdot \frac{R_2}{R_1 + R_2}$$

$$\frac{V_-}{R_3} = \frac{V_0 - V_-}{R_4} \Leftrightarrow \frac{V_-}{R_3} + \frac{V_-}{R_4} = \frac{V_0}{R_4} \Leftrightarrow$$
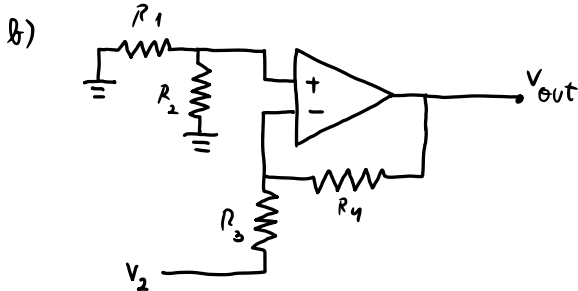
$$\Leftrightarrow V_1 \cdot \frac{R_2}{R_1 + R_2} \cdot \left( \frac{1}{R_3} + \frac{1}{R_4} \right) \cdot R_4 = V_0 \Leftrightarrow V_0 = \left( 1 + \frac{R_4}{R_3} \right) \cdot \frac{R_2}{R_1 + R_2} \cdot V_1$$



$$i_- = i_+ = 0 \quad V_- = V_+ = 0$$

$$\frac{V_- - V_2}{R_3} = \frac{V_0 - V_-}{R_4} \Leftrightarrow -\frac{V_2}{R_3} = \frac{V_0}{R_4} \Leftrightarrow V_0 = -\frac{R_4}{R_3} V_2$$

c)  $V_0 = V_0 V_1 + V_0 V_2 = \left( 1 + \frac{R_4}{R_3} \right) \cdot \frac{R_2}{R_1 + R_2} \cdot V_1 - \frac{R_4}{R_3} V_2$


d)  $-\frac{R_4}{R_3} = -2 \Leftrightarrow R_4 = 2R_3$

$$(1+2) \cdot \frac{R_2}{R_1 + R_2} = 2 \Leftrightarrow R_2 = 2R_1$$

Logo f. exm/lo  $R_4 = 2R_3 = R_2 = 2R_1 = 10k\Omega$

7.2)  $\frac{V_0}{V_1} = -50$

$$R_i = 1k\Omega$$

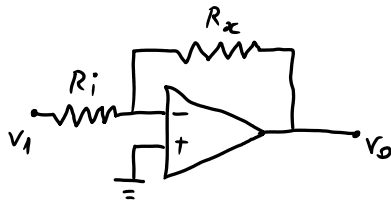


$$\frac{V_- - V_1}{R_i} + \frac{V_- - V_0}{R_x} = 0 \Leftrightarrow -\frac{R_x}{1k} = \frac{V_0}{V_1} \Leftrightarrow R_x = 50k\Omega!$$

Logo  $R_x = 50k\Omega$  e  $R_1 = 1k\Omega$

7.3) Montagem: regulador de tensão


Logo  $V_2 = \frac{20k}{10k + 20k} \cdot 6 = 4V$  ou  $\frac{V_+ - 6}{10k} + \frac{V_-}{20k} = 0$ ;  $V_+ = V_- = V_2 \Leftrightarrow V_2 - 6 = -\frac{1}{2} V_2 \Leftrightarrow \frac{3}{2} V_2 = 6 \Leftrightarrow V_2 = 4V$

sem regulador

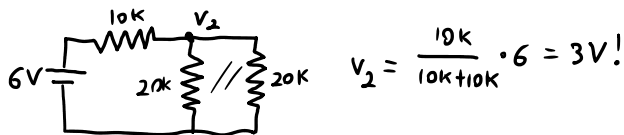

$$V_2 = \frac{10k}{10k + 10k} \cdot 6 = 3V!$$

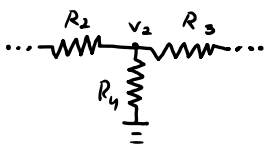7.4)  $V_+ = V_- = 0$   
 $i_+ = i_- = 0$



$$\left. \begin{aligned} \frac{V_- - V_1}{R_1} + \frac{V_- - V_2}{R_2} &= \\ \frac{V_2 - V_-}{R_3} + \frac{V_2 - V_0}{R_4} + \frac{V_2}{R_4} &= 0 \end{aligned} \right\} \Leftrightarrow \left\{ \begin{aligned} V_1 &= -\frac{R_1}{R_2} \cdot V_2 \\ V_2 &= \frac{V_0}{R_3 \left( \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)} \end{aligned} \right.$$

Logo  $\frac{V_0}{V_1} = -\frac{R_2 R_3 \left( \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)}{R_1}$

7.5) a)  $V_2 = 1V$

$V_3 = 0V$

$V_1 = V_{1m} \cos(\omega t)$

Por superposição  $V_2: V_1 = 0 = V_-, V_2 = 1V$

$\frac{V_- - V_2}{1k} + \frac{V_- - V_4}{10k} = 0 \Leftrightarrow V_4 = -10V$

$V_1: V_2 = 0 = V_-, V_1 = V_{1m} \cos(\omega t)$

$\frac{V_- - V_1}{2k} + \frac{V_- - V_0}{10k} = 0 \Leftrightarrow V_0 = -5V_1(t)$

$V_0 = V_{0V_2} + V_{0V_1} = -10 - 5V_1(t)$

$-16 = -10 - 5V_{1m} \Leftrightarrow \frac{6}{5} = V_{1m} = 1.2V$

$16 = -10 - 5V_{1m} \Leftrightarrow -\frac{26}{5} = V_{1m} = -5.2V$

Logo  $V_{1m \text{ Max}} = 1.2V$

b)  $V_1 = V_2 = 0$

$V_3 = V_- = V_+$

$\frac{V_3}{2k} + \frac{V_3}{1k} + \frac{V_3 - V_4}{10k} = 0 \Leftrightarrow V_0 = 16V_3$

Logo  $V_0(t) = \begin{cases} -16 V, & V_3 \leq -1V \\ 16 V_3 & -1V < V_3 < 1V \\ 16 V, & 1V \leq V_3 \end{cases}$

7.6)  $V_- = V_+$

$i_- = i_+$

$\frac{V_- - V_5}{R_1} + \frac{V_- - V_0}{R_2} = 0$

$\frac{V_+ - 0}{R_3} + \frac{V_+ - 0}{Z_f} + \frac{V_+ - V_0}{R_4} = 0$

$\Leftrightarrow V_+ \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \cdot R_2 - \frac{R_2}{R_1} V_5 = V_0$

$\Leftrightarrow \left( \frac{V_+}{R_3} + i_L + \frac{V_+}{R_4} \right) \cdot R_4 = V_0$

$\Leftrightarrow V_+ \left( \frac{R_2}{R_1} + 1 \right) - \frac{R_2}{R_1} V_5 = \frac{R_4}{R_3} V_+ + i_L R_4 + V_0 \Leftrightarrow$

$\Leftrightarrow i_L = -\frac{R_2}{R_1 \cdot R_4} V_5 = -\frac{V_5}{R_3}$

7.7) a)  $V_- = V_+ = 0$

$Z_f = \frac{1}{j\omega C} \parallel R_2 = \frac{R_2}{j\omega C R_2 + 1}$

$\frac{V_- - V_1}{R_1} + \frac{V_- - V_0}{Z_f} = 0 \Leftrightarrow \frac{V_0}{V_1} = -\frac{Z_f}{R_1} = -\frac{R_2}{R_1} \cdot \frac{1}{j\omega C R_2 + 1}$

b) Sem  $R_2: -\frac{V_1}{R_1} = j\omega C V_0 \Leftrightarrow \frac{V_0}{V_1} = -\frac{1}{j\omega C R_1} \Rightarrow$  Com  $R_2$  temos o ganho limitado a  $-\frac{R_2}{R_1}$