

Parte II

a) $\pi \approx 0 \Rightarrow$ linha sem perdas

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} \quad A = D = \cos(\beta d) = 0.9498 \, \Omega$$

$$B = j \cdot Z_0 \cdot \sin(\beta d) = j 88.03 \, \Omega$$

$$C = j \frac{1}{Z_0} \sin(\beta d) = j 1.11 \text{ mS}$$

$$d = 300 \text{ km}$$

$$\beta = \omega \sqrt{LC} = 1.06 \times 10^{-3}$$

$$Z_0 = \sqrt{\frac{L}{C}} = 281.366$$

$$b) \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} \Leftrightarrow \begin{bmatrix} V_m \\ I_2 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_3 \\ 0 \end{bmatrix}$$

\Downarrow

$$V_m = A V_3 \Rightarrow V_3 = 231.6 \text{ kV (compensação)}$$

$$I_2 = C V_3$$

$$V : V_3 \propto A^{-1} V_2$$

$$V : I_2 \propto C V_3$$


$$F : G_0 \left(\frac{d}{2} \cdot \beta \right) \cdot V_m = \frac{V d}{2}$$

$$c) V_{2T} = 220 \text{ kV}$$

$$I_{2T} = 148.59 \text{ A}$$

$$P_{CC} = R_t I_m^2 \Leftrightarrow R_t = \frac{P_{CC}}{I_m^2} = 5 \times 10^{-3} \, \mu\Omega$$
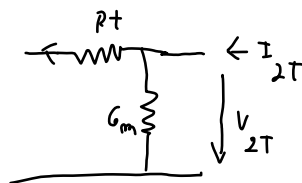
$$P_0 = G_m V_m^2 \Leftrightarrow G_m = \frac{P_0}{V_m^2} = 2 \times 10^{-3} \, \mu\text{S}$$



$$P_{fe} = G_m \cdot V_{2T}^2 = 2 \times 10^{-3} \cdot 1^2 = 200 \text{ kW}$$


$$I_f = G_m V_{2T} = 2 \times 10^{-3} \, \mu\text{A}$$

$$I_{cm} = I_{2T} - I_f = 0.2811 \, \mu\text{A}$$

$$P_{cm} = R_t \cdot I_{cm}^2 = 5 \times 10^{-3} \cdot (0.2811)^2 = 74.017 \text{ kW}$$

$$I_{cm} = I_{1T} = \frac{0.2811 \cdot \frac{S_b}{\sqrt{3} \cdot 10^3}}{\sqrt{3} \cdot 10^3} = 3.245 \text{ kA}$$

d)

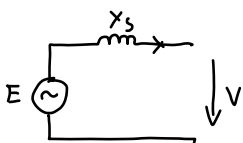

$$E = V + j X_s I$$

$$\rightarrow E = 1 + j \cdot 1.2 \cdot 0.2811 \Rightarrow |E| = 1.055$$

$$V = V_{1T} \quad X_s = 1.2 \, \mu\Omega$$

$$I = I_{1T}$$