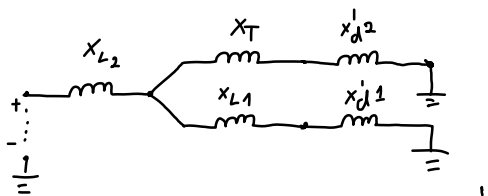


a)



$$x_{th} = x_{L2} + \left[(x_T + x_{d'2}) // (x_{L1} + x_{d'1}) \right]$$

$$x_{L2} = x_{L1} = \frac{0,4 \cdot 100}{\left(\frac{150 \text{ kV}}{100 \text{ M}} \right)^2}$$

$$x_T = 0,07$$

$$x_{th} \approx 0,3147 \quad \frac{1}{x_{th}} = 3,1776 \quad P_{cc} = 3,1776 \cdot 100 \times 10^6 = 317,76 \text{ MVA}$$

$$x_{d'1} = 1 \rightarrow 1 \cdot \frac{100}{1000} = 0,1$$

$$x_{d'2} = 0,2$$

$$I_{cc2} = \frac{x_{L1} + x_{d'1}}{x_{L1} + x_{d'1} + x_T + x_{d'2}} \cdot \frac{1}{x_{th}} = 1,6114 \mu \rightarrow 620,23 \mu$$

b)

$$[-B] = \begin{bmatrix} \frac{1}{x_L} & -\frac{1}{x_L} & 0 \\ -\frac{1}{x_L} & \frac{2}{x_L} & -\frac{1}{x_L} \\ 0 & -\frac{1}{x_L} & \frac{1}{x_L} \end{bmatrix}$$

$$[P] = [-B]^{-1} [P]$$

$$P_1 = 1,2 \quad \theta_1 = 0$$

$$P_2 = 0,8 \quad \theta_2 = -0,21(3) = -12,2^\circ$$

$$P_3 = -2 \quad \theta_3 = -0,56(8) = -32,5956^\circ$$

$$P_{12} = \frac{\theta_1 - \theta_2}{x_L} = 120 \text{ MW}$$


$$P_{23} = \frac{\theta_2 - \theta_3}{x_L} = 200 \text{ MW}$$

$\theta_3 > 30^\circ$, logo a aproximação não é particularmente boa

$$c) P_{max} \approx \frac{V^2}{2x_L} = \frac{1}{2x_L} = 2,813 \mu \rightarrow 281,3 \text{ MW}$$

$$a) S = 3V I^* \Leftrightarrow I = \frac{S^*}{3V^*} = \frac{(18 - j3) \times 10^6}{3 \cdot \frac{30 \times 10^3}{\sqrt{3}}} = 351,19 e^{-j0,165149} \text{ A}$$
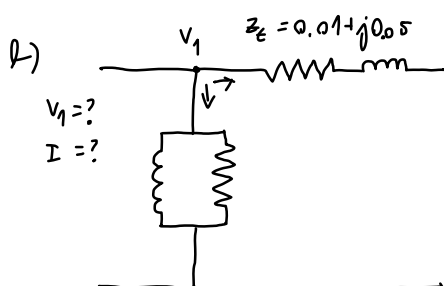
$$Z = \frac{V}{I} = 48,65 + j8,11 \Omega$$



$$V_2 = V \rightarrow 1 \mu$$

$$I_2 = I \rightarrow 0,912 \mu$$

$$V_e = \bar{e}_e - I_2$$

$$V_1 = V_2 + V_e$$

$$I_m = V_1 \cdot Y_m$$

$$I_1 = I_m + I_2$$

$$S = I_1^* \cdot V_1$$

$$R_e \{ S \} = 18,21$$

$$I_m \{ S \} = 4,25$$