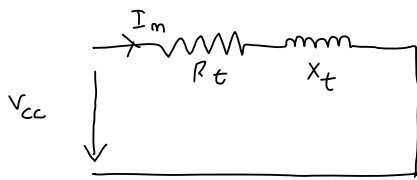


1. Em C.C.



$$|V_{cc}| = \sqrt{R_t^2 + X_t^2} I_m \Rightarrow \text{Em 1.u.} \Rightarrow |V_{cc}| = \sqrt{0,01^2 + 0,04^2} \cdot 1 \Rightarrow$$

$$\Rightarrow |V_{cc}| = 0,041 \text{ 1.u.} \Rightarrow V_{cc} \hat{=} \approx 4\% \text{ de } V_b \text{ que é } V_m.$$


B

$$I_m = I_b$$

$$V_m = V_b$$

$$S_m = S_b$$

2. Em varçor

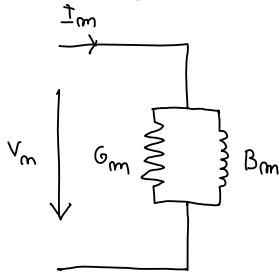

$$P_a = G_m V_m^2 \Rightarrow \text{Em 1.u.} \Rightarrow P_a = G_m = 0,002 \text{ 1.u.}$$

$$\text{Para unidades } P_a = 0,002 \cdot S_b = 40 \text{ kW}$$

A

3. carga = 10 MVA $\Rightarrow S_a = 0.5$

f. p = 1 = cos(φ) $\Rightarrow \phi = 0$ carga puramente resistiva

$$V_2 = V_m = 1 \text{ 1.u.}$$

$$S_a = V_2 \cdot I_2^* \Rightarrow I_2 = \left(\frac{S_a}{V_2} \right)^* = \frac{0.5}{1} \text{ 1.u.} = 0.5 \text{ 1.u.}$$

$$V_1 = (R_t + X_t j) I_2 + V_2 = (0.01 + 0,04 j) 0.5 + 1 = 1.005 + 0.02 j \text{ 1.u.}$$

$$|V_2| = 1 \text{ 1.u.} = 1.30 \text{ kV} = 30 \text{ kV}$$

$$|V_1| = \sqrt{1,005^2 + 0,02^2} = 1,005 \text{ 1.u.} = 1,005 \cdot 60 \text{ kV} = 60.3 \text{ kV}$$

$$q. d. t = |V_1| - |V_2| = 60.3 \text{ kV} - 30 \text{ kV} = 30.3 \text{ kV} !$$