



1. $I_r = 527 \text{ A}$

$P_C = 3 \cdot I_r^2 \cdot (R_r + R_s) \approx 750 \text{ kW}$ A

2. $\delta = 0,04$

$\delta = \frac{\omega_s - \omega_r \cdot PP}{\omega_s} \Leftrightarrow \frac{\omega_s - \delta \omega_s}{PP} = \omega_r \Leftrightarrow \omega_r = 48\pi \Rightarrow \left. \begin{array}{l} f_r = 24 \text{ Hz} \\ N_r = 1440 \text{ rpm} \end{array} \right\}$

$V_m = 10 \text{ kV} \rightarrow V_\delta = \frac{V_m}{\sqrt{3}}$ (Entá em estrela)

$|I_\delta| = \left| \frac{V_\delta}{R_s + \frac{R_r}{\delta} + j(X_s + X_r)} \right| = 510 \text{ A}$

$P_M = 3 \cdot \frac{1-\delta}{\delta} \cdot R_r \cdot I_r^2 \approx 8 \text{ MW}$ C

b) $P_m = 8 \text{ MW}$

$\delta = 0,04$

$P_m = 3 \cdot I_r^2 \cdot \frac{1-\delta}{\delta} R_r \Leftrightarrow \sqrt{\frac{P_m}{3 R_r} \cdot \frac{\delta}{1-\delta}} = I_r \Leftrightarrow I_r = 527 \text{ A}$

$V_s = \sqrt{3} \cdot I_r \cdot \left(\frac{R_r}{\delta} + R_s + j(X_s + X_r) \right) = 10,3 e^{21,8^\circ} \text{ kV}$

$T_m = \frac{P_m}{\omega_r} = 53 \text{ kNm}$

$T = 53 \text{ kNm} \quad V_s = 10,3 \text{ kV}$