

a)

$$S_m = 200 \text{ MVA} \quad d = 300 \text{ km}$$

$$V_m = 220 \text{ KV} \quad Z_0 = 400 \Omega$$

$$f = 50 \text{ Hz} \quad v = 300\,000 \text{ km/s}$$

$$\alpha \approx 0 \rightarrow \text{linha sem perdas}$$

$$\text{fp} = 1$$

$$Z_0 = \sqrt{\frac{L}{C}}$$

$$\beta = \omega \sqrt{LC} \rightarrow \beta = \frac{\omega}{v}$$

$$V = \frac{1}{\sqrt{LC}}$$

$$A = \cos(\beta d) = \cos\left(\frac{\omega}{v} \cdot d\right) = 0.951$$

$$B = j Z_0 \sin(\beta d) = j \cdot 123.6$$

$$C = j \sin(\beta d) \frac{1}{Z_0} = j \cdot 0.177 \cdot 10^{-3}$$

$$\text{Lago} \begin{bmatrix} 0.951 & j 123.6 \\ j \cdot 0.177 \cdot 10^{-3} & 0.951 \end{bmatrix}$$

b) $V_L = \frac{220}{\sqrt{3}} \times 10^3 \text{ V}$

$$I_R = \left(\frac{S}{3 V_L} \right)^* = \frac{200 \times 10^6}{3 \cdot \frac{220}{\sqrt{3}} \times 10^3} = \frac{\sqrt{3} \cdot 200 \times 10^3}{3 \cdot 220} \text{ A}$$

$$\begin{bmatrix} V_e \\ I_e \end{bmatrix} = \begin{bmatrix} 0.951 & j 123.6 \\ j \cdot 0.177 \cdot 10^{-3} & 0.951 \end{bmatrix} \cdot \begin{bmatrix} V_R \\ I_R \end{bmatrix} \Rightarrow \begin{aligned} V_e' &= 137.1 e^{j 28.24^\circ} \text{ KV} \\ I_e &= 508.6 e^{j 11.09^\circ} \text{ A} \end{aligned}$$

Como eles pedem tensão completa: $V_e = \sqrt{3} \cdot V_e' = 237.5 e^{j 28.24^\circ} \text{ KV}$