


I) 1) D

2) B

3) C



4) D

III d)

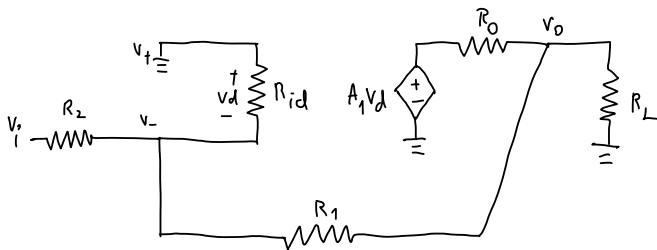

Paralelo - Paralelo

Transimpedancia

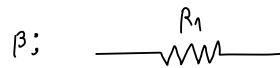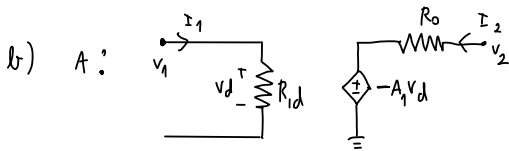

$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{1}{R_{id}}$$

$$y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} = 0$$

$$y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = \frac{A}{R_o}$$

$$y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = \frac{1}{R_o}$$

$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{1}{R_1}$$

$$y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} = -\frac{1}{R_1}$$


$$y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = -\frac{1}{R_1}$$

$$y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = \frac{1}{R_1}$$

$$A = \begin{bmatrix} \frac{1}{R_{id}} & 0 \\ \frac{A}{R_o} & \frac{1}{R_o} \end{bmatrix} = \begin{bmatrix} 2\mu & 0 \\ 100 & 1m \end{bmatrix} S$$

$$\beta = \begin{bmatrix} \frac{1}{R_1} & -\frac{1}{R_1} \\ -\frac{1}{R_1} & \frac{1}{R_1} \end{bmatrix} = \begin{bmatrix} 10\mu & -10\mu \\ -10\mu & 10\mu \end{bmatrix} S$$

c)

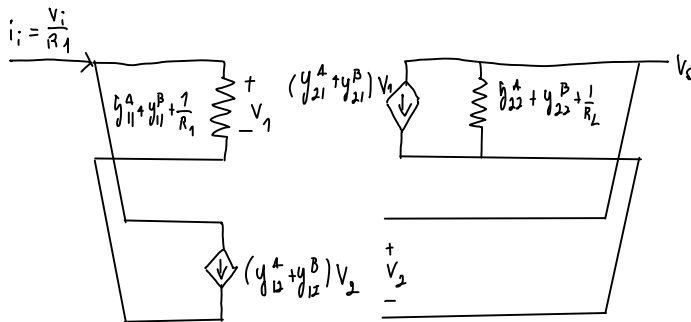

$$A' = -4.095 M\Omega$$

$$\beta' = -10\mu S$$

$$d) A_f = \frac{A}{1+AB} \approx \frac{1}{\beta} = -100 k\Omega$$

$$K_V = \frac{V_o}{v_i} = \frac{V_o}{i_i R_1} = \frac{A_f}{R_1} = -1$$

$$y_i' = y_{11}^A + y_{11}^B + \frac{1}{R_1}$$

$$y_i' = (1+AB) \left( y_{11}^A + y_{11}^B + \frac{1}{R_1} \right)$$

$$y_i = y_i' - \frac{1}{R_1} = 0.9 S$$

$$Z_i = \frac{1}{y_i} = 1.11 \Omega$$


III a) Passa - alto

$$A_p = 0,5 \text{ dB}$$

$$A_s = 19 \text{ dB}$$

$$\omega_p = 2\pi \cdot 4 \text{ kHz}$$

$$\omega_s = 2\pi \cdot 1 \text{ kHz}$$

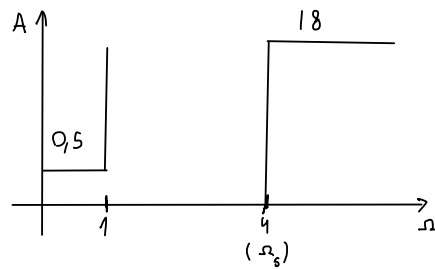

$$\Omega_s = \frac{\omega_p}{\omega_s} = 4$$

$$A(\Omega) = 10 \log(1 + \varepsilon^2 C_m^2(\Omega))$$

$$A(1) = 10 \log(1 + \varepsilon^2) \Leftrightarrow \sqrt{10 \frac{A_p}{10} - 1} = \varepsilon \Leftrightarrow \varepsilon = 0.35$$

$$A(4) = 10 \log(1 + \varepsilon^2 C_m^2(4)) \Leftrightarrow m = 2$$

$$C_2 = 2\Omega^2 - 1$$

$$m = 2 \Rightarrow K = 1.431$$

$$D(s) = s^2 + 1.425s + 1.516$$

$$T(s) = \frac{K}{D(s)} = \frac{1.431}{s^2 + 1.425s + 1.516}$$

$$T(\Omega) = T(s) \Big|_{s = \frac{\omega_p}{\Omega}} = \frac{1.431 \Omega^2}{\omega_p^2 + 1.425\omega_p\Omega + 1.516\Omega^2} = \frac{\frac{1.431}{1.516} \Omega^2}{\frac{\omega_p^2}{1.516} + \frac{1.425\omega_p}{1.516} \Omega + \Omega^2} = \frac{0.943 \Omega^2}{416.66 \times 10^6 + 23.62 \times 10^3 \Omega + \Omega^2}$$

b)  $A(\Omega) = 0$

$$A(\Omega) = 10 \log(1 + \varepsilon^2 C_m^2(\Omega))$$

$$1 + \varepsilon^2 (2\Omega^2 - 1)^2 = 1 \Leftrightarrow 2\Omega^2 - 1 = 0 \Leftrightarrow \Omega^2 = \frac{1}{2}$$

$$\Omega = \frac{\omega_p}{\omega} \Leftrightarrow \omega = \sqrt{2} \omega_p \Rightarrow f = \sqrt{2} \cdot 4 \text{ kHz} \Leftrightarrow f = 5.66 \text{ kHz}$$

c) FIR  $\Rightarrow$  sempre estável

$$Y_n = x_n + 0,2x_{n-1} + 0,4x_{n-2} + 0,2x_{n-3} + x_{n-4}$$

$$\begin{aligned} d) T(e^{j\omega T}) &= 1 + 0,2e^{-j\omega T} + 0,4e^{-j2\omega T} + 0,2e^{-j3\omega T} + e^{-j4\omega T} = \\ &= e^{-j2\omega T} (0,4 + e^{j\omega T} + e^{-j2\omega T} + 0,2e^{-j\omega T} + 0,2e^{j\omega T}) = \\ &= e^{-j2\omega T} (0,4 + 2\cos(2\omega T) + 0,4\cos(\omega T)) \end{aligned}$$


$$\omega = 0$$

$$F_{\text{axe}} = -j2\omega T = 0$$

$$\text{Amplitude} = 0,4 + 2 + 0,4 = 2,8 \Rightarrow G = 8,94 \text{ dB}$$

IV

a)

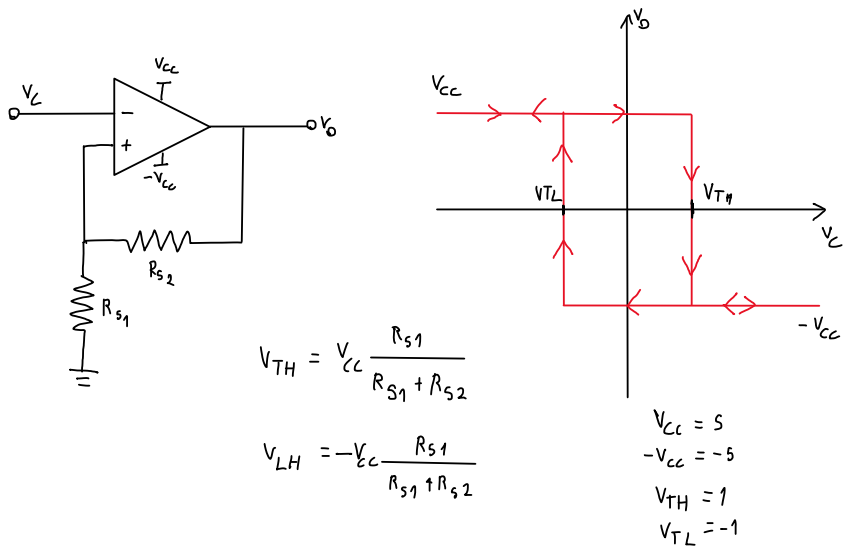

$$V_{TH} = V_{CC} \frac{R_{s1}}{R_{s1} + R_{s2}}$$

$$V_{TL} = -V_{CC} \frac{R_{s1}}{R_{s1} + R_{s2}}$$

$$\begin{aligned} V_{CC} &= 5 \\ -V_{CC} &= -5 \\ V_{TH} &= 1 \\ V_{TL} &= -1 \end{aligned}$$

b)  $R_1 = 15 \text{ k}\Omega$   
 $C_1 = 4,7 \text{ nF}$

$$V_c(t) = V_{cf} - (V_{cf} - V_{ci}) e^{-\frac{t}{\tau}}$$

Carregamento:

$$V_{ci} = -1 \quad V_{cf} = 5 \quad \tau = RC$$

$$V_c(t) = 5 - (5 + 1) e^{-\frac{t}{\tau}}$$

Se chega até 1V

$$1 = 5 - 6 e^{-\frac{t}{\tau}} \Leftrightarrow t = -R_1 C_1 \ln\left(\frac{4}{6}\right) = 28,58 \mu\text{s}$$

Descarregamento:


$$V_{ci} = 1 \quad V_{cf} = -5 \quad \tau = RC$$

$$V_c(t) = -5 - (-5 - 1) e^{-\frac{t}{\tau}}$$

Só chega até -1V

$$-1 = -5 + 6 e^{-\frac{t}{\tau}} \Leftrightarrow t = -R_1 C_1 \ln\left(\frac{4}{6}\right) = 28,58 \mu\text{s}$$
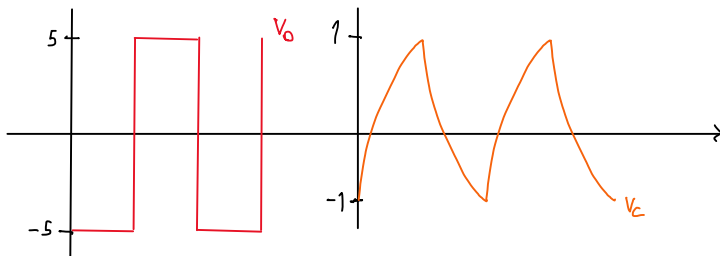
$$T = t_{\text{carrega}} + t_{\text{descarga}} = 57,16 \mu\text{s} \quad f = \frac{1}{T} = 17,495 \text{ KHz} \quad DC = \frac{t_1}{T} = 0,5 \text{ (50\%)}$$



c) Se  $V_{os} = 0,1 \text{ V}$  então  $V_{TH} = 1,1 \text{ V}$  e  $V_{TL} = -0,9 \text{ V}$ , ou seja, já não é simétrico

sendo assim, temos:

$$V_c(t) = V_{cf} - (V_{cf} - V_{ci}) e^{-\frac{t}{\tau}}$$

$$V_{ci} = -0,9$$

$$V_{cf} = 5$$

$$1,1 = 5 - (5 + 0,9) e^{-\frac{t_c}{\tau}} \Leftrightarrow t_c = -RC \ln\left(\frac{1,1 - 5}{-5,9}\right) = 29,19 \mu\text{s}$$

$$-0,9 = -5 - (-5 - 1,1) e^{-\frac{t_D}{\tau}} \Leftrightarrow t_D = -RC \ln\left(\frac{-0,9 + 5}{5 + 1,1}\right) = 28,01 \mu\text{s}$$

$$\Rightarrow f = \frac{1}{t_c + t_D} = 17,48 \text{ KHz} //$$

d)

$$\begin{aligned} B > 2,5 \\ \bar{B} < 2,5 \end{aligned} \Rightarrow \text{Bit} = 1$$

o amplificador vai levar B a 5V e  $\bar{B}$  a 0V //