

I
1.) Não invertida → Seta-Paralela → Z_{oV}

c)

2.) B)

3.) C)

4.) D)

5.) E)

II a) $\omega_{p1} \cdot \omega_{p2} = \omega_0^2$
 $\omega_{s1} \cdot \omega_{s2} = \omega_0^2 \Rightarrow \omega_{p1} \omega_{p2} = \omega_{s1} \omega_{s2}$

$800 \times 1200 = 5500 \times 160 \Leftrightarrow$

$\Leftrightarrow 960 \times 10^3 = 880 \times 10^3$ (Não verifica simetria)

$\omega_{s1} = \frac{\omega_{p1} \omega_{p2}}{\omega_{s2}} = 1097 \text{ rad/s} \Rightarrow 174,6 \text{ Hz}$

$\Omega_s = \frac{\omega_{p1} - \omega_{p2}}{\omega_{p1} + \omega_{p2}} = 13,3$

b) m=1

$A_B(\Omega) = 10 \log(1 + \varepsilon^2 \Omega^2)$ Para m=1 Cheby e Butter não ignora

$A_C(\Omega) = 10 \log(1 + \varepsilon^2 \Omega^2)$

$A(\Omega) = 10 \log(1 + \varepsilon^2 \Omega^{2m})$

$A(1) = 3 \text{ dB} \Rightarrow 3 = 10 \log(1 + \varepsilon^2) \Rightarrow \varepsilon = 1$

$A(13,3) = 18 \text{ dB} \Rightarrow 18 = 10 \log(1 + 13,3^{2m}) \Rightarrow m=1 \rightarrow A(13,3) = 22,5 \text{ dB}$

$m=1 \quad \varepsilon=1 \quad S = \frac{\Omega^2 + \omega_0^2}{B \Omega}$


$H(s) = S + 1 \rightarrow T(\Omega) = \frac{1}{H(s)} \Big|_S = \frac{\Omega^2 + \omega_0^2}{B \Omega} = \frac{B \Omega}{\Omega^2 + \omega_0^2 + B \Omega}$

$B = \omega_{p1} - \omega_{p2} = 400 \cdot 2\pi \text{ rad/s}$

$\omega_0 = \sqrt{\omega_{p1} \omega_{p2}} = 979,79 \cdot 2\pi \text{ rad/s}$

$\Rightarrow \frac{2513 \Omega}{\Omega^2 + 2513 \Omega + 37,9 \times 10^6} //$

c)

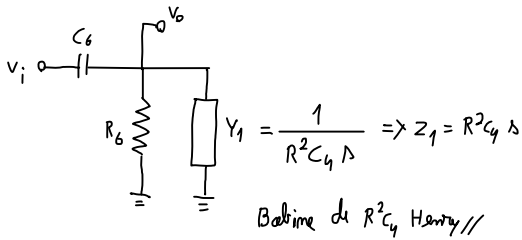

$R = R_1 = R_2 = R_3 = R_5$

$v_o = \frac{R_6 // Z_1}{\frac{1}{sC_6} + R_6 // Z_1} v_i \Rightarrow T(s) = \frac{\left(\frac{1}{R_6} + \frac{1}{R^2 C_4 s}\right)^{-1}}{\frac{1}{sC_6} + \left(\frac{1}{R_6} + \frac{1}{R^2 C_4 s}\right)^{-1}} = \frac{1}{\frac{1}{sC_6 R_6} + \frac{1}{s^2 C_6 C_4 R^2} + 1} = \frac{s^2}{s^2 + \frac{1}{C_6 R_6} s + \frac{1}{C_6 C_4 R^2}}$

$\omega_p^2 = 2,527 \times 10^3 \frac{K \Omega^2}{\Omega^2 + \frac{\omega_p}{Q_p} \Omega + \omega_p^2}$

$Q_p = \sqrt{5}$

$K=1$

$\left. \begin{aligned} \omega_p^2 &= \frac{1}{C_6 C_4 R^2} \Rightarrow C_4 = \frac{1}{\omega_p^2 C_6 R^2} = 39,6 \text{ nF} \\ \frac{\omega_p}{Q_p} &= \frac{1}{C_6 R_6} \Rightarrow R_6 = \frac{Q_p}{\omega_p C_6} = 1,407 \text{ k}\Omega \end{aligned} \right\}$

d) TIL \Rightarrow Malhas encaxadas \Rightarrow Menos sensibilidade



$$a) \quad \lambda = \frac{2}{T} \frac{1-z^{-1}}{1+z^{-1}} \Rightarrow z^{-1} = \frac{2-\lambda T}{2+\lambda T}$$

$$\alpha = 0,38587 \quad \beta = 0,22826$$

$$T(\lambda) = T(z) \Big|_{z^{-1} = \frac{2-\lambda T}{2+\lambda T}} = \frac{\alpha \left(1 + \frac{2-\lambda T}{2+\lambda T}\right)}{1 - \beta \frac{2-\lambda T}{2+\lambda T}} = \frac{\alpha(2+\lambda T + 2-\lambda T)}{2+\lambda T - \beta(2-\lambda T)} = \frac{4\alpha}{2-2\beta + \lambda T(1+\beta)} = \frac{4\alpha}{T(1+\beta)} = \frac{31,4 \times 10^3}{\lambda + 31,4 \times 10^3}$$

$$b) \quad A\left(\frac{1}{2}\right) = T(\lambda) \Big|_{\lambda \rightarrow \infty} = 0 \Rightarrow A = \infty$$

c)

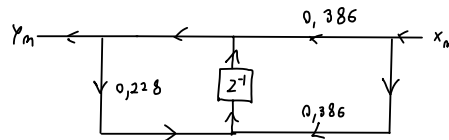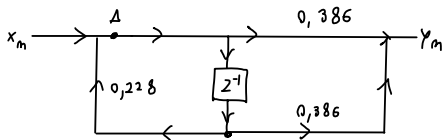

$$IV a) \quad A = -K$$


$$\beta = \left(\frac{R}{R + \frac{1}{sC}} \right)^3 = \left(\frac{sCR}{1 + sCR} \right)^3$$

$$A\beta = 1$$

$$A\beta = \frac{-K \cdot s^3 C^3 R^3}{1 + 3sCR + 3s^2 C^2 R^2 + s^3 C^3 R^3} = \frac{-K}{\frac{1}{s^3 C^3 R^3} + \frac{3}{s^2 C^2 R^2} + \frac{3}{sCR} + 1}$$

$$Re: \quad \frac{-K}{1 - \frac{3}{\omega^2 C^2 R^2}} = 1 \Leftrightarrow -K = 1 - \frac{3}{3R^2 C^2 R^2} \Rightarrow K = 8$$
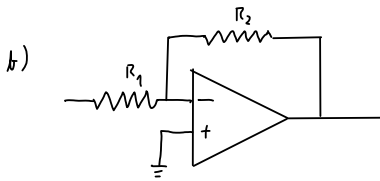
$$Im: \quad -\frac{3}{\omega CR} + \frac{1}{\omega^3 C^3 R^3} = 0 \Leftrightarrow \omega = \frac{1}{\sqrt{3} RC} = 5,774 \times 10^3 \text{ rad/s} \Rightarrow 918,94 \text{ Hz}$$



$$G = -8 = -\frac{R_2}{R_1}$$

$$R_2 = 8R_1 = 1,6 \text{ k}\Omega$$

$$R_1 = R // R_1 = 100 \text{ k}\Omega \Rightarrow R = 200 \text{ k}\Omega //$$

c) A Ponte de Wien f. K_{ra}

d) Um divisor de tensão na entrada