

- 1) C 2) A 3) A 4) B 5) A

II a) $A_p = 0,5 \text{ dB}$ $A_s = 20 \text{ dB}$ $A_c(\omega) = 10 \log [1 + \epsilon^2 C_m^2(\omega)]$ $A_c(4) = 10 \log (1 + 0,35^2 C_m^2(4))$
 $\omega_p = 2\pi \times 1 \text{ K}$ $\omega_s = 2\pi \times 4 \text{ K}$ $A_c(1) = 0,5 \text{ dB} \Leftrightarrow \sqrt{10^{\frac{0,5}{10}} - 1} = \epsilon = 0,35$ $m=1 \rightarrow A_c(4) = 4,7 \text{ X}$
 \downarrow \downarrow $m=2 \rightarrow A_c(4) = 20,7 \checkmark$
 $\Omega_p = 1$ $\Omega_s = 4$

$A_p = 0,5 \text{ dB}$ $\epsilon = 0,35$ $m = 2$

$$T(s) = T(s) \Big|_{s=\frac{\Delta}{\omega_p}} = \frac{K}{s^2 + 1,425s + 1,516} \Big|_{s=\frac{\Delta}{\omega_p}} = \frac{\omega_p^2 \times 1,431}{s^2 + 1,425 \omega_p s + 1,516 \omega_p^2} = \frac{5,65 \times 10^7}{s^2 + 8953s + 5,98 \times 10^7} //$$

b) $A_c(\omega) = 10 \log (1 + 0,35^2 (2\omega^2 - 1)^2) = 0 \Leftrightarrow (2\omega^2 - 1)^2 = 0 \Leftrightarrow \omega = \sqrt{\frac{1}{2}} = \frac{\sqrt{2}}{2}$
 $\omega = \Omega \omega_p = 4443 \text{ rad/s} \rightarrow 707 \text{ Hz}$

c) $Y_1 = Y_3 = Y_4 = \frac{1}{R}$ $T(s) = - \frac{\frac{1}{R^2}}{(\frac{1}{R} + sC_2 + \frac{1}{R} + \frac{1}{R})sC_5 + \frac{1}{R^2}} = - \frac{\frac{1}{R^2 C_2 C_5}}{s^2 + \frac{3}{R C_2} s + \frac{1}{R^2 C_2 C_5}}$ $\frac{3}{R C_2} = 8,886 \times 10^5 \Leftrightarrow C_2 = 750 \text{ pF}$
 $Y_2 = sC_2$ $\frac{1}{R^2 C_2 C_5} = 3,948 \times 10^{11} \Leftrightarrow C_5 = 167 \text{ pF}$
 $Y_5 = sC_5$

d) Malhas encastadas \Rightarrow Menos redundância

III a) $T(z) = \frac{6z}{z + 5 \times 10^4} = \frac{6 \frac{z}{T} (1 - z^{-1})}{\frac{z}{T} (1 - z^{-1}) + 5 \times 10^4 (1 + z^{-1})} = \frac{\frac{12}{T} - \frac{12}{T} z^{-1}}{\frac{z}{T} - \frac{6}{T} z^{-1} + 5 \times 10^4 + 5 \times 10^4 z^{-1}} = \frac{1 - z^{-1}}{1 - 0,778 z^{-1}} \times 5,334$
 $\Omega = \frac{z}{T} \frac{1 - z^{-1}}{1 + z^{-1}}$


b) Filtro analógico é estável \Rightarrow Filtro digital é estável (Polos dentro do círculo unitário)

$Y_m = (x_m - x_{m-1}) 5,334 + y_{m-1} \cdot 0,778$

$100 \text{ kHz} = \frac{6s}{2} \Rightarrow A(z) = A(s) \Big|_{s \rightarrow \infty} = \frac{1}{6} \rightarrow -15,56 \text{ dB}$

c) $T(z) = \frac{0,5}{1 + 0,5z^{-1} - 0,5z^{-2}}$ $Y_m = 0,5(-x_m^0 + z^{-1}x_m^1 + z^{-2}x_m^2 + z^{-3}x_m^3) +$
 $-0,5(-y_{m-1}^0 + z^{-1}y_{m-1}^1 + z^{-2}y_{m-1}^2 + z^{-3}y_{m-1}^3) +$
 $+0,5(-y_{m-2}^0 + z^{-1}y_{m-2}^1 + z^{-2}y_{m-2}^2 + z^{-3}y_{m-2}^3)$
 $Y_m = 0,5x_m - 0,5y_{m-1} + 0,5y_{m-2}$

x_m^i	y_{m-1}^i	y_{m-2}^i		ROM
0	0	0	0	0 0 0 0
0	0	1	0,5	0 1 0 0
0	1	0	-0,5	1 1 0 0
0	1	1	0	0 0 0 0
1	0	0	0,5	0 1 0 0
1	0	1	1	0 1 1 1
1	1	0	0	0 0 0 0
1	1	1	0,5	0 1 0 0 //

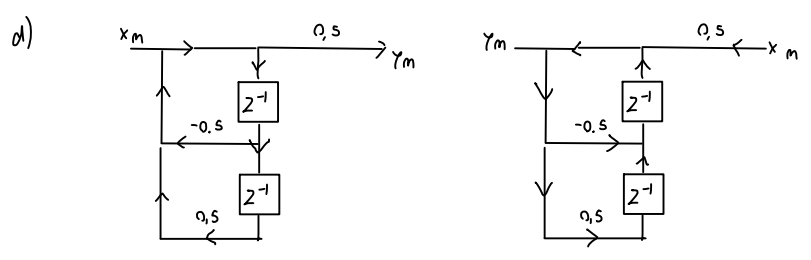

IV a)

$$A = -K$$

$$\beta = \left(\frac{nCR}{1 + nCR} \right)^3$$

$$A\beta = \frac{-K}{1 + \frac{3}{nCR} + \frac{3}{n^2 C^2 R^2} + \frac{1}{n^3 C^3 R^3}}$$

$$A\beta = 1$$

$$\operatorname{Im}\{A\beta\} = 0$$

$$\frac{3}{\omega CR} - \frac{1}{\omega^3 C^3 R^3} = 0 \Leftrightarrow 3 = \frac{1}{\omega^2 C^2 R^2} \Leftrightarrow \omega = \frac{1}{\sqrt{3} RC} = 5,774 \times 10^3 \text{ rad/s} \Rightarrow 918,9 \text{ Hz}$$

$$\operatorname{Re}\{A\beta\} = 1$$

$$\frac{-K}{1 - \frac{3}{\omega^2 C^2 R^2}} = 1 \Leftrightarrow -K = 1 - \frac{3}{\frac{R^2 C^2}{3 R^2 C^2}} \Leftrightarrow K = 8$$