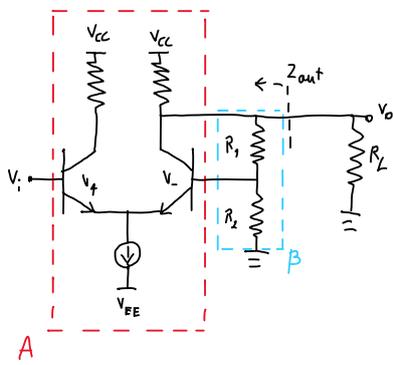



a)




→ Malha à entrada ⇒ Série - Paralelo → Tensão - Tensão  
 → Na saída

$$\text{Matriz } H: \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

Esquema equivalente de A

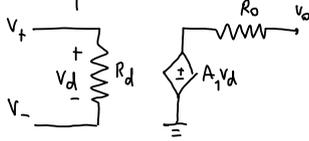


Esquema equivalente de β

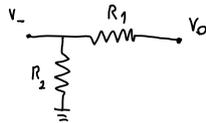

$A_1 = 8000$       $R_L = 100 \text{ k}\Omega$   
 $R_d = 10 \text{ k}\Omega$       $R_1 = 40 \text{ k}\Omega$   
 $R_0 = 5 \text{ k}\Omega$       $R_2 = 10 \text{ k}\Omega$

Circuito total

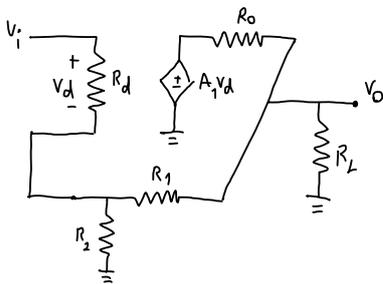


b) A:

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} = R_d$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0} = \frac{A_1 V_d}{R_0} = \frac{A_1 R_d}{R_0}$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} = 0$$

$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0} = \frac{1}{R_0}$$

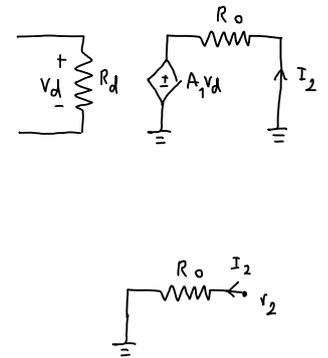



β:

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} = R_2 // R_1$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0} = -\frac{R_2}{R_2 + R_1}$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} = \frac{R_2}{R_2 + R_1}$$


$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0} = \frac{1}{R_2 + R_1}$$

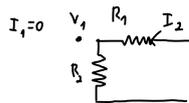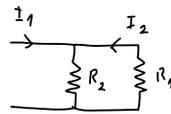

$$H_A = \begin{bmatrix} R_d & 0 \\ \frac{A_1 R_d}{R_0} & \frac{1}{R_0} \end{bmatrix} = \begin{bmatrix} 10 \text{ k}\Omega & 0 \\ -16 \text{ K} & 0.2 \text{ mS} \end{bmatrix}$$

$$H_\beta = \begin{bmatrix} R_2 // R_1 & \frac{R_2}{R_2 + R_1} \\ -\frac{R_2}{R_2 + R_1} & \frac{1}{R_1 + R_2} \end{bmatrix} = \begin{bmatrix} 8 \text{ k}\Omega & 0.2 \\ -0.2 & 10 \mu\text{S} \end{bmatrix}$$

c)/d)

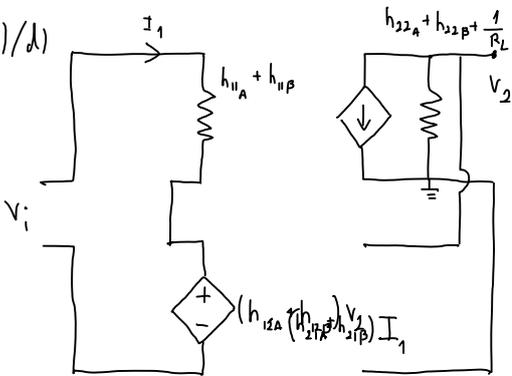

$$A' = \frac{V_2}{V_1 A} = -\frac{h_{21A} + h_{21\beta}}{(h_{11A} + h_{11\beta})(h_{22A} + h_{22\beta} + \frac{1}{R_L})} = 3865$$

$$A_f = \frac{V_2}{V_1} = \frac{A'}{1 + A'\beta'} = 4.99 \approx 5$$

$$\beta' = h_{12A} + h_{12\beta} = 0.2$$

$$Z_{0A'} = \frac{1}{h_{22A} + h_{22\beta} + \frac{1}{R_L}}$$

$$Z_{of} = \frac{Z_{0A'}}{1 + \beta' A'}$$

$$Z_{out} = \frac{1}{\frac{1}{Z_{of}} - \frac{1}{R_L}}$$

$$Z_{0A'} = 4.35 \text{ k}\Omega$$

$$Z_{of} = 5.6 \Omega$$

$$Z_{out} = 5.6 \Omega$$

2)  $A_0 = 134 \text{ dB}$

$\beta = 0,2 \Rightarrow -14 \text{ dB}$

$A_0 \beta = 120 \text{ dB}$

Antes realimentación

$M_F = 0$

$M_G = -60 \text{ dB}$

Después realimentación

$M_F = 45^\circ$

$M_G = 40 \text{ dB}$

