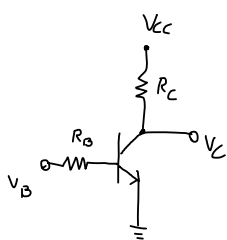


1 a)

a)



$$\begin{aligned} V_{CC} &= 10V \\ R_B &= 50k\Omega \\ R_C &= 1k\Omega \\ \beta &= 100 \end{aligned}$$

Caso $V_B = 0V$

Corte: logo $i_B = i_C = i_E = 0$

$$\begin{aligned} V_{BE} &= 0 \\ V_{CE} &= 10V \\ V_{CB} &= 10V \end{aligned}$$

Caso $V_B = 3.2V$

$$V_B - V_{R_B} - V_{BE} = 0 \Leftrightarrow i_B = \frac{V_B - V_{BE}}{R_B} = 0.05mA$$

$$i_C = \beta i_B = 5mA$$

$$V_C = V_{CE} = V_{CC} - R_C i_C = 5V$$

Porém tudo errado!

$$V_{CE} = 5V \quad i_B = 0.05mA$$

$$V_{BE} = 0.7V \quad i_C = 5mA$$

$$V_{CB} = 4.3V \quad i_E = 5.05mA$$

Caso $V_B = 10V$

Super Saturação:

$$i_B = \frac{V_B - V_{BE}}{R_B} = 0.186mA$$


$$i_C = \frac{V_{CC} - V_{CE}}{R_C} = 9.8mA$$

$$V_{BE} = 0.7V \quad i_B = 0.186mA$$

$$V_{CE} = 0.2V \quad i_C = 9.8mA$$

$$V_{CB} = 0.5V \quad i_E = 9.986mA$$

b)

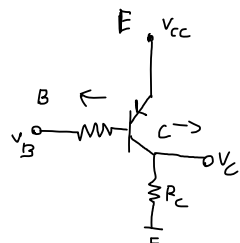

$$V_B = 10V$$

Assumindo corte

$$\begin{aligned} i_B &= 0 \\ i_C &= 0 \\ i_E &= 0 \end{aligned}$$

$$V_{CC} = V_{EB} + V_B + V_{R_B} \Leftrightarrow$$

$$V_{EB} = 0$$

$$V_{CC} = V_{EC} + V_{R_C} \Leftrightarrow V_{EC} = 10V$$


$$V_{EC} = 10V \quad i_B = 0$$

$$V_{EB} = 0 \quad i_C = 0$$


$$V_{EB} = 0 \quad i_E = 0$$

$$\frac{\Delta V_C}{\Delta V_B} = -\frac{R_C \beta}{R_B} = -2$$

mpm:

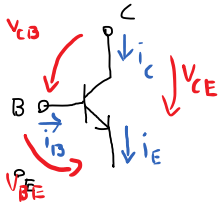

Pmp

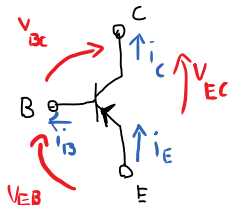

Equações fundamentais

mpm:

$$i_C + i_B = i_E$$

$$V_{CB} + V_{BE} = V_{CE}$$

Pmp:

$$i_C + i_B = i_E$$

$$V_{EB} + V_{BC} = V_{EC}$$

Caso $V_B = 6.8V$

Assumindo Z.A.D. $V_{BE} = 0.7V$

$$V_B = V_{R_B} + V_{BE} \Leftrightarrow i_B = \frac{V_B - V_{BE}}{R_B} = 0.122mA$$

$$i_C = \beta i_B = 12.2mA$$

$$V_C = V_{CE} = V_{CC} - R_C i_C = -2.2V \leftarrow \text{Impossível!}$$

Está em saturação!

$$i_C = \frac{V_{CC} - V_{CE}}{R_C} = 9.8mA$$

$$V_{BE} = 0.7V \quad i_B = 0.122mA$$

$$V_{CE} = 0.2V \quad i_C = 9.8mA$$

$$V_{CB} = 0.5V \quad i_E = 9.922mA$$

Z.A.D

$$\frac{\Delta V_C}{\Delta V_B} = \frac{V_{Cf} - V_{Ci}}{V_{Bf} - V_{Bi}} = \frac{-R_C (\Delta i_C)}{R_B (\Delta i_B)} = \frac{-R_C \beta (\Delta i_B)}{R_B (\Delta i_B)} = -\frac{R_C \beta}{R_B} = -2$$

$$V_B = 3.2V$$

Assumindo condução

$$i_B = \frac{V_{CC} - V_B - V_{EB}}{R_B} = 0.122mA$$

Assumindo ZAD

$$i_C = 100 i_B = 12.2mA$$

$$V_{EC} = V_{CC} - V_{R_C} = -2.2 \text{ ! Impossível!}$$

Assumindo saturação

$$i_C = \frac{V_{CC} - V_{EC}}{R_C} = 9.8mA$$

$$V_{EC} = 0.2V \quad i_C = 9.8mA \quad V_C = 9.8V$$

$$V_{EB} = 0.7V \quad i_B = 0.25mA$$

$$i_E = 10.05mA$$

Funcionamento do BJT (mpm):

- Corte:


$$V_{BE} < 0 \quad [V_{BE} < 0,5V]$$

$$V_{CE} > 0$$

$$i_B = 0$$

$$i_C = 0$$

Esquema:

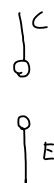

- Saturação:


$$V_{BE} > 0$$

$$V_{CE} < V_{BE}$$

$$i_C > 0 \text{ e } i_C < \beta i_B$$

$$i_B > 0$$

Esquema:

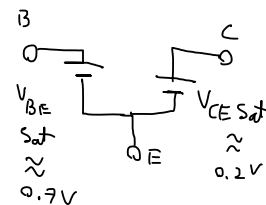

- Zona ativa


$$V_{BE} > 0$$

$$V_{CE} > V_{BE}$$

$$V_{BE} \approx 0.7V$$

$$i_C = \beta i_B$$

Esquema:

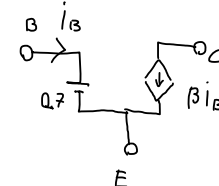

$$V_B = 6.8V$$

Assumindo condução e ZAD

$$i_B = \frac{V_{CC} - V_B - V_{EB}}{R_B} = 0.05mA$$

$$i_C = \beta i_B = 5mA$$

$$V_{EC} = V_{CC} - V_{R_C} = 5V$$


$$V_{EC} = 5V \quad i_C = 5mA$$

$$V_{EB} = 0.7V \quad i_B = 0.05mA$$

$$i_E = 5.05mA$$

$$V_C = 5V$$

1.2) a)

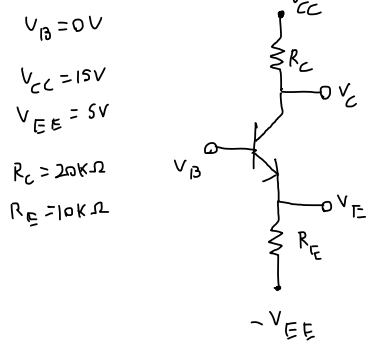

Assumir conclusão a e z ad

$V_C = V_{R_C} + V_{C_B}$
 $V_{E_E} = V_{R_E} + V_{B_E} \Rightarrow$
 $i_E = \frac{V_{E_E} - V_{B_E}}{R_E} = 0.43 \text{ mA} \quad i_C \approx i_E$


$V_E = 4.3 \Rightarrow -0.7 \text{ V}$
 $V_C = 15 - R_C i_C = 6.4 \text{ V}$

$V_{B_{min}} = 0.5 - V_{E_E} = -4.5 \text{ V (para não saturar)}$
 $V_{B_{max}} = V_{B_E} + R_E i_E - V_{E_E} = 0.7 + R_E i_{C_{max}} - 5 = 2.1 \text{ V (para não saturar)}$


$-V_{E_E} + V_{R_E} + V_{C_E} + V_{R_C} = V_{C_C} \Leftrightarrow \frac{20 - 0.7}{30 \times 10^3} = I_{C_{max}}$

$\Delta V_C = -R_C \Delta i_C$
 $\Delta V_B = R_E \Delta i_C$
 $\frac{\Delta V_C}{\Delta V_B} \approx -\frac{R_C}{R_E}$
 $\frac{\Delta V_E}{\Delta V_B} \approx 1$



b)

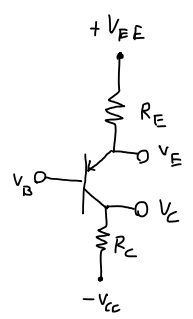

$V_C = 15 \text{ V}$
 $V_{E_E} = 5 \text{ V}$
 $R_C = 20 \text{ k}\Omega$
 $R_E = 10 \text{ k}\Omega$
 $V_{R_C} + V_{B_C} = V_{C_C}$
 $V_{E_E} = V_{R_E} + V_{B_E}$
 $\frac{\Delta V_C}{\Delta V_B} = -\frac{R_C}{R_E} \quad \frac{\Delta V_B}{\Delta V_E} = 1$
 $\frac{5 - 0.7}{10 \text{ k}} = I_E = 0.43 \text{ mA}$
 $I_C = 0.43 \text{ mA}$
 $V_E = V_{E_E} - R_E I_E = 0.7 \text{ V}$
 $V_C = R_C I_C - V_{C_C} = -6.4 \text{ V}$

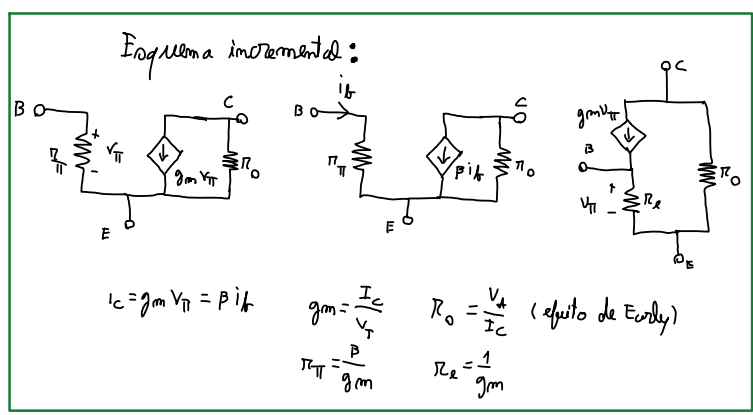


1.4)

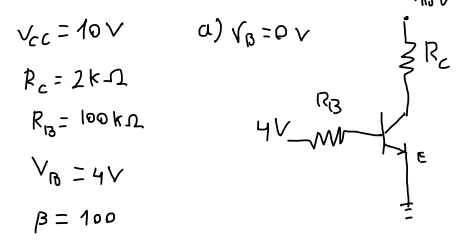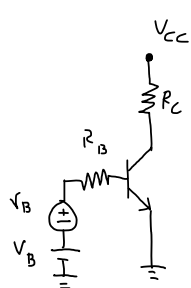

$i_B = 0.033 \text{ mA}$
 $i_C = 3.3 \text{ mA}$
 $i_E = 3.333 \text{ mA}$
 $V_{B_E} = 0.7 \text{ V}$
 $V_{C_B} = 2.7 \text{ V}$
 $V_{C_E} = 3.4 \text{ V}$


$4 = V_{R_B} + V_{B_E} \Leftrightarrow \frac{4 - V_{B_E}}{R_B} = i_B$
 $4 - 10 - R_B i_B + V_{C_B} + R_C i_C = 0 \Leftrightarrow V_{C_B} = 2.7$
 $i_B = 0.033 \text{ mA}$
 $i_C = \beta i_B = 3.3 \text{ mA}$

b)

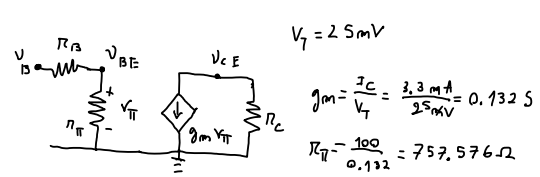

$V_B = \sin(\omega t) \text{ V}$
 $V_B = V_{B_B} + V_{B_E} \Leftrightarrow$
 $\Leftrightarrow V_B - i_B r_{B_B} = V_{B_E} \Leftrightarrow$
 $\Leftrightarrow V_{B_E} = V_B \left(1 - \frac{r_{B_B}}{r_{B_B} + r_{B_E}}\right) = 7.5 \text{ mV}(\omega t) \text{ mV}$
 $V_{C_E} = -i_C R_C = -g_m V_{B_E} r_{C_E} = -2 \sin(\omega t) \text{ V}$
 $i_B = \frac{g_m V_{B_E}}{\beta} = 0.01 \sin(\omega t) \text{ mA}$
 $i_C = \sin(\omega t) \text{ mA}$



1.5)

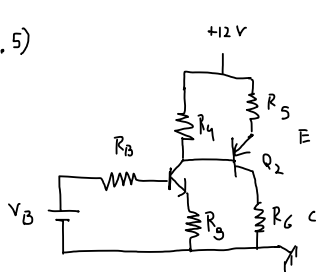

$V_B = V_{C_C} \frac{R_2}{R_1 + R_2} \quad R_{B_B} = R_1 // R_2$
 $V_B = R_B i_{B_1} + V_{B_E_1} + R_3 i_{E_1}$
 $I_E = I_C + I_B \Leftrightarrow I_E = (1 + \beta) I_B$
 $I_C = \beta I_B$
 $V_B = R_B i_{B_1} + V_{B_E_1} + R_3 (1 + \beta) i_{B_1} \Rightarrow i_{B_1} = 24.4 \mu\text{A}$
 $i_{E_1} = 1.24 \text{ mA} \Rightarrow i_{C_1} = 1.22 \text{ mA}$
 $R_5 i_{E_2} + V_{E_B_2} = I_4 R_4$
 $i_{E_2} = -i_{B_2} + i_{C_1}$
 $i_{E_2} = I_{C_2} + i_{B_2}$
 $i_{C_2} = \beta i_{B_2}$
 $R_5 (\beta i_{B_2} + i_{B_2}) + V_{E_B_2} = -i_{B_2} R_4 + I_{C_1} R_4 \Leftrightarrow$
 $\Leftrightarrow R_5 \beta i_{B_2} + R_5 i_{B_2} + i_{B_2} R_4 = I_{C_1} R_4 - V_{E_B_2} \Leftrightarrow$
 $\Leftrightarrow i_{B_2} = 90.9 \mu\text{A}$
 $12 = V_{R_4} + V_{C_E_1} + V_{R_3} \Leftrightarrow V_{C_E_1} = 5 \text{ V}$
 $12 = V_{R_5} + V_{E_C_2} + V_{R_6} \Leftrightarrow V_{E_C_2} = 6.36 \text{ V}$

$i_{B_1} = 24.4 \mu\text{A} \quad V_{B_E_1} = 0.7 \text{ V}$
 $i_{E_1} = 1.24 \text{ mA} \quad V_{C_B_1} = 4.3 \text{ V}$
 $i_{C_1} = 1.22 \text{ mA} \quad V_{C_E_1} = 5 \text{ V}$
 $i_{B_2} = 90.9 \mu\text{A} \quad V_{E_B_2} = 0.7 \text{ V}$
 $i_{E_2} = 1.41 \text{ mA} \quad V_{B_C_2} = 5.6 \text{ V}$
 $i_{C_2} = 1.82 \text{ mA} \quad V_{E_C_2} = 6.36 \text{ V}$


1.6)

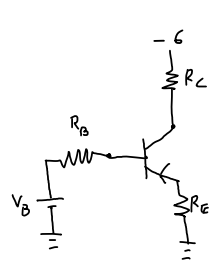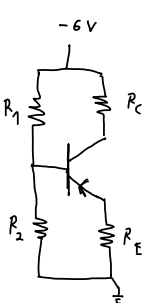

$R_B = R_1 // R_2$
 $V_B = V_{C_C} \frac{R_2}{R_1 + R_2}$
 $V_B = -R_B i_B - V_{E_B} - R_E (1 + \beta) i_B$
 $i_B = \frac{V_B + V_{E_B}}{-R_B - R_E (1 + \beta)} = 11.4 \mu\text{A}$
 $I_C = 100 i_B = 1.14 \text{ mA}$
 $I_E = I_C + I_B = 1.15 \text{ mA}$
 $-6 = -I_C R_C - V_{C_E} - I_E R_E \Leftrightarrow V_{C_E} = 2.57 \text{ V}$

a) $i_B = 11.4 \mu\text{A} \quad V_{B_E} = 0.7 \text{ V}$
 $I_C = 1.14 \text{ mA} \quad V_{C_B} = 1.872$
 $I_E = 1.15 \text{ mA} \quad V_{C_E} = 2.57 \text{ V}$

b)

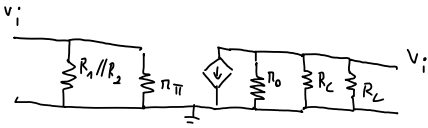

$g_m = 0.0456 \text{ S}$
 $V_i = V_{B_E}$
 $i_B = g_m V_{B_E}$
 $r_o = \frac{V_A}{I_C}$
 $r_{B_E} = \frac{\beta}{g_m}$
 $r_i = R_1 // R_2$
 $r_o = 0.0456 \text{ S}$
 $V_i = V_{B_E}$
 $i_B = g_m V_{B_E}$
 $r_o = \frac{V_A}{I_C}$
 $r_{B_E} = \frac{\beta}{g_m}$
 $r_i = R_1 // R_2$