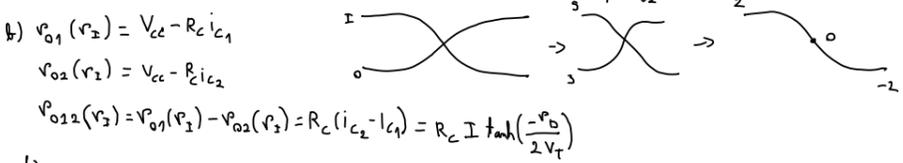



4.1) a) $i_{c1} = \frac{1}{I_{EE}} \frac{1}{1 + e^{-\frac{v_D}{V_T}}}$ $i_{c2} = \frac{1}{I_{EE}} \frac{1}{1 + e^{\frac{v_D}{V_T}}}$...

$v_D = v_{BE1} - v_{BE2}$ $i_{c1} = \frac{\alpha I}{1 + e^{-\frac{v_D}{V_T}}}$ $i_{c2} = \frac{\alpha I}{1 + e^{\frac{v_D}{V_T}}}$ $\tanh(x) = \frac{e^{2x} - 1}{e^{2x} + 1}$ $\tanh(\theta) \approx \frac{\theta}{4V_T}$




b) $v_{O1}(v_D) = V_{CC} - R_C i_{c1}$
 $v_{O2}(v_D) = V_{CC} - R_C i_{c2}$
 $v_{O12}(v_D) = v_{O1}(v_D) - v_{O2}(v_D) = R_C (i_{c2} - i_{c1}) = R_C I_{EE} \tanh\left(\frac{-v_D}{2V_T}\right)$

Re $|v_D| \geq 4V_T$ esta totalmente desequilibrado
 Re $|v_D| \ll 2V_T$ ($|v_D| < 10mV$) \rightarrow amplificador lineal

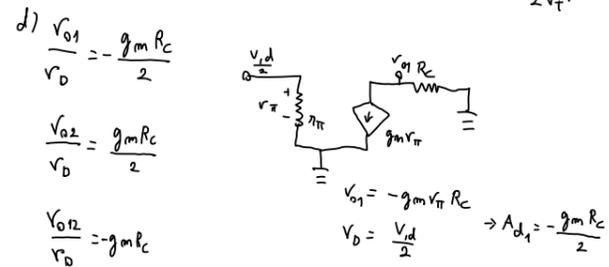


4.3)

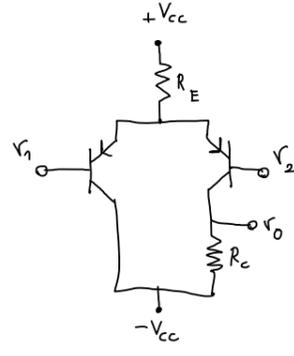

$\beta = 100$
 $V_{CC} = 6V$
 $R_E = 100k\Omega$
 $R_C = 10k\Omega$

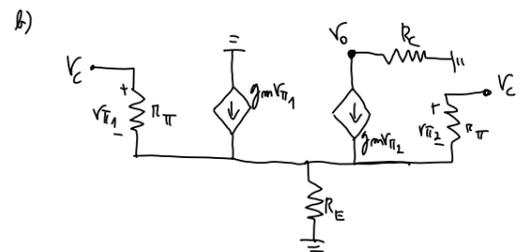a) $V_{CC} - v_{O1} = V_{R_C} + v_{R_{E1}}$
 $V_{R_E} = V_{CC} - v_{O1} - v_{R_{E1}} = 6 - 0.7 = 5.3V$
 $2 \cdot I_{E1} = \frac{V_{R_E}}{R_E} \Leftrightarrow I_{E1} = I_{E2} = 26.5\mu A$
 $V_{R_{E1}} = -V_{R_E} + V_{CC} - (-V_{CC}) = 6.7V$
 $V_{R_{E2}} = -V_{R_E} + 2 \cdot V_{CC} - R_C i_{c2} = 6.435V$



D:

$v_{O1} = -R_C g_m v_{\pi 1}$ $v_{\pi 1} = \frac{v_{id}}{2}$
 $v_{O2} = R_C g_m v_{\pi 2}$ $v_{\pi 2} = -\frac{v_{id}}{2}$
 $A_d = \frac{v_O}{v_{id}} = \frac{R_C g_m}{2} = -5.3$


C: $v_O = -g_m v_{\pi 3} R_C$

$\frac{v_{\pi 1}}{r_{\pi 1}} + g_m v_{\pi 1} + g_m v_{\pi 2} + \frac{v_{O2}}{R_C} = \frac{v_C - v_{\pi 1}}{R_E} \Rightarrow v_{\pi 1} = \frac{v_C}{2R_E(\frac{1}{r_{\pi 1}} + g_m) + 1}$
 $v_{\pi 1} = v_{\pi 2} = v_E$
 $A_C = \frac{v_O}{v_C} = -\frac{g_m R_C}{2R_E(\frac{1}{r_{\pi 1}} + g_m) + 1} \approx -\frac{R_C}{R_E} = -0.05$

CMRR = $\left| \frac{A_d}{A_C} \right| = 106$
 CMRR_{dB} = 40.5 dB


c) $R_{ic} = \frac{v_C}{i_{b1} + i_{b2}} = \frac{v_C}{\frac{v_{\pi 1}}{r_{\pi 1}} + \frac{v_{\pi 2}}{r_{\pi 2}}} = \frac{v_C}{\frac{v_C}{2R_E(\frac{1}{r_{\pi 1}} + g_m) + 1} \cdot \frac{2}{r_{\pi 1}}}$
 $R_{ic} \approx 10M\Omega$
 D: $R_{id} = 2r_{\pi 1}$

3.1)

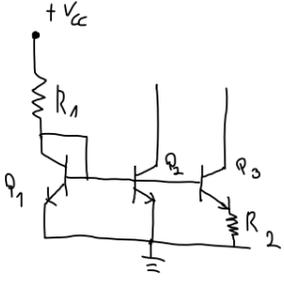


$V_A = 100V$
 $\beta = 100$
 $V_{CC} = 6V$
 $R_1 = 20k\Omega$

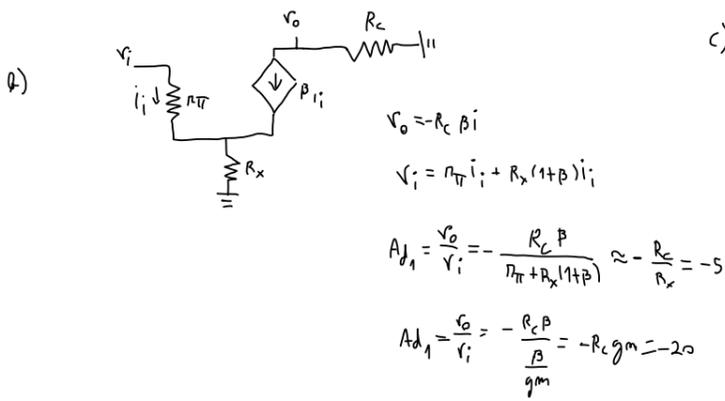a) $I_{REF} = I_{C1} + \frac{I_{C1}}{\beta} + \frac{I_{C2}}{\beta}$
 $I_C = I_S e^{\frac{V_{BE}}{V_T}} \left(1 + \frac{V_{CE}}{V_A} \right) \Rightarrow \frac{I_{C2}}{I_{C1}} = \frac{1 + \frac{V_{CE2}}{V_A}}{1 + \frac{V_{CE1}}{V_A}}$




4.2)

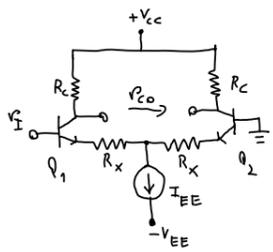

$I_{EE} = 100\mu A$
 $R_C = 10k\Omega$

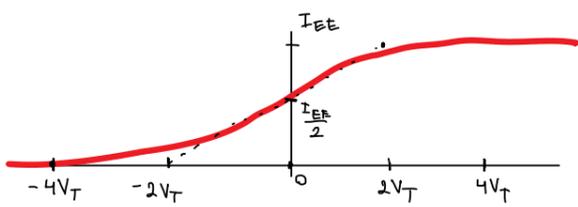
a) $i_{c1}(v_I) \quad v_{O1}(v_I)$
 $v_I = v_{BE1} + R_x i_{c1} - R_x i_{c2} - v_{BE2} \Leftrightarrow v_I = R_x (i_{c1} - i_{c2}) + v_{BE1} - v_{BE2}$
 $R_x = 0 \Rightarrow v_I = v_{BE1} - v_{BE2}$



$i_{c1} = \frac{I_{FE}}{1 + \frac{i_{c2}}{i_{c1}}}$ $\Leftrightarrow i_{c1} = \frac{I_{FE}}{1 + e^{-\frac{v_I}{V_T}}}$


$V_{CC} - v_O = R_C i_{c1} \Rightarrow v_O = V_{CC} - R_C i_{c1}$ or $v_O = v_{O1} - v_{O2} = R_C (i_{c2} - i_{c1}) = R_C I_{EE} \tanh\left(\frac{-v_I}{2V_T}\right)$

$R_x = 2k\Omega \Rightarrow v_I = R_x (i_{c1} - i_{c2}) + v_{BE1} - v_{BE2} \ll$
 $I_{EE} = i_{c1} + i_{c2} \Rightarrow \begin{cases} v_I = R_x (i_{c1} - i_{c2}) \\ I_{EE} = i_{c1} + i_{c2} \end{cases} \Rightarrow \begin{cases} \frac{v_I}{R_x} + i_{c2} = i_{c1} \\ I_{EE} = \frac{v_I}{R_x} + 2i_{c2} \end{cases} \Rightarrow \begin{cases} i_{c1} = \frac{I_{EE}}{2} + \frac{v_I}{2R_x} \\ i_{c2} = \frac{I_{EE}}{2} - \frac{v_I}{2R_x} \end{cases}$

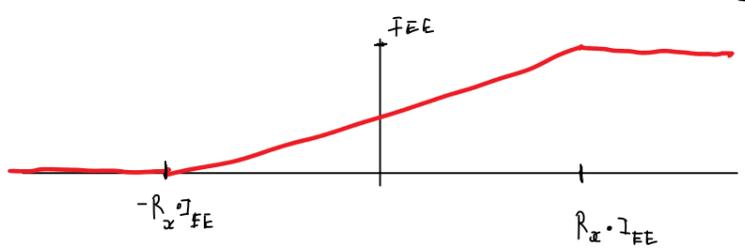


$v_O = V_{CC} - R_C i_{c1}$
 $v_O = R_C I_{EE} \tanh\left(\frac{-v_I}{2V_T}\right)$

1)

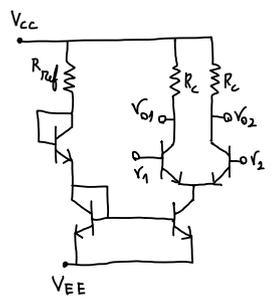


$V_{CC} = -V_{EE} = 4V$
 $R_C = 2k\Omega$
 $V_{BE_{on}} = 0,7V$
 $\beta = 80$
 $V_A = 50V$

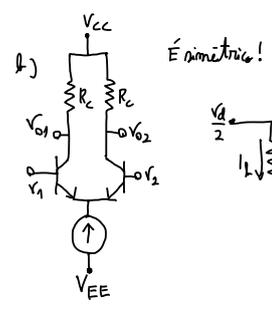a) $V_{CC} - V_{EE} = V_{R_{ref}} + 0,7 + 0,7 \Leftrightarrow$
 $\Leftrightarrow 8 - 1,4 = V_{R_{ref}} \Leftrightarrow$
 $\Leftrightarrow 6,6 = R_{ref} \cdot I_{C3} \Leftrightarrow$
 $\Leftrightarrow \frac{6,6}{I_{C1} + I_{C2}} = R_{ref} \Leftrightarrow R_{ref} = 3,3k\Omega$



É simétrica!


$r_o = \frac{V_A}{I_C} = 50k\Omega$
 $R_o = r_o // R_C$
 $V_1 = i_{b1} \pi_{\pi} \Rightarrow \frac{V_1}{\pi_{\pi}} = i_{b1}$
 $R_o = -\frac{V_{o1}}{\beta i_b} \Leftrightarrow -R_o \cdot \beta \cdot \frac{V_1}{\pi_{\pi}} = V_{o1}$
 $A_{d1} = \frac{V_{o1}}{V_d} = -\frac{R_o \beta}{2 \cdot \pi_{\pi}} = -38,46$
 $A_{d2} = \frac{V_{o2}}{V_d} = \frac{R_o \beta}{2 \cdot \pi_{\pi}} = 38,46$
 $A_d = \frac{V_{o12}}{V_d} = -\frac{R_o \beta}{\pi_{\pi}} = -76,923$

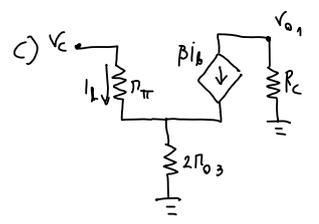

$r_{o3} = \frac{V_A}{I_{C3}} = 25k\Omega$
 $V_C = i_{b1} \pi_{\pi} + (1 + \beta) i_b \cdot 2\pi_{o3}$
 $V_{o1} = -\beta i_b R_C \Rightarrow \frac{V_{o1}}{V_C} = -\frac{\beta R_C}{\pi_{\pi} + (1 + \beta) \cdot 2 \cdot \pi_{o3}} = -0,039$
 $\frac{V_{o1}}{V_C} = -0,039 \Rightarrow A_{C12} = 0$

d) Q_1 e Q_2 : $V_{C_{Max}} = V_{CC} - R_C I_{C1} = 2V$ (Para mão direita)
 Q_3 : $V_{C_{Min}} = V_{EE} + \underbrace{V_{CE3}}_{0,7V} + V_{BE1} = -2,6V$ (Aumentando limite de saturação)

e) T. Bifreqüência

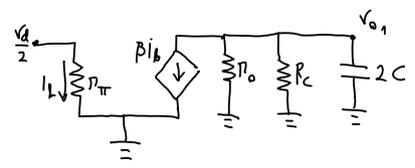

$s = j\omega$
 $V_{o1} = -(\pi_0 // R_C // \frac{1}{2C\Delta}) \beta i_b$
 $i_b = \pi_{\pi} \frac{V_d}{2}$
 $A_{d1} = -\frac{\pi_{\pi} \beta}{2} \cdot \frac{R_o R_C}{R_C + \pi_0 + 2C \pi_0 R_C \Delta}$
 $A_d = -\frac{\beta \pi_{\pi} \pi_0 R_C}{1 + \frac{2C \pi_0 R_C}{R_C + \pi_0} \Delta} \Rightarrow \text{freq. corte } -3dB = \text{freq. } f_{db}$
 $\omega_p = \frac{R_C + \pi_0}{2C \pi_0 R_C} \Rightarrow f_c = \frac{R_C + \pi_0}{4\pi C \pi_0 R_C} = 41MHz$