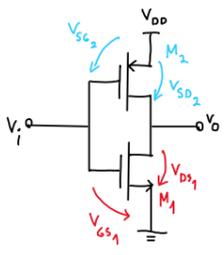


1)



$V_i = 0$

$V_i = V_{GS1} = 0 < V_{TH}^m \Rightarrow M_1$ ao corte $\Rightarrow i_{D1} = 0$

$M_2 \rightarrow$ Triodo $\Rightarrow i_{D2} = k_p [2(V_{GS2} - V_{TH}^p)V_{SD2} - V_{SD2}^2] = 0 \Leftrightarrow$

$\Leftrightarrow (2(V_{GS2} - V_{TH}^p) - V_{SD2}) V_{SD2} = 0 \Leftrightarrow \begin{cases} V_{SD2} = 0 \\ V_{SD2} = 2(V_{GS2} - V_{TH}^p) = 2(V_{DD} - V_{TH}^p) = 6.6V \end{cases}$

$V_{SD2} = 0 \leadsto V_{SD2} < V_{GS2} - V_{TH}^p \Leftrightarrow 0 < 5 - 1.7 = 3.3V$

\hookrightarrow Confirma triodo $\Rightarrow V_o = V_{DD} - V_{SD2} = 5V$

$V_i = V_{DD}$

$V_{GS2} = V_{DD} - V_i = 0 < V_{TH}^p \Rightarrow M_2$ ao corte $\Rightarrow i_{D2} = 0$

$M_1 \rightarrow$ Triodo $\Rightarrow i_{D1} = k_n [2(V_{GS1} - V_{TH}^m)V_{DS1} - V_{DS1}^2] = 0 \Leftrightarrow$

$\Leftrightarrow (2(V_{GS1} - V_{TH}^m) - V_{DS1}) V_{DS1} = 0 \Leftrightarrow \begin{cases} V_{DS1} = 0 \\ V_{DS1} = 2(V_{GS1} - V_{TH}^m) = 2(V_{DD} - V_{TH}^m) = 6.2V \end{cases}$

$V_{DS1} = 0 \leadsto V_{DS1} < V_{GS1} - V_{TH}^m \Leftrightarrow 0 < 5 - 1.9 = 3.1V$

\hookrightarrow Confirma o triodo $\Rightarrow V_o = V_{DS1} = 0$

$\Rightarrow V_i = \frac{V_{DD}}{2}$

Vamos ver para M_1 e M_2 no saturação

$i_{D1} = k_n (V_{GS1} - V_{TH}^m)^2 = 105 \mu A$
 $i_{D2} = k_p (V_{GS2} - V_{TH}^p)^2 = 154 \mu A$
 $\Rightarrow i_{D2} \neq i_{D1}$ Não temos os 2 em saturação!

i_{D2} pode passar na M_2 só se estiver no triodo:


$i_{D1} = k_p [2(V_{GS2} - V_{TH}^p)V_{SD2} - V_{SD2}^2] \Leftrightarrow k_p V_{SD2}^2 - 2k_p (V_{GS2} - V_{TH}^p) V_{SD2} + i_{D1} = 0 \Leftrightarrow$

$\Leftrightarrow V_{SD2} = \frac{2k_p (V_{GS2} - V_{TH}^p) \pm \sqrt{4k_p^2 (V_{GS2} - V_{TH}^p)^2 - 4k_p i_{D1}}}{2k_p} = \begin{cases} V_{SD2} = 1.25V \\ V_{SD2} = 0.35V \end{cases}$


$V_{SD2} = 0.35V \leadsto V_{SD2} < V_{GS2} - V_{TH}^p \Leftrightarrow 0.35 < 2.5 - 1.7 \Leftrightarrow 0.35 < 0.8 \Rightarrow$ Confirma M_2 a triodo!

Logo $V_o = V_{DD} - V_{SD2} = 4.65V$ e $i_D = i_{D1} = i_{D2} = 105 \mu A$

3.2)

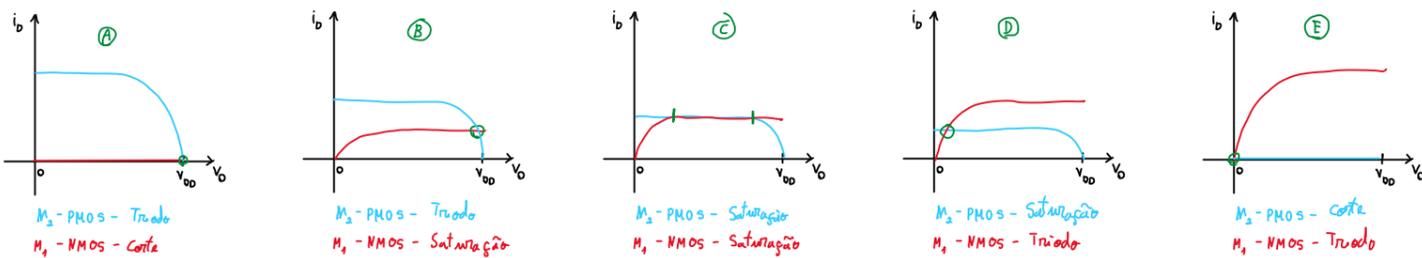

	A	B	C	D	E
PMOS	C	S	S	T	T
NMOS	T	T	S	S	C

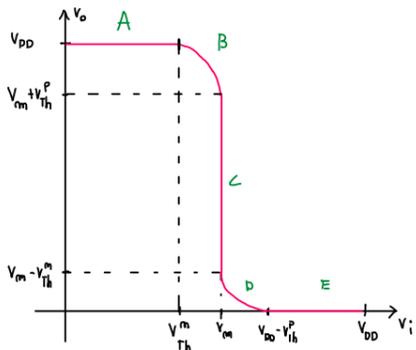

$V_{TH}^m = 1.9V$

$V_{DD} - V_{TH}^p = 3.3V$

$V_m = 2.57V$

$V_m + V_{TH}^p = 4.27V$

$V_m - V_{TH}^m = 0.67V$

$V_m = ?$
 $i_{D1} = k_n (V_{GS1} - V_{TH}^m)^2$
 $i_{D2} = k_p (V_{GS2} - V_{TH}^p)^2$

$\Rightarrow k_n (V_i - V_{TH}^m)^2 = k_p (V_{DD} - V_i - V_{TH}^p)^2 \Rightarrow V_m = V_i = \frac{\sqrt{k_n} V_{TH}^m + \sqrt{k_p} (V_{DD} - V_{TH}^p)}{\sqrt{k_n} + \sqrt{k_p}} = 2.57V$

3.3) i_D Max \Rightarrow Saturação

$V_i = V_m \Rightarrow i_D = k_n (V_m - V_{TH}^m)^2 = 130 \mu A$

3.4) $V_{OH} = V_{DD} = 5V$

$V_{TL} \rightarrow$ Zona B

$V_{OL} = V_{GS} = 0V$

$i_{D1} = i_{D2} \Rightarrow k_n (V_i - V_{TH}^m)^2 = k_p [2(V_{DD} - V_i - V_{TH}^p)(V_{DD} - V_o) - (V_{DD} - V_o)^2]$

$V_{TL} = 2.73V$

Deriva em ordem a V_i :

$V_{TH} = 2.38V$

$2k_n (V_i - V_{TH}^m) = 2k_p [V_{DD} - V_{DD} + (V_{DD} - V_i - V_{TH}^p) \left(\frac{dV_o}{dV_i}\right) - (V_{DD} - V_o) \left(\frac{dV_o}{dV_i}\right)]$

$NM_L = V_{TL} - V_{OL} = 2.38V$

Com $\frac{dV_o}{dV_i} = -1$ e $V_i = V_{TL}$:

$NM_H = V_{OH} - V_{TH} = 2.27V$

$k_n (V_i - V_{TH}^m) = k_p (2V_o - V_{TL} - V_{TH}^p - V_{DD}) \Leftrightarrow V_o = \frac{1}{2} \left(1 + \frac{k_n}{k_p}\right) V_{TL} + \frac{1}{2} \left(V_{DD} - \frac{k_n}{k_p} V_{TH}^m + V_{TH}^p\right)$

$\begin{cases} V_{TL} = -11.5V \\ V_{TL} = 2.38V \end{cases}$

Temos que ter $V_{GS1} = V_{TL} > V_{TH}^m \Rightarrow V_{TL} = 2.38V$

$V_{TH} \Rightarrow$ Zona D

$i_{D1} = i_{D2} \Rightarrow k_n [2(V_i - V_{TH}^m)V_o - V_o^2] = k_p (V_{DD} - V_i - V_{TH}^p)^2 \Rightarrow \begin{cases} V_{TH} = -11.85V \\ V_{TH} = 2.73V \end{cases}$

Deriva em ordem a V_i :


$2k_n [V_o + (V_{TH}^m - V_i) \left(\frac{dV_o}{dV_i}\right) + V_o \left(-\frac{dV_o}{dV_i}\right)] = -2k_p (V_{DD} - V_i - V_{TH}^p)$

Temos que ter $V_{GS1} = V_{TH} > V_{TH}^m \Rightarrow V_{TH} = 2.73V$

Com $\frac{dV_o}{dV_i} = -1$ e $V_i = V_{TH}$:

$k_n (2V_o - V_{TH} + V_{TH}^m) = -k_p (V_{DD} - V_{TH} - V_{TH}^p) \Rightarrow V_o = \frac{1}{2} \left(1 + \frac{k_p}{k_n}\right) V_{TH} + \frac{1}{2} \left(\frac{k_p}{k_n} V_{TH}^p - V_{TH} - \frac{k_p}{k_n} V_{DD}\right)$

3.5)

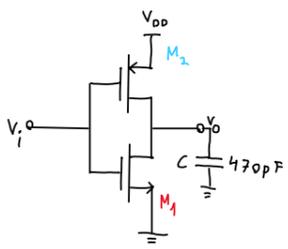

$$i_c = C \frac{dV_o}{dt} \Rightarrow \bar{i} \approx C \frac{\Delta V_o}{\Delta t} \Rightarrow \Delta t = \frac{C}{\bar{i}} \Delta V_o$$

$$\frac{d i_c}{d t} \approx 0 \Rightarrow i_c = \bar{i}$$

$$\Delta V_o = V_o(t_f) - V_o(t_i)$$

$$\bar{i} = \frac{i_c(t_f) + i_c(t_i)}{2}$$

$t_{pHL} \rightarrow M_1$ Condutiva
 M_2 corte

$$E_m t_i: \begin{cases} V_o(t_i) = V_{oH} = 5V \quad (V_{SD1} > V_{SD2} - V_{th}^m) \\ i_{D1}(t_i) = K_m (V_{oH} - V_{th}^m)^2 = 2.806 \text{ mA} \quad (M_1 \text{ Sat}) \end{cases}$$

$$\begin{aligned} \Delta V_o &= -2.5V \\ \bar{i} &= -2.754 \text{ mA} \Rightarrow t_{pHL} = 427 \text{ ns} \end{aligned}$$

Descarga!

$$E_m t_f: \begin{cases} V_o(t_f) = \frac{V_{oL} + V_{oH}}{2} = 2.5V \\ i_{D1}(t_f) = K_m \left[2(V_{oH} - V_{th}^m) \left(\frac{V_{oH} + V_{oL}}{2} \right) - \left(\frac{V_{oH} + V_{oL}}{2} \right)^2 \right] = 2.701 \text{ mA} \quad (M_1 \text{ Triodo}) \end{cases}$$

$t_{pLH} \rightarrow M_1$ corte
 M_2 Condutiva

$$E_m t_i: \begin{cases} V_o(t_i) = V_{oL} = 0 \quad (V_{SD2} > V_{SD1} - V_{th}^p) \\ i_{D2}(t_i) = K_p (V_{SD2} - V_{th}^p)^2 = K_p (V_{DD} - V_{oL} - V_{th}^p)^2 = 2.614 \text{ mA} \quad (M_2 \text{ Sat}) \end{cases}$$

$$\begin{aligned} \Delta V_o &= 2.5V \\ \bar{i} &= 2.537 \text{ mA} \Rightarrow t_{pLH} = 463 \text{ ns} \end{aligned}$$

Carga!

$$E_m t_f: \begin{cases} V_o(t_f) = \frac{V_{oL} + V_{oH}}{2} = 2.5V \\ i_{D2}(t_f) = K_p \left[2(V_{SD2} - V_{th}^p) (V_{SD2} - V_{oL}) - (V_{SD2} - V_{oL})^2 \right] = 2.460 \text{ mA} \quad (M_2 \text{ Triodo}) \end{cases}$$

$$t_p = \frac{t_{pHL} + t_{pLH}}{2} = 445 \text{ ns}$$

Equações simplificadas

$$t_{pHL} = \frac{C V_{th}^m}{k_m (V_{DD} - V_{th}^m)^2} + \frac{C}{2k_m (V_{DD} - V_{th}^m)} \ln \left(\frac{3V_{DD} - 4V_{th}^m}{V_{DD}} \right) = 420 \text{ ns}$$

$$t_{pLH} = \frac{C V_{th}^p}{k_p (V_{DD} - V_{th}^p)^2} + \frac{C}{2k_p (V_{DD} - V_{th}^p)} \ln \left(\frac{3V_{DD} - 4V_{th}^p}{V_{DD}} \right) = 453 \text{ ns}$$

$$\Rightarrow t_p = 436 \text{ ns}$$