
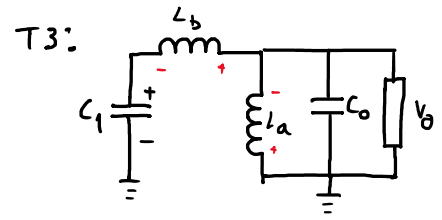
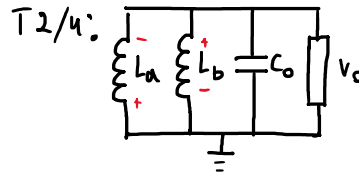
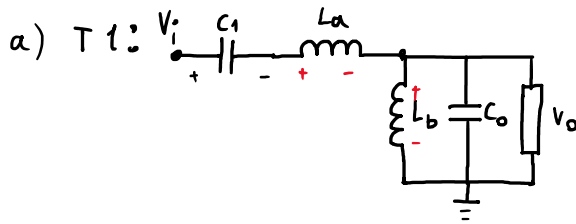


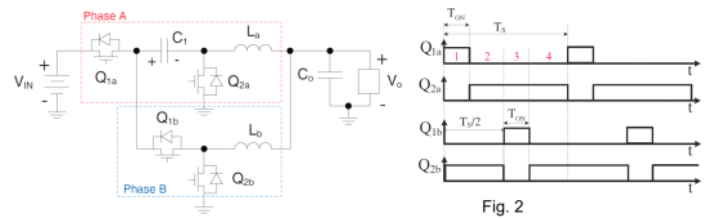1) The two-phase series capacitor buck converter shown in Fig. 1 operates in CCM at $f_{sw} = 1/T_s = 1\text{MHz}$. The switch driving waveforms are illustrated in Fig. 2.
a) Derive the DC voltage transfer function V_o/V_i as a function of D (assume the converter is lossless and the inductance values are matched (i.e. $L_a = L_b$)).
Assuming $V_i = 12\text{V}$, $V_o = 1.2\text{V}$, $P_o = 12\text{W}$:
b) calculate the average currents I_a and I_b .
c) Select the inductance values, L_a and L_b , such that the peak-to-peak current ripple is less than 20% of the average current.
d) Sketch a plot of the current flowing through C_1 as a function of time.
e) Select C_1 to ensure that the peak-to-peak voltage ripple is less than 0.3V .
f) Sketch a plot of the current flowing through L_a and L_b .
g) Calculate the peak-to-peak current ripple in C_o .
h) Calculate the peak-to-peak output voltage ripple ($C_o = 47\text{ }\mu\text{F}$, $\text{ESR} = 5\text{m}\Omega$).



$$L_a: (V_i - V_{C1} - V_o) D T_s - V_o \left(\frac{T_s}{2} - D T_s \right) 2 - V_o D T_s = 0 \Leftrightarrow$$

$$\Leftrightarrow V_i D - V_{C1} D - V_o D - V_o (1 - 2D) - V_o D = 0 \Leftrightarrow V_i D - V_{C1} D - V_o = 0$$

$$L_b: V_o D T_s + V_o \left(\frac{T_s}{2} - D T_s \right) 2 + (V_o - V_{C1}) D T_s = 0 \Leftrightarrow$$

$$V_o D + V_o (1 - 2D) + V_o D = V_{C1} D \Leftrightarrow V_{C1} = \frac{V_o}{D}$$

$$V_i D - 2V_o = 0 \Leftrightarrow \frac{V_o}{V_{im}} = \frac{D}{2}$$

b) $\frac{V_o}{V_{im}} = \frac{1.2}{12} = 0.1 \Rightarrow D = 0.2$


c) $V = L \frac{\Delta i}{\Delta t}$

$$I_o + I_b = I_a \quad I_a = \frac{I_o}{2} = 9\text{ A}$$

$$I_a: L > \frac{V_o D' T_s}{0.2 I_a} \Leftrightarrow L > 9.6 \mu\text{H}$$

$$C_1: I_a D = -I_b D \quad I_b = -I_a = \frac{I_o}{2} = -9\text{ A}$$
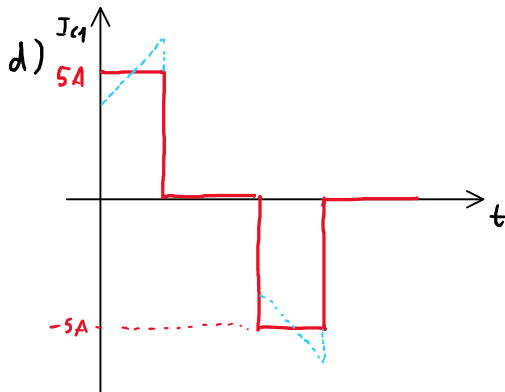
$$I_b: L > \frac{V_o D' T_s}{0.2 I_a} \Leftrightarrow L > 9.6 \mu\text{H}$$



e)


$$i = C \frac{\Delta V}{\Delta t} \Leftrightarrow \Delta V = \frac{I \Delta t}{C} \Leftrightarrow C > \frac{I \Delta t}{\Delta V} \Leftrightarrow C > \frac{I D T_s}{\Delta V}$$

$$C > 3.33 \mu\text{F}$$

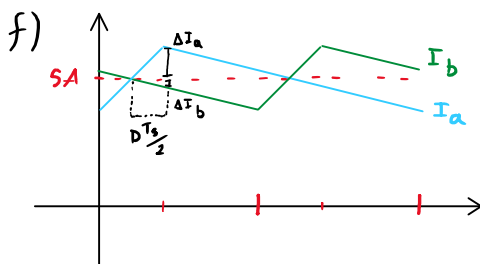g) $\frac{\Delta i_o}{2} = \Delta I_a - \Delta I_b \Leftrightarrow \Delta i = \frac{V_o (1 - 2D)}{L f_s} = 0.75\text{ A}$

$$\Delta I_a = (V_{in} - V_{C1} - V_o) \frac{D}{2} T_s \cdot \frac{1}{L}$$

$$\Delta I_b = V_o \frac{D}{2} T_s \cdot \frac{1}{L}$$



h) $\Delta V_o = \Delta V_C + \Delta V_{\text{ESR}}$

$$\Delta V_C = \frac{1}{2} \frac{T_s}{4} \cdot \frac{1}{C} \cdot \frac{\Delta i_o}{2} = \frac{\Delta I_o}{16 f_s C} = 1\text{ mV}$$

$$\Delta V_{\text{ESR}} = \Delta I_o \cdot \text{ESR} = 3.75\text{ mV}$$

2) The converter in Fig. 3 can be drawn in the electrically identical form shown in Fig. 4 ($q(t)=1$ when the switches are in position 1).

a) Use the circuit averaging method to derive a large-signal averaged model for this converter.
b) Perturb and linearize the averaged circuit model to obtain a small-signal ac equivalent circuit of the converter.

c) Derive the transfer function $G_{od}(s) = \frac{\tilde{v}_o}{\tilde{d}}$. Sketch the Bode plot of $|G_{od}(j\omega)|$.

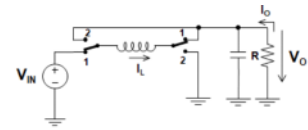


Fig. 3


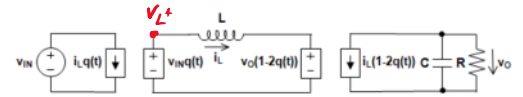



Fig. 4

$$\begin{aligned} \text{a)} \quad i_{IN} &= i_L q(t) & \text{Avg.} \quad \langle i_{IN} \rangle &= \langle i_L \rangle d(t) \\ V_L^+ &= V_{IN} q(t) & \langle V_L^+ \rangle &= \langle V_{IN} \rangle d(t) \\ V_L^- &= V_O (1 - 2q(t)) & \Rightarrow \quad \langle V_L^- \rangle &= \langle V_O \rangle (1 - 2d(t)) \\ i_O &= i_L (1 - 2q(t)) & \langle i_O \rangle &= \langle i_L \rangle (1 - 2d(t)) \end{aligned}$$

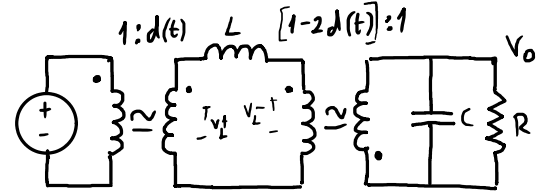


$$\begin{aligned} \text{b)} \quad \langle i_{IN} \rangle &= \langle i_L \rangle d(t) & I_{IN} + \tilde{i}_{IN} &= (I_L + \tilde{i}_L) (D + \tilde{d}) \\ \langle V_L^+ \rangle &= \langle V_{IN} \rangle d(t) & V_L^+ + \tilde{v}_L^+ &= (V_{IN} + \tilde{v}_{IN}) (D + \tilde{d}) \\ \langle V_L^- \rangle &= \langle V_O \rangle (1 - 2d(t)) & \Rightarrow \quad V_L^- + \tilde{v}_L^- &= (V_O + \tilde{V}_O) (1 - 2D - 2\tilde{d}) \\ \langle i_O \rangle &= \langle i_L \rangle (1 - 2d(t)) & I_O + \tilde{i}_O &= (I_L + \tilde{i}_L) (1 - 2D - 2\tilde{d}) \end{aligned}$$
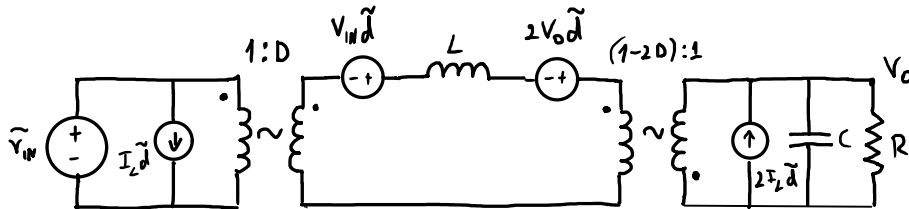
$$\begin{aligned} \text{DC:} \quad I_{IN} &= I_L D & \text{AC:} \quad \tilde{i}_{IN} &= I_L \tilde{d} + \tilde{i}_L D \\ V_L^+ &= V_{IN} D & \tilde{v}_L^+ &= V_{IN} \tilde{d} + \tilde{v}_{IN} D \\ V_L^- &= V_O (1 - 2D) & \tilde{v}_L^- &= \tilde{V}_O (1 - 2D) - V_O 2\tilde{d} \\ I_O &= I_L (1 - 2D) & \tilde{i}_O &= \tilde{i}_L (1 - 2D) - I_L 2\tilde{d} \end{aligned}$$


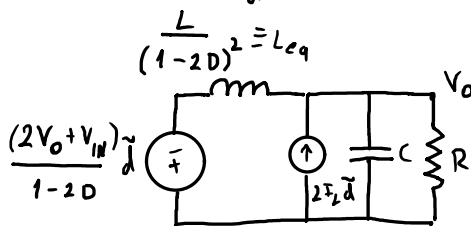
$$\text{c)} \quad G_{od}(s) = \frac{\tilde{v}_o}{\tilde{d}}$$



$$\begin{aligned} \frac{(-2V_O + V_{IN} \tilde{d} - \tilde{v}_O)}{L_{eq} s} + 2I_L \tilde{d} &= \tilde{i}_O \\ \tilde{v}_O = \tilde{i}_O (R // C) &= \frac{R}{1 + sRC} \tilde{i}_O \end{aligned}$$

$$\left(\frac{(-2V_O + V_{IN} \tilde{d} - \tilde{v}_O)}{L_{eq} s} + 2I_L \tilde{d} \right) \cdot \frac{R}{1 + sRC} = \tilde{v}_O$$

$$\tilde{d} \frac{2(1-2D)I_L L_{eq} s - 2V_O - V_{IN}}{(1-2D)L_{eq} s R} = \tilde{v}_O \frac{\Delta L_{eq} + s^2 R C L_{eq} + R}{L_{eq} s}$$

$$\frac{\tilde{v}_O}{\tilde{d}} = \frac{2(1-2D)I_L L_{eq} s - 2V_O - V_{IN}}{(1-2D)L_{eq} s R} \cdot \frac{L_{eq} s}{\Delta L_{eq} + s^2 R C L_{eq} + R} = -\frac{V_{IN} + 2V_O}{(1-2D)} \cdot \frac{1-2D}{s^2 C L_{eq} + s \frac{L_{eq}}{R} + 1}$$

$$\frac{V_0}{V_{IN}} = - \frac{V_{IN} + 2V_0}{(1-2D)} \cdot \frac{1 - 2\lambda L_{eq} I_L \frac{1-2D}{V_{IN} + 2V_0}}{\lambda^2 C L_{eq} + \lambda \frac{L_{eq}}{R} + 1}$$

$$\frac{V_0}{V_{IN}} = - \frac{V_{IN}}{(1-2D)^2} \cdot \frac{1 - 2\lambda L_{eq} \frac{1}{R} D}{\lambda^2 C L_{eq} + \lambda \frac{L_{eq}}{R} + 1}$$

$$\frac{V_0}{V_{IN}} = - \frac{V_{IN}}{(1-2D)^2} \cdot \frac{\left(1 - \frac{\lambda}{\omega_{HRPZ}}\right)}{\frac{\lambda^2}{\omega_o^2} + \lambda \frac{2g}{\omega_o} + 1}$$

$$V_0 = V_{IN} \frac{D}{1-2D}$$

$$I_L = \frac{V_0}{R} \frac{1}{1-2D}$$

$$\omega_{HRPZ} = \frac{R}{2L_{eq}D}$$

$$\omega_o = \sqrt{\frac{1}{CL_{eq}}}$$

$$g = \frac{1}{2R} \sqrt{\frac{L_{eq}}{C}}$$