

1) The DC/DC converter shown in Fig. 1 operates in CCM. The control signals applied to switches S1 and S2 are shown in Fig. 2. $V_O = 5\text{ V}$, $P_O = 100\text{ W}$; $V_{INmin} = 280\text{ V}$, $V_{INmax} = 340\text{ V}$, $f_{sw} = 250\text{ kHz}$.
a) Derive the DC voltage transfer function V_O/V_{IN} as a function of D .
b) Calculate the turn ratio n such that $D_{max} \leq 40\%$.
c) Draw a plot of i_{D1} , i_{D2} , i_L and i_{Lm} as a function of time (ignore the current ripple in L).
d) Calculate the minimum inductance value L to ensure CCM operation.
e) The output filter capacitor has the following specifications: $C = 220\text{ }\mu\text{F}$; $\text{ESR} = 35\text{ m}\Omega$. Select L such that the output voltage ripple is less than 1% of the nominal value.
f) Select L_m such that the maximum magnetizing current is less than 10% of the current through the ideal transformer primary.


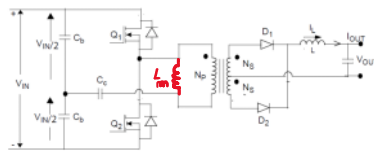
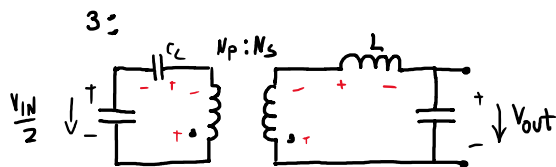
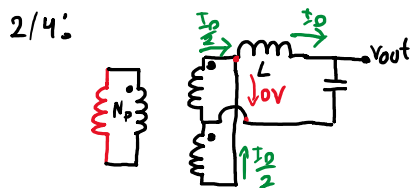
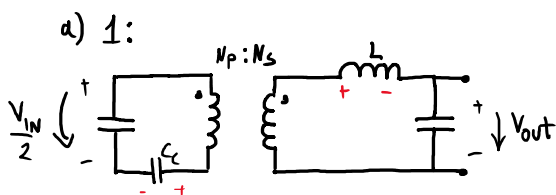


Fig. 1

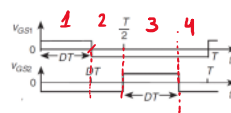

$$L: \left[\frac{N_s}{N_p} \left(\frac{V_{in}}{2} - V_c \right) - V_{out} \right] D + \left[\frac{N_s}{N_p} \left(\frac{V_{in}}{2} - V_c \right) - V_{out} \right] D - 2V_{out} \left(\frac{1}{2} - D \right) = 0$$

$$\left[\frac{N_s}{N_p} \left(\frac{V_{in}}{2} - V_c \right) - V_{out} \right] D - V_{out} \left(\frac{1}{2} - D \right) = 0$$

$$L_m: \left(\frac{V_{in}}{2} - V_c \right) D + \left(-\frac{V_{in}}{2} - V_c \right) D = 0 \Rightarrow V_c = 0$$

$$\left[\frac{N_s}{N_p} \frac{V_{in}}{2} - V_{out} \right] D - V_{out} \left(\frac{1}{2} - D \right) = 0 \Leftrightarrow \frac{V_o}{V_{in}} = D \frac{N_s}{N_p}$$

b) $D_{max} \leq 0.4$

$$\frac{V_o}{V_{in}} \frac{N_s}{N_p} \leq 0.4 \quad \text{worst case } V_{inmin} = 280$$

$$\frac{N_s}{N_p} \leq 0.4 \frac{V_{in}}{V_o} \Leftrightarrow \frac{N_s}{N_p} \leq 22.4 \Rightarrow m = \frac{N_s}{N_p} = 22$$

d) $\langle I_L \rangle \geq \frac{\Delta I_L}{2} \quad \langle I_L \rangle = I_o \quad \Delta I_L = \frac{V_o \left(\frac{1}{2} - D \right)}{L \cdot f_s}$

$$I_o \geq \frac{V_o \left(\frac{1}{2} - D \right)}{2 L \cdot f_s} \Leftrightarrow L \geq \frac{R_o \left(\frac{1}{2} - D \right)}{2 f_s} \quad R_o = 0.29 \Omega \quad f_s = 250 \text{ kHz}$$

$$L \geq 88.24 \text{ mH}$$

$$P_{min} = \frac{V_o}{V_{inM}} m = 0.32$$




e) $\Delta V_o = \Delta \text{ESR} + \Delta V_c$

$$\Delta \text{ESR} = \text{ESR} \cdot \Delta I_o \quad \Rightarrow \Delta V_o \leq \left(\text{ESR} + \frac{T_s}{16C} \right) \Delta I_o \Leftrightarrow$$

$$\Delta V_c = \frac{T_s}{4} \cdot \frac{1}{2} \cdot \frac{I_o}{2} \cdot \frac{1}{C} = \frac{T_s \Delta I_o}{16C} \Leftrightarrow \Delta I_o \geq \frac{0.01 V_o}{\text{ESR} + \frac{T_s}{16C}}$$

$$\Delta I_o \geq 1.38 \text{ A}$$
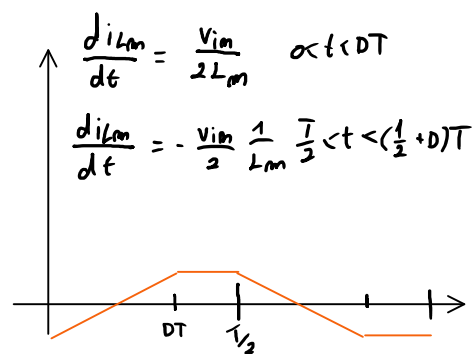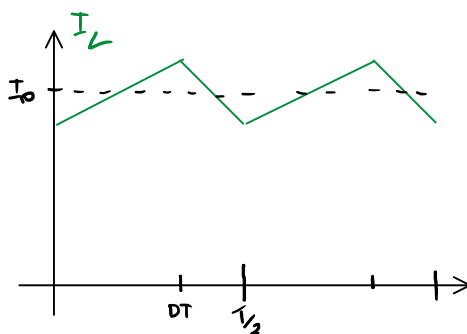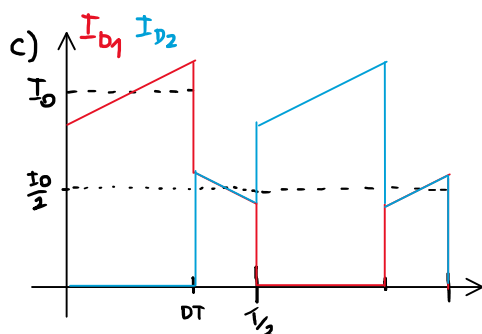
$$L \geq \frac{V_o \left(\frac{1}{2} - D \right)}{\Delta I_o f_s} \Leftrightarrow L \geq 2.6 \mu\text{H}$$



f) $\frac{V_{im}}{2L_m} \cdot \frac{DT_s}{2} = I_{Lmmax} \quad \frac{I_p}{I_s} = m \quad \frac{V_o}{V_{in}} = Dm \Leftrightarrow \frac{V_o}{m} = V_{in} D$

$$\frac{V_{im}}{2L_m} \cdot \frac{DT_s}{2} = 0.1 m I_o \Leftrightarrow \frac{10 V_o}{4 m^2 I_o} \leq L_m \Leftrightarrow L_m \geq 1.2 \text{ mH}$$

2) The DC-DC converter shown in Fig. 2 works at a switching frequency $f_{sw}=250$ kHz.
a) Draw a plot of the DC voltage transfer function V_o/V_{in} as a function of the duty cycle D , assuming that the inductors L and L_m work in CCM.
Given the following specifications: $V_{in} = 5V$, $V_o = 24V$, $P_o = 6W$.
b) Select the turn ratio n_2/n_1 such that $D=40\%$.
c) Select L such that the peak-to-peak current ripple is less than 25% of the average current.
d) Select L_m such that the inductor operates at the boundary CCM-DCM at $D=40\%$.
e) Select the capacitor C such that the voltage ripple (peak-to-peak) is less than 10% of the nominal voltage V_{C1} .
f) Calculate the peak-to-peak output voltage ripple ($C=470 \mu F$, $ESR=20m\Omega$).



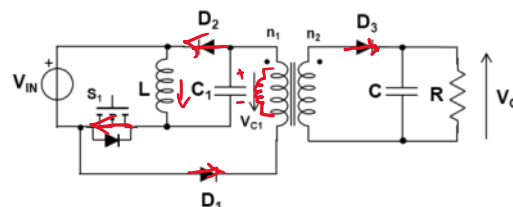


Fig. 2

ON

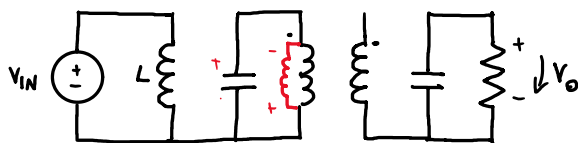

OFF

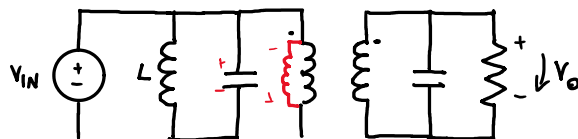

$$a) L: V_{in} D + V_{C1} (1-D) = 0$$

$$L_m: -V_{C1} D - V_o \frac{m_1}{m_2} (1-D) = 0$$

$$V_{C1} = -V_o \frac{m_1}{m_2} (1-D) / D \Rightarrow \frac{V_o}{V_{in}} = \frac{D^2}{(1-D)^2} \frac{m_2}{m_1}$$

$$b) D=0.4 \quad \frac{24}{5} \cdot \frac{(0.6)^2}{(0.4)^2} = \frac{m_2}{m_1} = 10.8$$

$$V_o = 24V$$

$$V_{in} = 5V$$

$$m = 11!$$

$$c) \Delta I_L \leq 0.25 \cdot \bar{I}_L \quad \Delta I_L = \frac{V_{in} D}{f_s L}$$

$$\frac{V_{in} D}{f_s L} \leq \frac{\bar{I}_L}{4D}$$

$$\bar{I}_L = \frac{I_{in}}{D}$$

$$\frac{4 \cdot V_{in} \cdot D^2}{f_s I_{in}} \leq L \Leftrightarrow L \geq 10.67 \mu H$$

$$d) D=0.4$$

$$\bar{I}_{Lm} = \frac{\Delta I_{Lm}}{2}$$

$$L \cdot 2 \bar{I}_{Lm} = V_o \frac{(1-D)}{m f_s} \Rightarrow L = 592.6 \mu H$$

$$\Delta I_{Lm} = V_o \frac{(1-D)}{m} \cdot \frac{1}{f_s L}$$

$$\bar{I}_{Lm} = \frac{1}{1-D} I_o \frac{m_2}{m_1} = 4.5 A$$


$$e) V_{in} D + V_{C1} (1-D) = 0 \Rightarrow V_{C1} = -\frac{V_{in} D}{1-D} = -3.33 V$$

$$i = C \frac{\Delta V}{\Delta t} \quad I_{Lm} \leq C \frac{0.1 V_{C1}}{D T_s} \Leftrightarrow C \geq \frac{D I_{Lm}}{0.1 V_{C1} T_s} \Leftrightarrow C \geq 21.6 \mu C$$


why the triangle in 9f?
ripple inductor?

$$f) \Delta V_o = \Delta ESR + \Delta V_C$$

$$\Delta ESR = ESR \cdot \Delta I_o$$

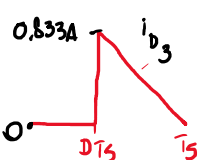

$$i_C = i_{D3} - i_o$$

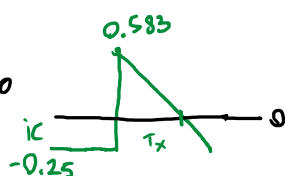

$$\frac{0.833}{(1-D) T_s} = \frac{0.5833}{T_x}$$

$$T_x = 1.68 \mu s$$

$$\Delta Q = \Delta I \cdot t_x = \frac{0.583 \cdot t_x}{2} = 490 nC$$

$$\Delta ESR = 20 m\Omega \cdot 0.833 A = 16.7 mV$$

$$\Delta V_o = \frac{\Delta Q}{C} = 1.04 mV$$