

a) Determine the ratio $I_{\text{ML}}/I_{\text{A}}$.
The load current is limited to the nominal value of 10 A by a "peak current-mode" controller operating at $f_{\text{SW}} = 200 \text{ kHz}$. The MOS switch is mounted on a heat sink ($R_{\text{thJC}} = 3.12 \text{ }^{\circ}\text{C/W}$, $R_{\text{thCA}} = 5 \text{ }^{\circ}\text{C/W}$, $T_{\text{A}} = 40 \text{ }^{\circ}\text{C}$).

b) Calculate the duty-cycle and the current ripple in the load.

c) Calculate the average junction temperature.

d) Due to a fault, the MOS switch sticks to the ON position. The current protection circuit ($I_{\text{MAX}} = 12\text{A}$) switches off the MOS after a delay of 30 ms. By using the thermal impedance curves shown in Fig. 4, calculate the maximum junction temperature at the end of the delay time.


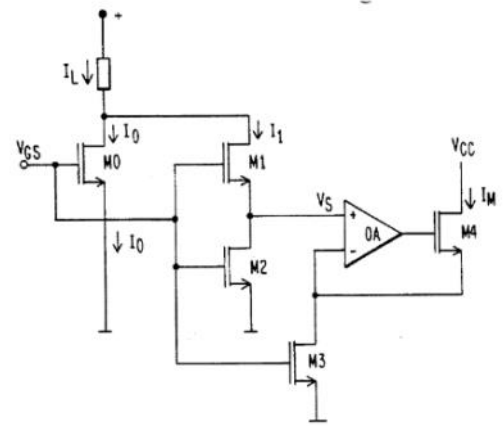


Fig. 1

a)

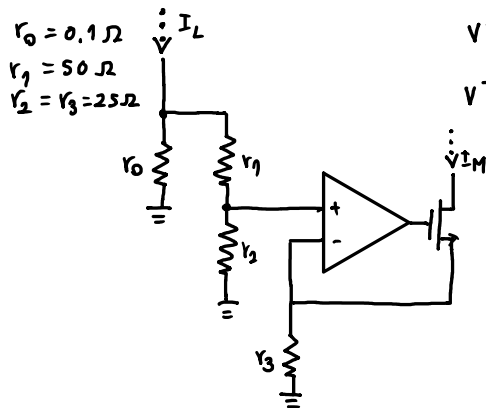

$$V^+ = r_2 \cdot I_1 = r_2 \cdot \frac{r_0}{r_0 + r_1 + r_2} \cdot I_L$$

$$V^- = r_3 \cdot I_M$$

$$r_3 \cdot I_M = r_2 \cdot \frac{r_0}{r_0 + r_1 + r_2} \cdot I_L$$

$$\frac{I_M}{I_L} = \frac{r_2}{r_3} \cdot \frac{r_0}{r_0 + r_1 + r_2} = 1.33 \times 10^{-3}$$


$$b) I_{L_{\max}} = 10 \text{ A} \quad (V_S - (R + r_0) I_L) D + R I_L (1-D) = 0 \Rightarrow D = \frac{R I_L}{V_S - r_0 I_L} = 0.652$$

$$\Delta i = \frac{R I_L \cdot (1-D)}{L f_s} = 26 \text{ mA}$$

$$c) P_{nos} = r_o I_L^2 D = 6.52 \text{ W}$$

$$T_j = T_A + P_{Mos} (R_{ojc} + R_{oca}) = 93^\circ C$$

d)

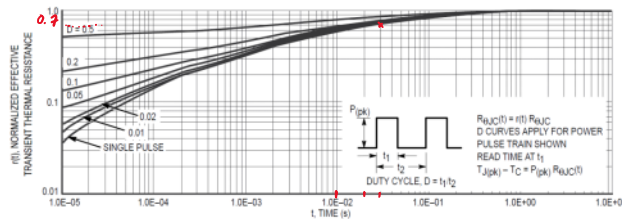

Step response $\tau = \frac{L}{R + r_{om}} = 0.625 \text{ s}$

$$t = 30 \text{ ns}$$

$t \gg \tau$ use $i(\infty) = \frac{V_S}{R + r_{in}} = 15 \text{ A}$

$$\Delta P = |P_{mos} - P_{max}| \approx 16W \Rightarrow \Delta T_j = \Delta P \cdot R_{thjc} \cdot \gamma(t_1 D) \approx 35^\circ C$$

$$T_{jmax} = T_{j0} + \Delta T_j = 93 + 35 = 128^\circ C$$

2) A solenoid valve ($L=0.3 \text{ mH}$; $R=1 \Omega$) is driven by a low-side switch ($r_{\text{ds(on)}} = 0.25 \Omega$) operating at a fixed frequency of 100 kHz (Fig. 2). The valve is activated by applying the current profile represented in Fig. 3. A "peak current mode" controller is used to limit the load current to the desired value.

a) Calculate the duty cycle of the switch in the time intervals T1 and T2 ($V_S=12\text{V}$, $V_D=1\text{V}$).

b) Calculate the average power dissipated by the power MOS in the time intervals T1 and T2.

Using the curves in Fig. 4:

c) calculate the junction temperature at the end of the time interval T1 ($R_{\text{thJC}} = 3.12 \text{ }^\circ\text{C/W}$; $T_C = 80 \text{ }^\circ\text{C}$);

d) calculate the junction temperature at the end of the time interval T2.

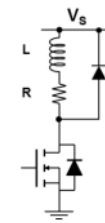


Fig. 2

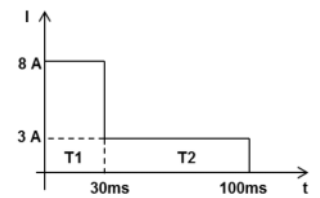


Fig. 3

a) Volt-Second balance L:

$$(V_S - I_L(R + r_{\text{ds(on)}}))D - (I_L R + V_D)(1-D) = 0 \quad D_{T1} = 0.818$$

$$(V_S - I_L(R + r_{\text{ds(on)}}) + I_L R + V_D)D = I_L R + V_D \Leftrightarrow D = \frac{I_L R + V_D}{V_S - I_L r_{\text{ds(on)}} + V_D} \quad D_{T2} = 0.327$$

$$b) P_{T1} = I_L^2 r_{\text{ds(on)}} D_{T1} = 13.1 \text{ W}$$

$$P_{T2} = I_L^2 r_{\text{ds(on)}} D_{T2} = 0.736 \text{ W}$$

$$c) T_j = T_C + P_{T1} R_{\text{thJC}} \cdot \gamma(30 \text{ ms}) = 108^\circ\text{C}$$

$$d) (T_j(100 \text{ ms}) - T_C) = \Delta T_{jC} = \left[P_1 \overbrace{\gamma(100 \text{ ms})}^{0.9} - P_1 \overbrace{\gamma(70 \text{ ms})}^{0.8} + P_2 \overbrace{\gamma(70 \text{ ms})}^{0.8} \right] R_{\text{th}} = 5.9^\circ\text{C}$$

$$T_j = 80 + 5.9^\circ\text{C} \approx 86^\circ\text{C}$$