

1) The current-fed push-pull converter shown in Fig. 1 is operating at $f_{sw}=500$ kHz (assume ideal switches, diodes and transformer).

a) Derive the DC transfer function V_o/I_{IN} assuming $n_1=n_2$.

Consider the following specifications: $I_{IN}=5$ A, $V_o=5$ V, $P_o=10$ W.

b) Calculate the duty-cycle D .

c) Sketch a plot of the current i_d as a function of time.

d) Calculate the peak-to-peak output voltage ripple ($C=470$ μ F, ESR = 10 m Ω).

e) Derive the transfer functions $G_{oc}(s) = \frac{\tilde{V}_o}{\tilde{V}_c}$, assuming $G_{PWM}(s)=1$ V $^{-1}$ (hint: perturb and linearize the average diode current $\langle i_d \rangle_{T_s}$). Sketch the Bode plot of $G_{oc}(s)$.

f) Determine the compensator transfer function, $G_c(s)$, such that the loop gain has a constant slope of -20 dB / dec, crossing the 0dB axis at $f_c = 50$ kHz.

g) Sketch the asymptotic plot of the closed-loop output impedance.

h) Sketch the transient response to a load step of 0.5A.



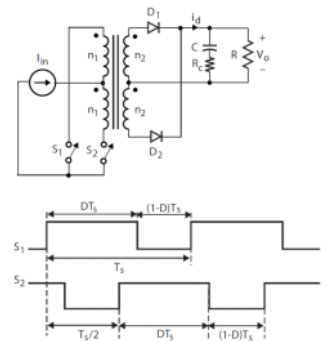


Fig. 1


a) S1 ON
S2 OFF

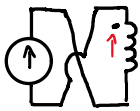

S1 OFF
S2 ON

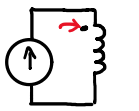


S1 ON
S2 ON

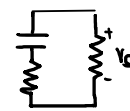

$$I_o = I_o = \frac{I_i (1-D) T_s + I_i (1-D) T_s}{T_s} \Leftrightarrow \frac{V_o}{R} = 2 I_i (1-D) \Leftrightarrow \frac{V_o}{I_i} = 2 R (1-D)$$

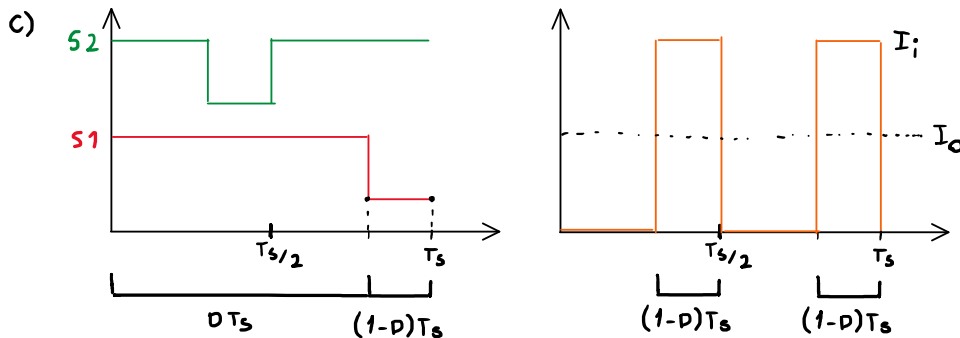b) $I_i = 5$ A
 $V_o = 5$ V $\Rightarrow I_o = 2$ A
 $P = 10$ W $\Rightarrow R = 2.5 \Omega$

$$1 - \frac{V_o}{2 \cdot R \cdot I_i} = D = 0.8$$



d)

$$\Delta V_o = \Delta V_c + \Delta ESR = 52.55 \text{ mV}$$

$$\Delta ESR = ESR \cdot \Delta I = 50 \text{ mV}$$

$$I = C \frac{\Delta V}{\Delta t} \Rightarrow \Delta V_c = \frac{(I_{im} - I_o)(1-D)}{f_s \cdot C} = 2.55 \text{ mV}$$


e) $I_d = 2 I_i (1-D)$

$$I_d + \tilde{i}_d = 2 (I_i + \tilde{i}_i) (1-D - \tilde{d})$$


$$I_d = 2 I_i (1-D)$$

$$\tilde{i}_d = 2 \tilde{i}_i (1-D) - 2 I_i \tilde{d}$$
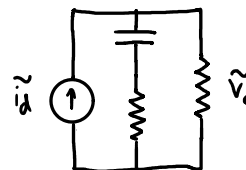
$$\frac{\tilde{i}_d}{\tilde{d}} = -2 I_i \Leftrightarrow \frac{\tilde{V}_o}{\tilde{d}} = -2 I_i \frac{R(1+D R C)}{1+D C(R+R_c)}$$


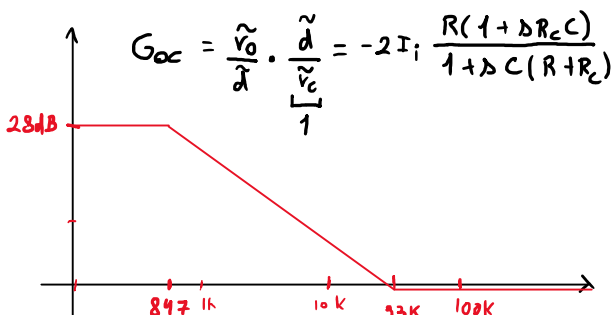
$$\frac{\tilde{V}_o}{\tilde{i}_d} = \frac{R(1+D R C)}{1+D C(R+R_c)}$$



$$|G_{oc}(0)| = 2 I_i R = 25 \approx 28 \text{ dB}$$

$$\omega_z = \frac{1}{R_c C} = 212 \text{ krad/s} = 33.9 \text{ kHz}$$

$$\omega_p = \frac{1}{C(R+R_c)} = 847 \text{ rad/s} = 135 \text{ Hz}$$



$$G_{oc} = -2I_i \frac{R(1+\beta R_c C)}{1+\beta C(R+R_c)} \quad L = \frac{\omega_c}{\Delta} \Rightarrow \frac{1}{1+L} = \frac{1}{1+\frac{\omega_c}{\Delta}} = \frac{\Delta/\omega_c}{\Delta/\omega_c + 1}$$

$$L = G_{oc} \cdot G_c \quad G_c = \frac{L}{G_{oc}} = \frac{1}{2I_i} \cdot \frac{\omega_c}{\Delta} \cdot \frac{1+\beta C(R+R_c)}{R(1+\beta R_c C)}$$

$$g) \quad Z_{ol} = \frac{Z_o}{1+L}$$

$$Z_o|_{ol} = R // (R_c + \frac{1}{\Delta C}) = \frac{R(1+\beta R_c C)}{1+\beta C(R+R_c)}$$

$$h) \quad I_{load} = 0.5 A$$

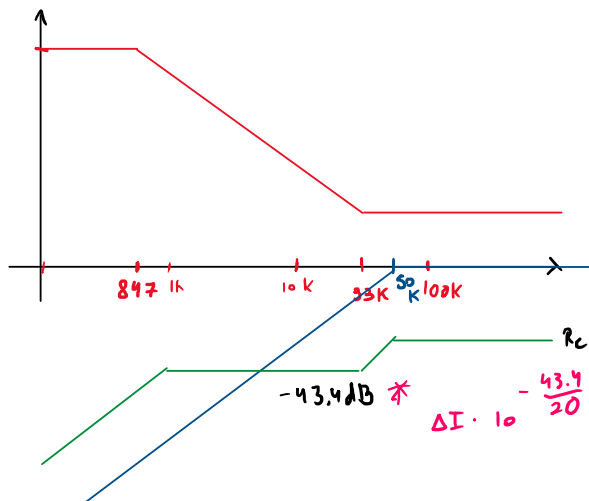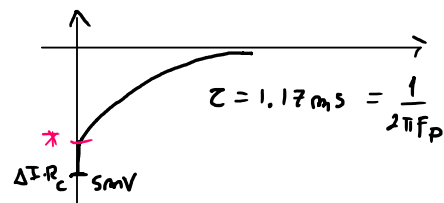

- 2) The Cuk converter in Fig. 2 operates in CCM at $f_{sw} = 250$ kHz. Consider the following specifications: $V_{IN} = 12V$, $V_O = 12V$, $P_O = 60W$; $L_1 = 54\mu H$; $L_2 = 27\mu H$; $C_1 = 22\mu F$; $C_2 = 100\mu F$. Ripples are small.
- Derive the DC voltage transfer function V_O/V_{IN} .
 - Calculate the average inductor currents I_{L1} and I_{L2} .
 - Calculate the peak-to-peak voltage ripple across C_1 .
- The output resistor is increased, pushing the converter toward the CCM/DCM boundary:
- Sketch a plot of i_D as a function of time at the CCM/DCM boundary (that is, $i_D(T_S) = 0$).
 - Calculate the boundary output power.
 - Show that the converter operates in DCM for $K < K_{crit}(D)$, where

$$K = \frac{2 \cdot L_1 // L_2}{R \cdot T_S} \quad \text{and} \quad K_{crit} = (1-D)^2$$

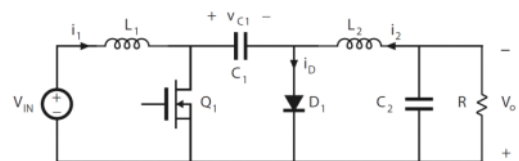



Fig. 2

$$a) \quad L_1: \quad V_{IN} D + (V_{IN} - V_{C1})(1-D) = 0 \Leftrightarrow V_{IN} = \frac{V_O}{D}(1-D) \Leftrightarrow \frac{V_O}{V_{IN}} = \frac{D}{1-D} \Rightarrow D = 0.5$$

$$L_2: \quad (V_{C1} - V_O)D - V_O(1-D) = 0 \Leftrightarrow V_{C1} = V_O/D$$

$$b) \quad \overline{I_{L1}} = I_{im} = 5A \quad c) \quad i = C \frac{dv}{dt} \Leftrightarrow \Delta V_{C1} = \frac{I_{im}(1-D)T_S}{C_1} = 0.45V$$

$$\overline{I_{L2}} = I_{out} = 5A$$

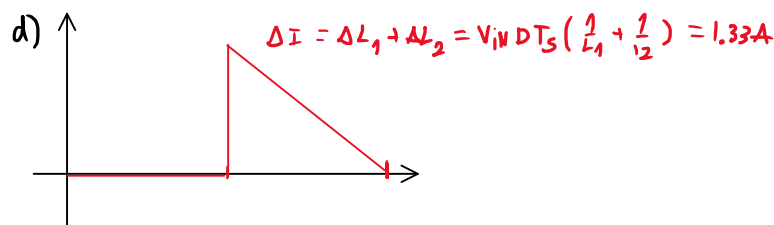

$$e) \quad P_O = P_{L1} + P_{L2} = (L_1 \cdot \Delta I_{L1}^2 + L_2 \cdot \Delta I_{L2}^2) \frac{f_{sw}}{2} = \left(\frac{V_{im}^2 D^2}{f_s^2 L_1} + \frac{V_{im}^2 D^2}{f_s^2 L_2} \right) \frac{f_{sw}}{2} = \frac{V_{im}^2 D^2}{f_s^2} \cdot \left(\frac{1}{L_1} + \frac{1}{L_2} \right) = 4W!$$

$$f) \quad \frac{V_{im} D}{2f_s L_1} + \frac{V_O(1-D)}{2f_s L_2} \geq \frac{P_O}{V_O} + \frac{P_O}{V_{im}} \Leftrightarrow \frac{V_O(1-D)}{f_s(L_1 // L_2)} \geq \frac{P_O}{R(1-D)} \Leftrightarrow (1-D)^2 \geq \frac{2(L_1 // L_2)}{R T_S}$$