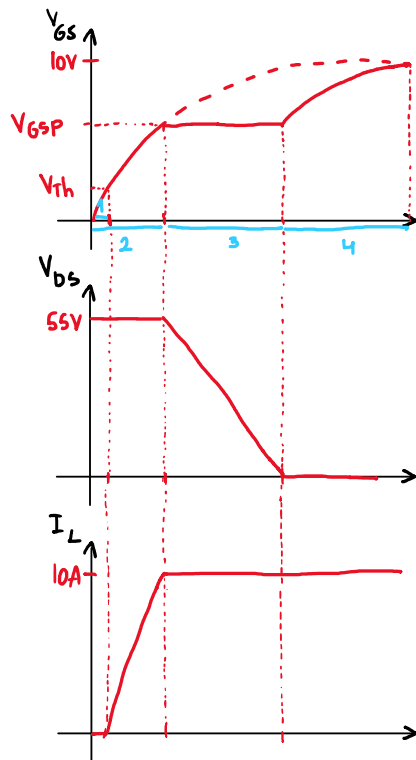


1) A low-side DMOS switch is used to drive a 10 A inductive load. The power MOSFET is driven by a MIC4428 biased at 10 V (Fig. 1). The MIC4428 driver has an output resistance, R_{out} of 6 Ω . Using the curves shown in Figures 2 and 3:

- a) calculate t_{ON} , t_{off} , t_{d} , t_{th} ($R_G = 33 \Omega$);
b) calculate the average switching loss in the power MOSFET transistor ($f_{sw} = 100 \text{ kHz}$);
c) calculate the driver loss.

a) T_{urm-ON}




$t_1 = t_{Th} = \text{Time to reach threshold voltage}$

$t_2 = t_{dom}$

$t_3 = t_r$

$t_4 = \text{Excess Charge Time}$

For t_{dom} equivalent circuit

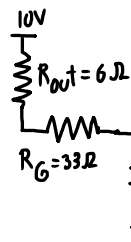

$$C_M = C_{iss} \big|_{V_{DS} = 55V} = 300 \text{ pF}$$

$$V_{GSP} = 7V$$

$$R_T = R_G + R_{out} = 39 \Omega$$

$$V_{C_{mos}} = V_{\infty} + (V_0 - V_{\infty}) e^{-t/2}$$

$$V_{GSP} = V_{DD} - V_{DD} e^{-t/C_M \cdot R_T} \Leftrightarrow$$


$$\Leftrightarrow t = C_M \cdot R_T \ln \left(\frac{V_{DD}}{V_{DD} - V_{GSP}} \right) = 14 \text{ ms}$$

$$Q = I \cdot t$$

$Q_p \rightarrow \text{Gate charge in plateau} \sim 5 \text{ nC}$

$$Q_p = I_G \cdot t_r \Leftrightarrow t_r = \frac{Q_p}{I_G} = \frac{Q_p \cdot R_T}{V_{DD} - V_{GSP}} = 65 \text{ ms}$$

For t_{doff} equivalent circuit

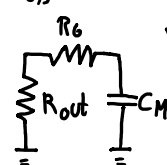

$$V_{GSP} = V_{DD} e^{t/2}$$

$$t_{doff} = C_M R_T \ln \left(\frac{V_{DD}}{V_{GSP}} \right) = 10 \text{ ms}$$

$$C_M = C_{iss} \big|_{V_{DS} = 0V} =$$

$$V_{GSP} = 7V$$

$$R_T = R_G + R_{out} = 39 \Omega$$

$t_1 = t_{doff}$

$t_2 = t_f$

$t_3 = t_d = \text{Discharge Time}$

$t_4 = t_{Th} = \text{Threshold Time}$

$$Q = I \cdot t$$

$$t_f = Q_p \cdot I_G = Q_p \cdot \frac{R_T}{V_{GSP}} = 28 \text{ ms}$$

$$t_{dom} = 14 \text{ ms}$$

$$t_{doff} = 10 \text{ ms}$$

$$t_r = 65 \text{ ms}$$



$$t_f = 28 \text{ ms}$$

other relevant times $V_{Th} = 4V$

$$t_{Thom} = t = C_M \cdot R_T \ln \left(\frac{V_{DD}}{V_{DD} - V_{Th}} \right) = 6 \text{ ms}$$

$$t_{dis} = t_d - t_{Thoff} = C_M \cdot R_T \ln \left(\frac{V_{GSP}}{V_{Th}} \right) = 6.5 \text{ ms}$$


$$C_M = C_{iss} \big|_{V_{DS} = 55V} = 300 \text{ pF}$$

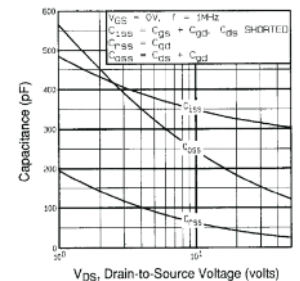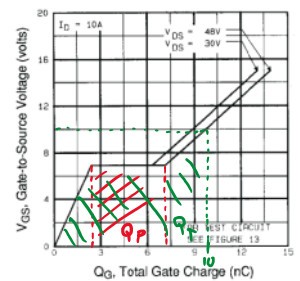

$$C_{iss} \big|_{V_{DS} = 0V} = \frac{\Delta Q}{\Delta V} = \frac{3 \text{ nC}}{4V} = 750 \text{ pF}$$

can be estimated using the gate charge

b) Turn-on

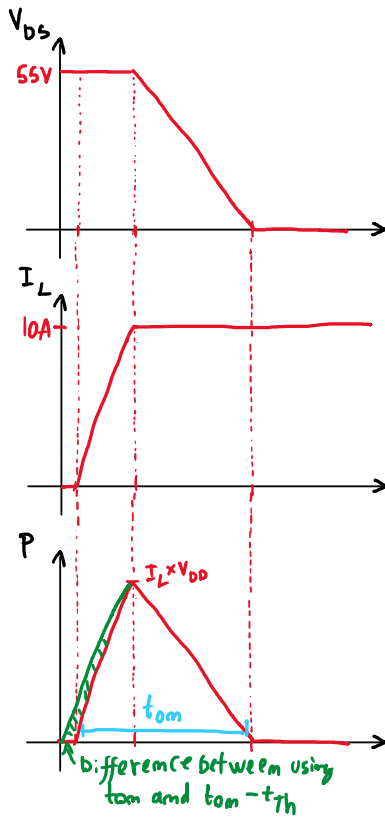

ON

With $t_{om} = t_{dom} + t_r = 82 \text{ ms}$

$$E_{ON} = t_{om} \cdot I_L \cdot V_{DD} \cdot \frac{1}{2} = 22.6 \mu\text{J}$$

With $t_{om} = t_{dom} + t_r - t_{TH} = 73 \text{ ms}$

$$E_{ON} = 20.1 \mu\text{J}$$


OFF

$$t_{off} = t_{dis} + t_f = 34.5 \text{ ms}$$

$$E_{OFF} = t_{off} \cdot I_L \cdot V_{DD} \cdot \frac{1}{2} = 9.5 \mu\text{J}$$

$$P_T = (E_{ON} + E_{OFF}) \cdot f_s = 29.6 \text{ mW}$$

Turn-off

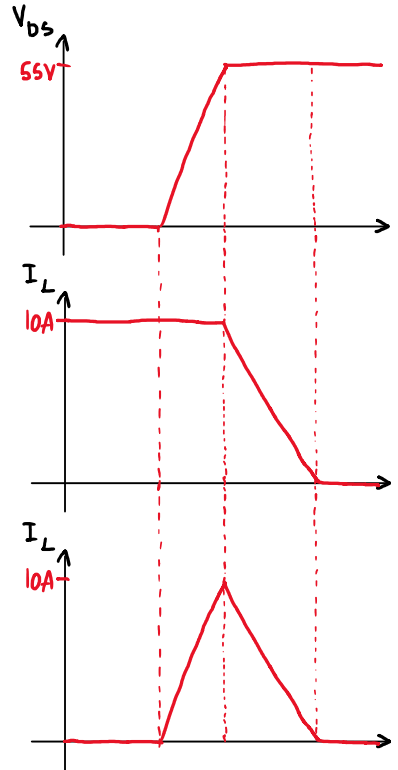

c) Driver loss $P_{DRV} = Q_T \cdot V_s \cdot f_s = 10 \text{ mW}$

$V_s = V_{G_{Max}}$ $Q_T \Rightarrow$ All the gate charge

- 2) The circuit shown in Figure 4 is used to drive a 10 A inductive load ($V_i = 5 \text{ V}$, $V_{BE(on)} = 0.8 \text{ V}$, $V_Z = 5.6 \text{ V}$, $R_1 = 130 \Omega$, $R_2 = 240 \Omega$, $f_{SW} = 10 \text{ kHz}$). The current gain of Q_2 is 150.
a) Using the curves shown in Figures 2 and 3 calculate t_{don} , t_{rise} , t_{doff} , t_{fall} .
b) Calculate the turn-on power loss assuming $V_{TH} = 4 \text{ V}$ and ideal freewheeling diode.
c) The freewheeling diode (STTH1202) has an abrupt recovery with $t_{rr} = t_b$ ($t_b \approx 0$). Using the curves in Fig. 5, calculate the additional power loss in the MOSFET due to the diode reverse recovery.


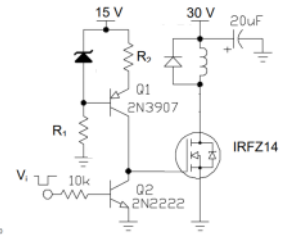
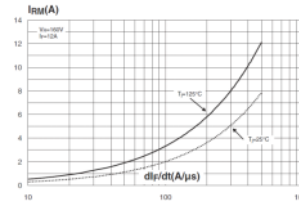


Fig. 4

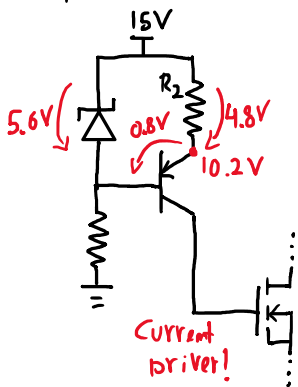a) ON

Equivalent ON circuit

With $V_{CE_{sat}} = 200 \text{ mV} \Rightarrow V_{GS_{max}} \approx 10 \text{ V}!$




$$I_E = \frac{V_{R_2}}{R_2} \approx I_C = 20 \text{ mA} \quad \text{Constant current}$$

$$Q = I \cdot t \Rightarrow t_{dom} = \frac{Q_1}{I_G} = \frac{2.3 \text{ mC}}{20 \text{ mA}} = 115 \text{ ms}$$

$$t_r = \frac{Q_P}{I_G} = \frac{4 \text{ mC}}{20 \text{ mA}} = 200 \text{ ms}$$

Equivalent OFF circuit

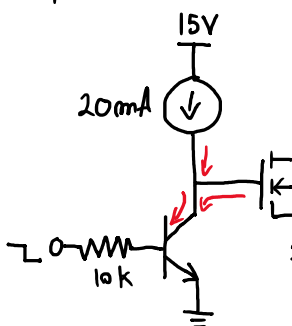

$$I_B = \frac{5 - 0.8}{10 \text{ k}} \text{ A} = 0.42 \text{ mA}$$

$$I_C = \beta I_B = 63 \text{ mA}$$

$$I_G = I_C - I_{Source} = 43 \text{ mA}$$

$$Q = I \cdot t \Rightarrow t_{doff} = \frac{Q_2}{I_G} = \frac{2.7 \text{ mC}}{43 \text{ mA}} = 63 \text{ ms}$$


$$t_f = \frac{Q_P}{I_G} = 93 \text{ ms}$$

b) Turn-on

$$P = (t_{dom} + t_r) \cdot I_L \cdot V_{DD} \cdot \frac{1}{2} \cdot f_s = 0.47 \text{ W}$$



$$P = (t_{dom} + t_r - t_{TH}) \cdot \frac{I_L V_{DD}}{2} f_s = 0.36 \text{ W} \quad \text{More Correct}$$
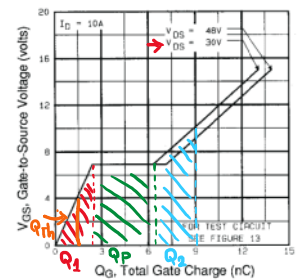
$$t_{TH} = \frac{Q_{TH}}{I_{G_{on}}} = \frac{1.5 \text{ mC}}{20 \text{ mA}} = 75 \text{ ms}$$



c)

With Reverse Recovery

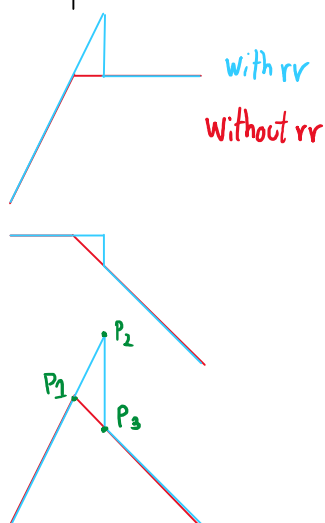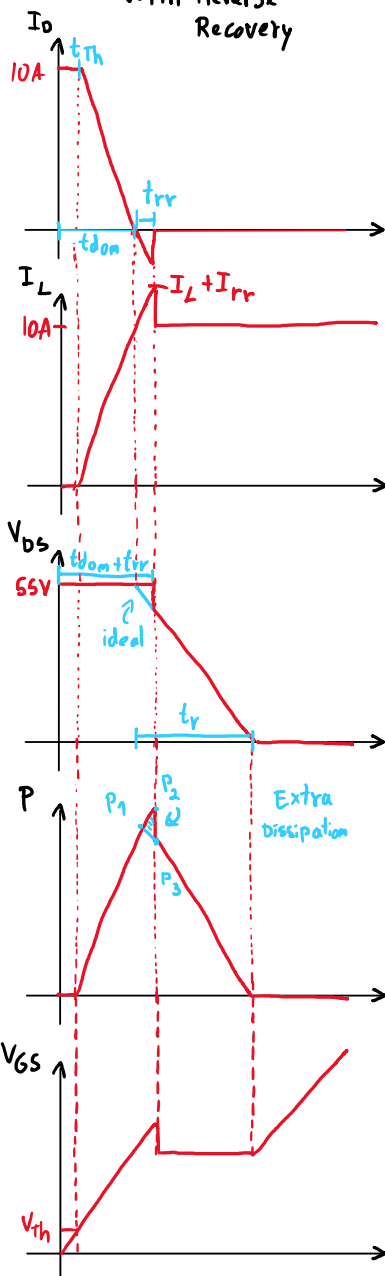

$$P_1 = V_{DD} \cdot I_L = 300W$$


$$P_2 = V_{DD} \cdot (I_L + I_{RR}) = 442.5W$$

$$P_3 = P_1 - \frac{dP}{dt} \cdot t_{RR} = 271.5W$$

$$\frac{dP}{dt} = \frac{P_1}{t_r} = 1.5W/ms$$

$$E_{Dis} = \frac{(P_2 - P_3) \times t_{RR}}{2} = 1.6\mu J$$
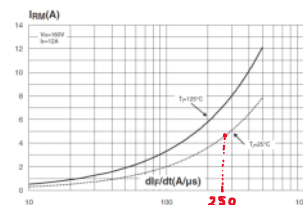
$$P_{Dis} = E_{Dis} \times f_s = 16mW //$$



$$\Rightarrow I_{RR} = 4.75A$$

$$\frac{dI_F}{dt} = \frac{I_L}{t_{dom}} = \frac{10}{40m} = 250A/\mu s$$

$$t_{RR} = \frac{I_{RR}}{\frac{dI_F}{dt}} = 19ms \Rightarrow Q_{RR} = 45mC$$

Less accurate alternative

$$P = Q_{RR} \cdot V_{DD} \cdot f_{sw} = 13.5mW$$