

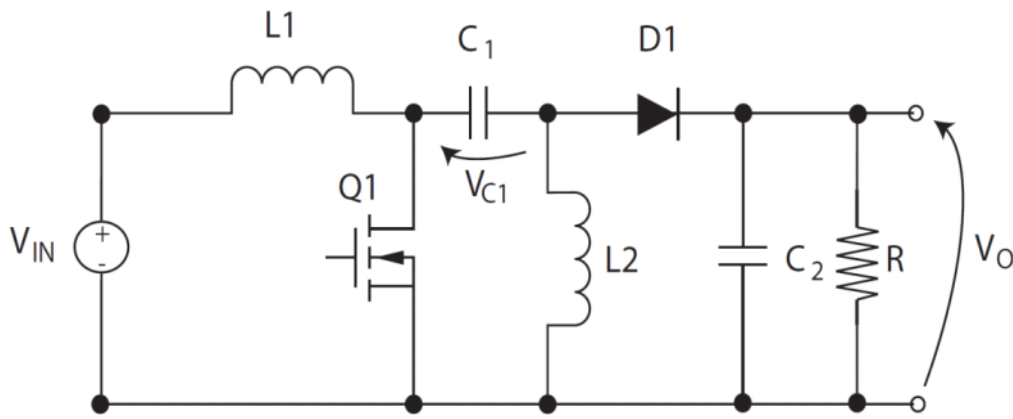


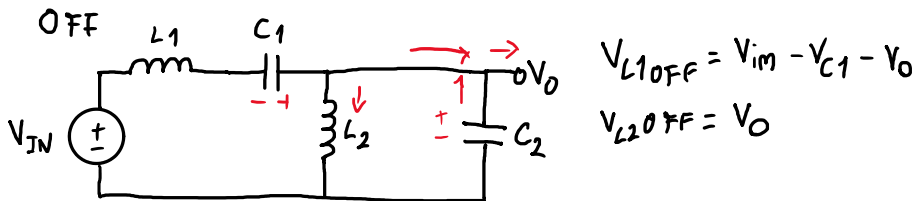

1) The DC-DC converter shown in Figure 1 operates in CCM.

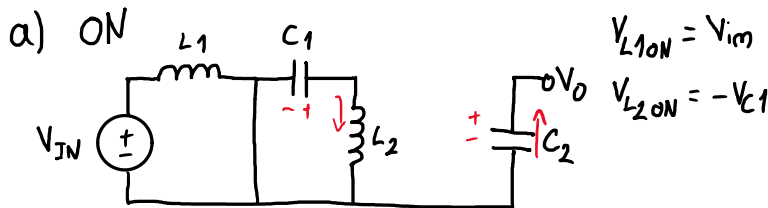a) Derive the DC voltage transfer function V_O/V_{IN} as a function of the duty cycle D (ignore the voltage ripple across the capacitor C_1).



$$\begin{aligned}
 L_1 &\Rightarrow V_{im} \cdot D \cdot T_s + (V_{im} - V_{C1} - V_O) \cdot (1-D) \cdot T_s = 0 \\
 L_2 &\Rightarrow -V_{C1} \cdot D \cdot T_s + V_O \cdot (1-D) \cdot T_s = 0
 \end{aligned}
 \Leftrightarrow \begin{cases} V_{im} \cdot D + (V_{im} - V_{C1} - V_O) \cdot (1-D) \\ \frac{V_O \cdot (1-D)}{D} = V_{C1} \end{cases}$$

$$\Leftrightarrow \begin{cases} V_{im} D + (V_{im} - \frac{V_O(1-D)}{D} - V_O) \cdot (1-D) = 0 \\ - \end{cases}$$

$$\Rightarrow V_{im} - V_O(1-D) \left(\frac{1-D}{D} + 1 \right) = 0 \Leftrightarrow V_{im} = V_O(1-D) \cdot \frac{1}{D} \Leftrightarrow \frac{V_O}{V_{im}} = \frac{D}{1-D}$$

Assuming $V_{IN} = 12V$, $V_O = 5V$, $L_1 = L_2 = 500 \mu H$, $C_1 = 4.7 \mu F$, $P_O = 10 W$, $f_{SW} = 250kHz$:

b) Calculate the average current in the inductors L_1 and L_2 .

$$V_{im} = 12 \text{ and } V_O = 5 \Rightarrow D = \frac{V_O}{V_O + V_{im}} = 0.294$$

$$P_O = 10W \Rightarrow I_O = 2A \Rightarrow \frac{I_{im}}{I_O} = \frac{V_O}{V_{im}} = \frac{D}{1-D} \leadsto I_{im} = 0.833A$$

Amp sec balance

$$I_{C2ON} = I_O \quad I_{C2OFF} = I_O - I_{im} - I_{L2}$$

$$I_{C1ON} = -I_{L2} \quad I_{C1OFF} = I_{im} \leadsto -I_{L2} \cdot D \cdot T_s + I_{im} \cdot (1-D) \cdot T_s = 0 \Rightarrow I_{L2} = \frac{I_{im}(1-D)}{D} = I_O = 2A$$

$$I_{L1} = I_{im} = 0.833A$$


c) Calculate the peak-to-peak current ripple in L_1 and L_2 .

$$V = L \frac{\Delta i}{\Delta t} \quad \text{ON } \nearrow$$

$$V_{L1\text{ON}} = V_{\text{in}} \Rightarrow \Delta i_{L1} = \frac{V_{\text{in}}}{L_1} \cdot D \cdot \frac{1}{f_s} = 28.24 \text{ mA}$$

$$V_{L2\text{OFF}} = V_o \Rightarrow \Delta i_{L2} = \left| \frac{V_o}{L_2} \cdot (1-D) \cdot \frac{1}{f_s} \right| = 28.24 \text{ mA}$$

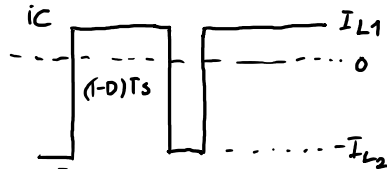d) Calculate the peak-to-peak voltage ripple across C_1 .



$$\Delta V_{C1} = \frac{I_{L2} D T_s}{C_1} = 0.5 \text{ V}$$

If the ripple from L_1 and L_2 is considered: $\Delta V_{C1} = 500 \text{ mV} + 3 \text{ mV} = 503 \text{ mV}$

Current in $C_1 \rightarrow$ Triangle $\Rightarrow$ Voltage $\rightarrow$ weird time $\nearrow \Delta V = \frac{1}{C} \Delta Q!$

$$i = C \frac{dv}{dt} \Rightarrow \Delta V = \frac{1}{C} \int i dt \quad \xrightarrow{\text{Area of the current}} \quad \Delta V = \frac{1}{C} \cdot \frac{T_s}{2} \cdot \frac{\Delta i_{L2}}{2} \cdot \frac{1}{2} \quad \xrightarrow{\Delta Q} \quad \Delta V = \frac{\Delta i_{L2} \cdot T_s}{8C} = 3 \text{ mV}$$

e) Calculate the peak-to-peak output voltage ripple ($C = 470 \mu\text{F}$, $\text{ESR} = 25 \text{ m}\Omega$).

$$I_{C2\text{ON}} = I_o \quad I_{C2\text{OFF}} = I_o - I_{\text{im}} - I_{L2} = -I_{\text{im}}$$

$$V_{\text{ESR}_{\text{ON}}} = \text{ESR} \cdot I_o \quad V_{\text{ESR}_{\text{OFF}}} = -\text{ESR} \cdot I_{\text{im}} \Rightarrow \Delta V_{\text{ESR}} = \text{ESR} (I_{\text{im}} + I_o)$$

$$\Delta V_{C2} = \frac{I_o D \cdot T_s}{C} + \Delta V_{\text{ESR}} = \frac{I_o D \cdot T_s}{C} + \text{ESR} (I_{\text{im}} + I_o) \Rightarrow 76 \text{ mV}$$