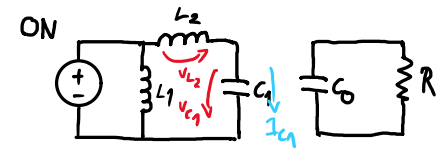



1) The DC/DC converter shown in Fig. 1 operates in CCM. The switches S1 and S2 are driven synchronously (both ON or OFF). All the components are ideal: losses may be ignored.

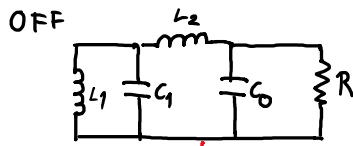a) Derive the DC voltage transfer function V_O/V_{IN} as a function of D and sketch its plot.



$$V_{in} \cdot D \cdot T_s + V_{C1} (1-D) \cdot T_s = 0$$

$$(V_{in} - V_{C1})D - (V_O - V_{C1})(1-D) = 0$$



$$V_{C1} = -\frac{V_{in} D}{1-D}$$

$$(V_{in} + \frac{V_{in} D}{1-D})D - (V_O + \frac{V_{in} D}{1-D})(1-D) = 0$$

$$V_{in} (D + \frac{D^2}{1-D}) - V_O (1-D) - V_{in} D = 0 \Rightarrow \frac{V_O}{V_{in}} = \frac{D^2}{(1-D)^2}$$

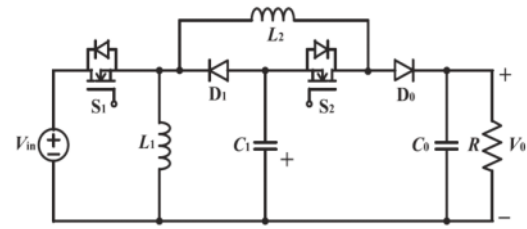
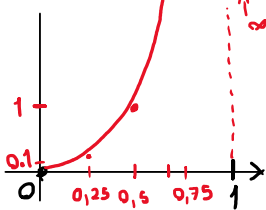


Fig. 1

b) Derive expressions for the average currents I_{L1} , I_{L2} as a function of D and I_O .

$$P_{in} = P_{out} \Leftrightarrow V_{in} \cdot I_{in} = V_O \cdot I_O \Rightarrow I_{in} = \frac{V_O}{V_{in}} I_O$$

$$I_{C1} \cdot D = (I_{L2} - I_O) (1-D) \Leftrightarrow I_O D + I_O (1-D) = I_{L2} (1-D) \Rightarrow I_{L2} = \frac{I_O}{1-D}$$

$$I_{in} = (I_{L1} + I_{L2}) D \Rightarrow \frac{D^2}{(1-D)^2} I_O = I_{L1} D + I_O \frac{D}{1-D} \Leftrightarrow \frac{2D-1}{(1-D)^2} I_O = I_{L1}$$

Assuming $V_{IN} = 1.5V$, $V_O = 48V$, $P_O = 10W$, $f_{sw} = 300 \text{ kHz}$:

c) Select L_1 and L_2 such that peak-to-peak current ripple is less than 20% of the average current.


$$\frac{V_O}{V_{in}} = \frac{D^2}{(1-D)^2} \Rightarrow D = \frac{\sqrt{V_O/V_{in}}}{1 + \sqrt{V_O/V_{in}}} = 0.85 \quad I_O = 0.208A \Rightarrow I_{L1} = 6.471A \quad V_{C1} = -3.5V$$

$$\hookrightarrow I_{L2} = 1.387A$$

$$\frac{V}{L_1} = \frac{\Delta i}{\Delta t} \Rightarrow \frac{V_{in} \cdot D \cdot 1/f_{sw}}{L_1} < 0.2 I_{L1} \Leftrightarrow L_1 > \frac{V_{in} \cdot D \cdot 1/f_{sw}}{0.2 I_{L1}} \Leftrightarrow L_1 > 3.3 \mu H$$

$$\frac{V}{L_2} = \frac{\Delta i}{\Delta t} \Rightarrow \frac{(V_{in} - V_{C1}) D \cdot 1/f_{sw}}{0.2 I_{L2}} < L_2 \Leftrightarrow L_2 > 102.1 \mu H$$

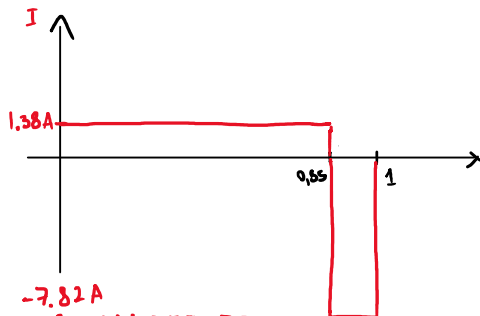d) Sketch a plot of the current flowing through C_1 as a function of time (neglect the current ripple in L_1 and L_2).



For on $I_{C1} = I_{L2}$
 For off


$$I_{C1} = -\frac{0.85 \times 1.38}{1 - 0.85} = -7.82A$$

e) Select C_1 to ensure that the peak-to-peak voltage ripple is less than 0.3V.

$$\frac{i}{C} = \frac{\Delta V}{\Delta t} \Rightarrow \Delta V < \frac{i \Delta t}{C} \Rightarrow C < \frac{i \Delta t}{\Delta V} \quad I_{L2} = 1.387 \text{ A}$$

$$\frac{I_{L2} \cdot D \cdot \frac{1}{f_{sw}}}{0.3} \geq C \Leftrightarrow C \leq 13.1 \mu\text{F}$$

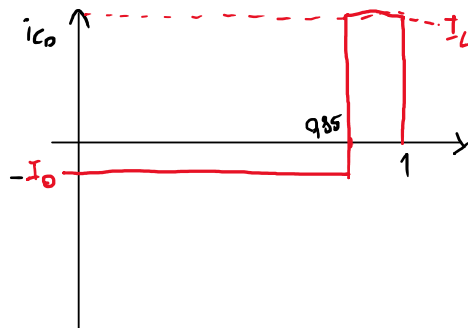f) Calculate the peak-to-peak output voltage ripple ($C = 910 \mu\text{F}$, $\text{ESR} = 25 \text{ m}\Omega$).



$$I_{L2} - I_o = 1.179 \text{ A}$$

$$I_o = 0.208$$


$$\Delta V = \frac{I_o \cdot D \cdot \frac{1}{f_{sw}}}{C} + \text{ESR} \cdot (I_{L2}) =$$

$$= 0.65 \text{ mV} + 34.7 \text{ mV} = 35.35 \text{ mV}$$

2) The DC/DC converter shown in Fig. 2 operates in CCM. The switches S1 and S2 are driven synchronously (both ON or OFF). All the components are ideal: losses may be ignored. Assume $V_{IN} = 12V$, $D = 0.63$, $R = 2\Omega$, $f_{sw} = 300$ kHz.

a) Derive the DC voltage transfer function V_O/V_{IN} as a function of D and sketch its plot.

ON:

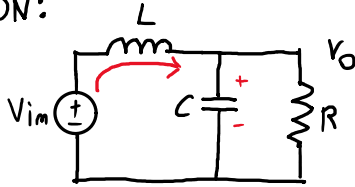

OFF:

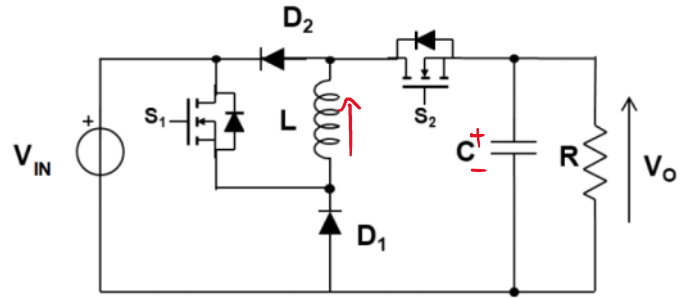
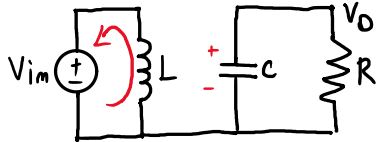



Fig. 2

$$V_O = 0.413 \cdot V_{im} = 4.95 V$$

$$I_O = \frac{V_O}{R} = 2.475 A$$

$$(V_{im} - V_O) D T_s - V_{im} (1-D) T_s = 0 \Leftrightarrow (V_{im} - V_O) D = V_{im} (1-D) \Leftrightarrow$$
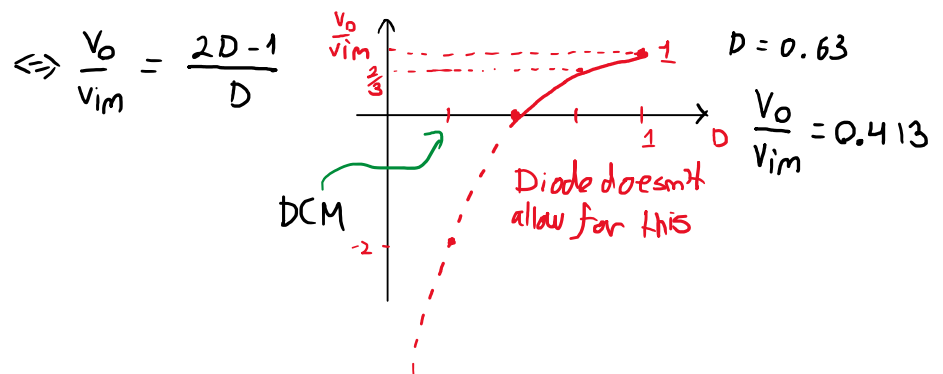
$$\Leftrightarrow V_{im} D - V_{im} (1-D) = V_O D \Leftrightarrow V_{im} (D - 1 + D) = V_O D \Leftrightarrow$$



b) Derive an expression for the conditions under which this converter operates in CCM. Express your result in the form $K > K_{crit}(D)$, and give an expression for $K_{crit}(D)$.

$$\Delta i = \frac{V}{L} \Delta t = \frac{V_{im}}{L} (1-D) T_s \Rightarrow I_{LB} = \frac{V_{im} (1-D) T_s}{2L} = \frac{V_O D (1-D) T_s}{2L(2D-1)}$$

$$\text{charge balance: } (I_L - I_O) D T_s - I_O (1-D) T_s = 0$$

$$I_L D = I_O D + I_O - I_O D \Rightarrow I_L D = I_O$$


$$\text{CCM if } I_L > I_{LB} \Rightarrow \frac{I_O}{D} > I_{LB}$$

$$\frac{I_O}{D} > \frac{V_O D (1-D) T_s}{2L(2D-1)} \Leftrightarrow \frac{2L}{R_o T_s} > \frac{D^2 (1-D)}{2D-1} \quad K_{crit}(D) = \frac{D^2 (1-D)}{2D-1}$$

c) Calculate the minimum inductance value such to ensure CCM operation.

$$L_{min} = \frac{R_o T_s D^2 (1-D)}{2(2D-1)} = 1.88 \mu H$$

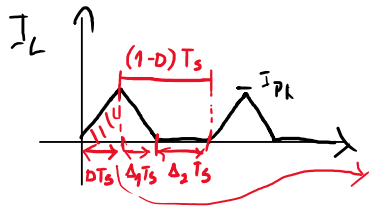d) Assume $L < L_{\min}$. Derive an expression for the DC voltage transfer function V_O/V_{IN} of the converter operating in DCM.



$$\frac{V_{im} - V_O}{L} \cdot DT_s = \frac{V_{im} \Delta_1 T_s}{L} \Leftrightarrow \Delta_1 = \frac{V_{im} - V_O}{V_{im}} D = D \cdot \left(1 - \frac{V_O}{V_{im}}\right)$$

Since $\bar{I}_C = 0$ then $\Rightarrow \bar{I}_O = \bar{I}_{s2} = \frac{I_{pk} \cdot D \cdot T_s}{2} = \frac{V_{im} \Delta_1 T_s}{2L} \cdot D$

$$\frac{V_O}{R} = \bar{I}_O = \frac{V_{im} T_s D^2}{2L} \left(1 - \frac{V_O}{V_{im}}\right) \Rightarrow \frac{V_O}{V_{im}} = \frac{D^2}{K} \cdot \frac{1}{\left(1 + \frac{D^2}{K}\right)}$$

e) Calculate the output voltage V_O assuming $L = 0.5 \mu\text{H}$.

$$L = 0.5 \mu\text{H}$$

$$K = \frac{2L}{R T_s}$$

$$V_O = \frac{D^2}{K} \cdot \frac{1}{\left(1 + \frac{D^2}{K}\right)} \cdot V_{im} = 8.7 \text{ V}$$