

1) The DC/DC converter shown in Fig. 1 operates in CCM. The switches are in position 1 for $0 < t < DT_s$ and in position 2 for $DT_s < t < T_s$. Assume that all components are ideal.
a) Derive the expression of V_O/V_{IN} as a function of D and sketch its plot.

$$L(V_S - V_O)D + L(V_S + V_O)(1-D) = 0$$

$$V_S D - V_O D + V_S - V_S D + V_O - V_O D = 0$$

$$V_S = (2D - 1)V_O$$

$$\frac{1}{2D-1} = \frac{V_O}{V_S}$$

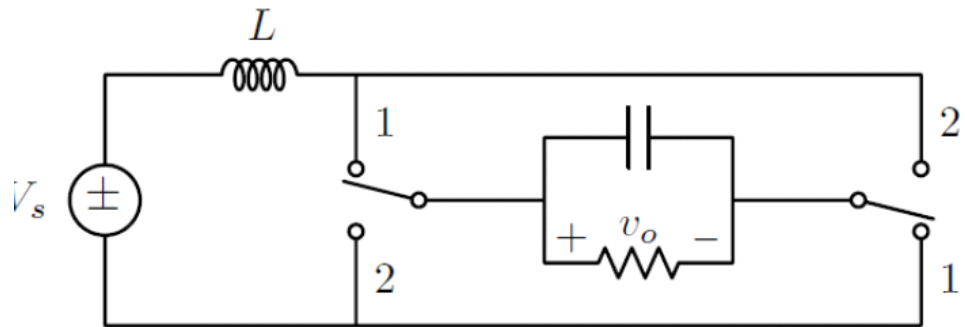


Fig. 1

Assuming $V_{IN} = 2.5V$, $D = 0.75$, $R = 5\Omega$, $f_{sw} = 1.5 \text{ MHz}$:

b) Calculate the output voltage, V_O .

$$\frac{1}{2 \cdot 0.75 - 1} \cdot 2.5 = V_O = 5V$$

c) Select L such that the peak-to-peak current ripple is 30% of the nominal current.


$$I_L = I_{im} \quad P_{im} = P_O = V_O I_O = \frac{V_O^2}{R} \Rightarrow I_L = \frac{V_O^2}{V_{in} R} = 2A$$

$$V = L \frac{\Delta i}{\Delta t} \quad \frac{(V_S - V_O)DT_s}{L} \leq 0.3 I_L \Rightarrow \frac{|V_S - V_O|DT_s}{0.3 I_L} \leq L \Rightarrow L \geq 2.083 \mu H$$

d) Calculate the peak-to-peak output voltage ripple (the ESR can be neglected).


$$I = C \frac{\Delta V}{\Delta t} \Rightarrow \frac{(I_1 - I_O)DT_s}{C} = \Delta V = \dots ?$$

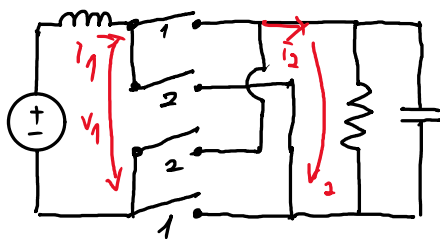e) Show that the converter of Fig. 1 can be drawn in the electrically identical form shown in Fig. 2. Sketch the waveforms $v_1(t)$ and $i_2(t)$. Use the circuit averaging method to derive a large-signal averaged model for this converter.



$$i_2(t) = i_1 q(t) - i_1 (1 - q(t)) = i_1 (2q(t) - 1)$$
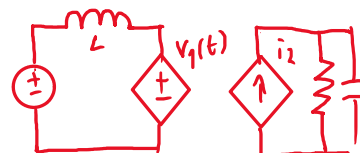
$$v_1(t) = v_2 q(t) - v_2 (1 - q(t)) = v_2 (2q(t) - 1)$$



$$\bar{v}_1(t) \cong \bar{v}_2(t) (2d(t) - 1)$$


$$\bar{i}_2(t) \cong \bar{i}_1(t) (2d(t) - 1)$$

f) Perturb and linearize the averaged circuit model to obtain a small-signal ac equivalent circuit of the converter.

g) Derive the transfer function $G_{oc}(s) = \frac{\tilde{V}_o}{\tilde{V}_{in}}$ (assume $G_{PWM}=1 \text{ V}^{-1}$). Sketch the Bode plot of $|G_{oc}(j\omega)|$.


Perturb
$$\begin{aligned} V_1 + \tilde{v}_1 &= (V_2 + \tilde{v}_2)(2(D + \tilde{d}) - 1) & V_1 + \tilde{v}_1 &= V_2(2D - 1) + 2V_2\tilde{d} + \tilde{v}_2(2D - 1) \\ I_2 + \tilde{i}_2 &= (I_1 + \tilde{i}_1)(2(D + \tilde{d}) - 1) & I_2 + \tilde{i}_2 &= I_1(2D - 1) + 2I_1\tilde{d} + \tilde{i}_1(2D - 1) \end{aligned}$$

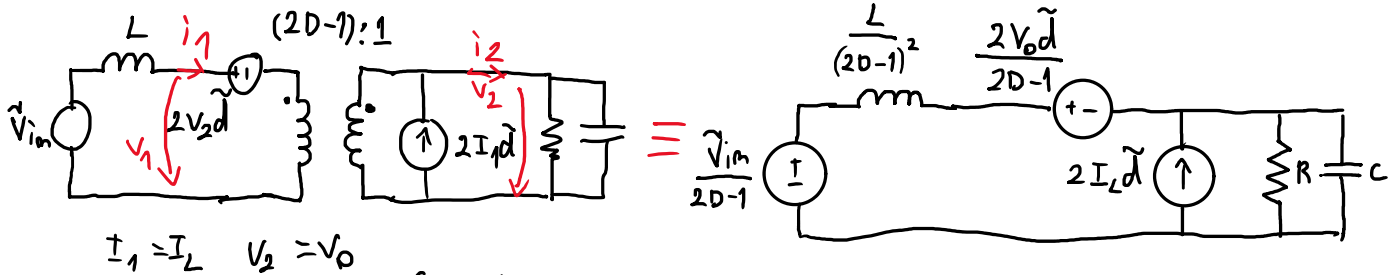DC
$$\begin{cases} V_1 = V_2(2D - 1) \\ I_2 = I_1(2D - 1) \end{cases} \quad AC \begin{cases} \tilde{v}_1 = 2V_2\tilde{d} + \tilde{v}_2(2D - 1) \\ \tilde{i}_2 = 2I_1\tilde{d} + \tilde{i}_1(2D - 1) \end{cases}$$



$$G_{oc} = \frac{\tilde{V}_o(s)}{\tilde{V}_L(s)} = \frac{\tilde{V}_o(s)}{\tilde{d}(s)} \cdot \frac{\tilde{d}(s)}{\tilde{V}_L(s)} = \frac{\tilde{V}_o(s)}{\tilde{d}(s)} \quad G_{PWM}=1$$

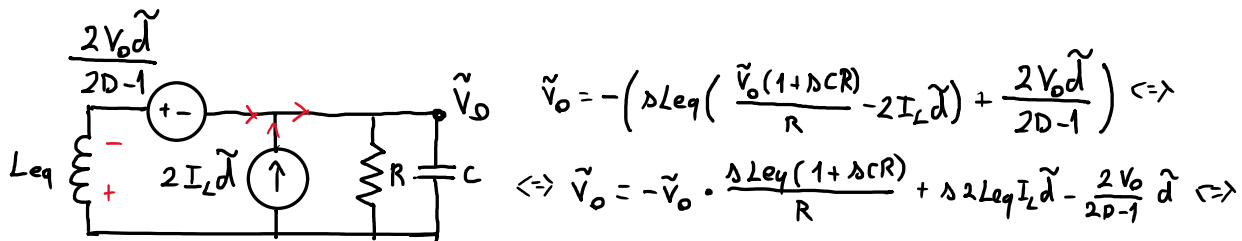$\tilde{V}_{in} = 0 \quad L_{eq} = \frac{L}{(2D-1)^2}$




$$\Leftrightarrow \tilde{V}_o \left(1 + \frac{sL_{eq}(1+sCR)}{R} \right) = \tilde{d} \frac{2V_o}{2D-1} \left(s \frac{L_{eq}}{R} - 1 \right) \Leftrightarrow$$

$$\Leftrightarrow \frac{\tilde{V}_o}{\tilde{d}} = \frac{2V_o}{2D-1} \frac{s \frac{L_{eq}}{R} - 1}{1 + \frac{sL_{eq}(1+sCR)}{R}} = \frac{2V_o}{2D-1} \cdot \frac{s \frac{L_{eq}}{R} - 1}{s^2 L_{eq}C + s \frac{L_{eq}}{R} + 1}$$

$$L_{eq} = \frac{L}{2D-1} \quad g = \frac{1}{2R} \sqrt{\frac{L_{eq}}{C}} \quad \frac{\tilde{V}_o}{\tilde{d}} = \frac{2V_o}{2D-1} \cdot \frac{1}{\frac{\omega^2}{\omega_m^2} + \frac{2g}{\omega_m^2} s + 1}$$

$$\omega_m = \frac{1}{\sqrt{L_{eq}C}} \quad \omega_{RHPZ} = \frac{R}{L_{eq}}$$

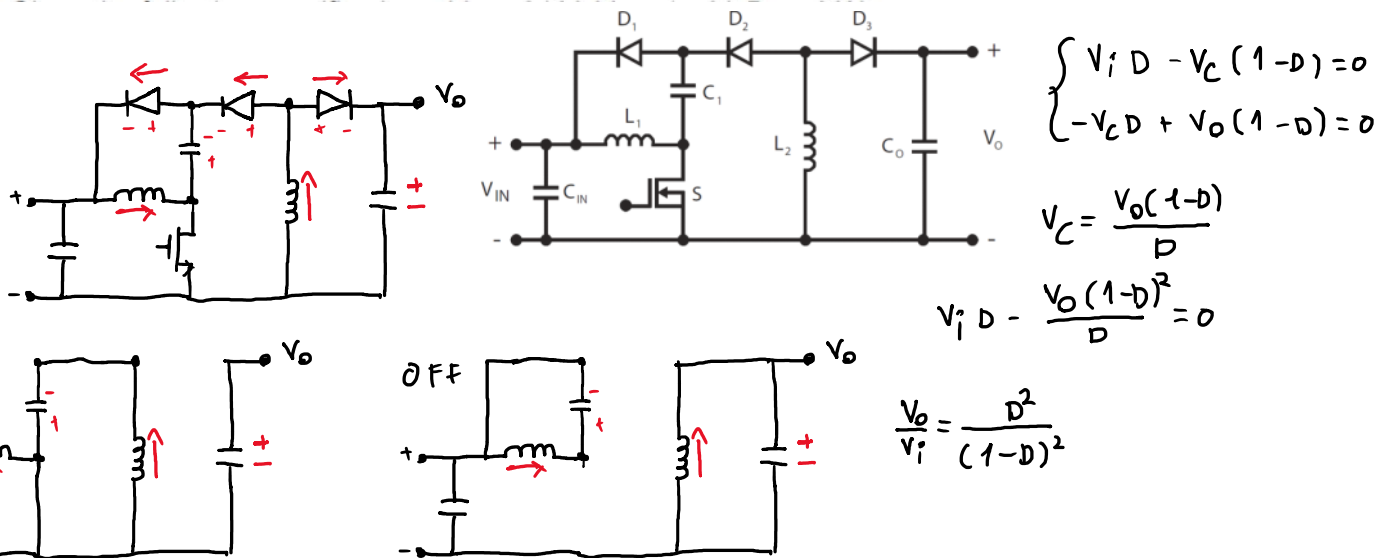- 2) The DC-DC converter shown in Fig. 3 operates in CCM at switching frequency $f_{sw} = 500$ kHz.
a) Draw a plot of the DC voltage transfer function V_O/V_{IN} as a function of the duty cycle D .



Given the following specifications: $V_{IN} = 24$ V, $V_O = 1.5$ V, $P_O = 6$ W

b) Calculate the duty-cycle D .

c) Calculate the average inductor currents.

$$\frac{V_O}{V_{in}} = \left(\frac{D}{(1-D)} \right)^2 \Rightarrow \frac{1}{4} = \frac{D}{1-D} \Rightarrow D = 0.20$$

$-I_{L2} D + I_{L1} (1-D) = 0 \leftarrow \text{charge balance}$

$$I_{L1} = \frac{I_2 D}{1-D} = 1.25 \text{ A}$$

$$I_O = I_{L2} \cdot (1-D) \Leftrightarrow \frac{6}{1.5 \cdot 0.8} = I_{L2} = 5 \text{ A}$$

$$I_0 = 4 \text{ A}$$

d) Select L_1 and L_2 such that the peak-to-peak current ripple is less than 25% of the average current.

$$V = L \frac{\Delta i}{\Delta t} \quad \frac{V \Delta t}{L} \ll \Delta i \quad L_1: \frac{V_i D T_s}{L_1} \leq 0.25 \cdot 1.25 \Rightarrow L_1 \geq \frac{24 \cdot 0.2 \cdot \frac{1}{500k}}{0.25 \cdot 1.25} \Leftrightarrow L_1 \geq 30.7 \mu\text{H}$$

$$L_2: \frac{V_O (1-D) T_s}{L_2} \leq 0.25 \cdot I_{L2} \Rightarrow L_2 \geq \frac{1.5 \cdot 0.8}{500k \cdot 0.25 \cdot 5} \Leftrightarrow L_2 \geq 1.92 \mu\text{H}$$

e) Select the capacitor C_1 such that the ripple voltage (peak-to-peak) is less than 1V.

$$I = C \frac{\Delta V}{\Delta t} \Rightarrow C > \frac{I_{L1} (1-D) T_s}{\Delta V} \Rightarrow C > 1.25 \cdot 0.8 \cdot \frac{1}{500k} \Rightarrow C > 2 \mu\text{F}$$

f) Derive expressions for L_{crit1} and L_{crit2} as a function of D .

$$\frac{V \Delta t}{L} = \Delta i \quad L_1: \frac{V_i D T_s}{L_{c1}} = 2 I_{L1} \Rightarrow \frac{V_O \frac{(1-D)^2}{D^2} T_s}{2 \cdot \frac{I_O D}{(1-D)^2}} = L_{c1} \Leftrightarrow L_{c1} = \frac{R_O T_s}{2} \frac{(1-D)^4}{D^2}$$

$$L_2: \frac{V_O (1-D) T_s}{L_{c2}} = 2 I_{L2} \Rightarrow L_{c2} = \frac{V_O}{I_O} \cdot \frac{(1-D)^2 T_s}{2} = \frac{R_O T_s}{2} (1-D)^2$$

g) Does the diode D_2 set a limit to the maximum duty-cycle? Briefly motivate your answer.

Yes it cannot boost
 $D_{max} = 0.5$