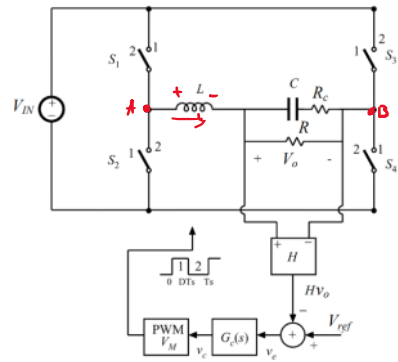


1) Consider the full-bridge converter shown in Fig. 1. $V_{IN} = 48 \text{ V}$, $f_{sw} = 500 \text{ kHz}$, $C = 470 \mu\text{F}$, $R_c = 50 \text{ m}\Omega$, $L = 50 \mu\text{H}$, $V_o = 5 \text{ V}$, $P_o = 25 \text{ W}$, $V_{ref} = 1.2 \text{ V}$, $V_M = 2 \text{ V}$.
a) Derive the DC transfer function V_o/V_{IN} .
b) Calculate the peak-to-peak output voltage ripple.



$$a) (V_{IN} - V_o)D + (0 - V_{IN} - V_o)(1-D) = 0 \Leftrightarrow$$

$$\Leftrightarrow V_{IN}D - V_{IN} + V_{IN}D - V_oD - V_o + V_oD = 0 \Leftrightarrow$$

$$\Leftrightarrow V_{IN}(2D-1) = V_o \Leftrightarrow \frac{V_o}{V_{IN}} = (2D-1)$$

$$D = 0.552 \quad R = 1$$

$$G_{PWM} = \frac{1}{V_M}!$$

$$b) \Delta V_o \approx \Delta V_c + \Delta V_{R_c}$$

$$\Delta I_L = \frac{(V_{IN} - V_o)}{L} \cdot D \cdot T_s = 949 \text{ mA}$$

$$\Delta V_{R_c} = \Delta I_L \cdot R_c = 47.5 \text{ mV}$$

$$\Delta V_c = \frac{\Delta Q}{C} = \frac{\Delta I_L \cdot T_s}{8C} = 0.5 \text{ mV} \Rightarrow \Delta V_o = 48 \text{ mV}$$

c) Derive the transfer function $G_{oc}(s) = \frac{\tilde{V}_o}{\tilde{V}_c}$, (**hint**: perturb and linearize the bridge voltage $\langle V_{AB} \rangle > T_s$).


Sketch the Bode plot of $G_{oc}(s)$.

$$\langle V_{AB} \rangle = d \cdot \langle V_{IN} \rangle - (1-d) \langle V_{IN} \rangle = (2d-1) \langle V_{IN} \rangle$$

$$\langle V_{AB} \rangle = V_{AB} + \tilde{V}_{AB}$$

$$\langle V_{IN} \rangle = V_{IN} + \tilde{V}_{IN}$$

$$d = D + \tilde{d}$$

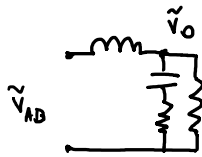

$$\Rightarrow \begin{cases} V_{AB} = (2D-1) V_{IN} \\ \tilde{V}_{AB} = (2D-1) \tilde{V}_{IN} + 2V_{IN} \tilde{d} \end{cases}$$

$$\tilde{d} = \frac{\tilde{V}_c}{V_M} = \frac{\tilde{V}_c}{2}$$

$$Z_1 = sL$$

$$Z_2 = \frac{(sCR_c + 1)R}{sCR_c + 1}$$

$$\tilde{V}_o = \tilde{V}_{AB} \cdot \frac{Z_2}{Z_2 + Z_1}$$

$$\left(\frac{Z_2}{Z_2 + Z_1} \right)^{-1} = (Z_2 + Z_1) \cdot \frac{1}{Z_2} = 1 + sL \cdot \frac{sCR_c + 1}{(sCR_c + 1)R}$$

$$R \gg R_c$$

$$G_{oc}(s) = \frac{\tilde{V}_o}{\tilde{V}_c} \Big|_{\tilde{V}_{IN}=0} \Leftrightarrow \tilde{V}_o \left(1 + sL \cdot \frac{sCR_c + 1}{(sCR_c + 1)R} \right) = V_{IN} \tilde{V}_c \Leftrightarrow \frac{\tilde{V}_o}{\tilde{V}_c} = V_{IN} \cdot \frac{sCR_c + 1}{s^2LC(1 + \frac{R_c}{R}) + s(\frac{L}{R} + CR_c) + 1}$$

$$\omega_{ESR} = \frac{1}{CR_c} = 42.5 \text{ K rad/s} \Rightarrow f_{ESR} = 6.77 \text{ kHz}$$

$$\omega_o = \frac{1}{\sqrt{LC(1 + \frac{R_c}{R})}} \Rightarrow f_o = 1.01 \text{ kHz}$$


$$\text{With } R_c \ll R \Rightarrow f_o = 1.04 \text{ kHz}$$

$$\xi = \left(\frac{L}{R} + CR_c \right) \frac{\omega_o}{2} = 0.20$$

$$\omega^1 = \omega_o \cdot 10^{-\xi} = 630 \text{ Hz}$$

$$\omega^1 = \omega_o \cdot 10^{\xi} = 1.6 \text{ kHz}$$
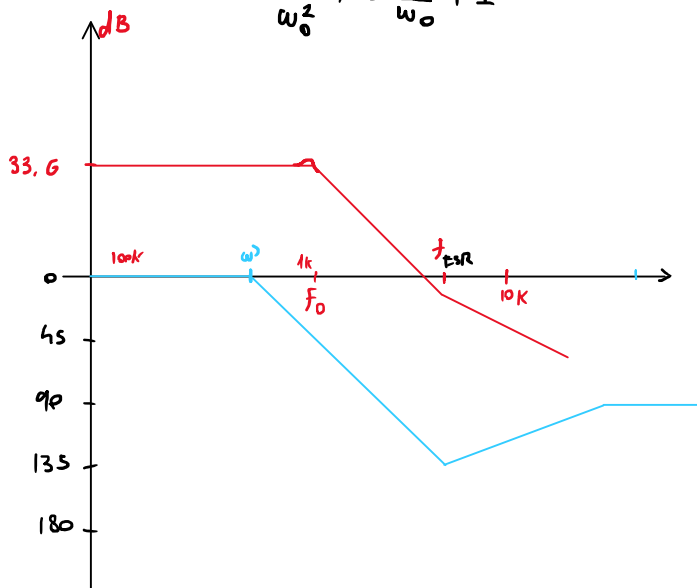
$$G_{oc}(s) = V_{IN} \cdot \frac{(1 + \frac{s}{\omega_z})}{\frac{s^2}{\omega_o^2} + s \frac{2\xi}{\omega_o} + 1}$$



d) Derive H such that $V_O = 5$ V.

e) Using the k-factor design method, determine the type-II compensator transfer function, $G_c(s)$, such that the loop transfer function crosses the 0dB axis at $f_c = 50$ kHz with a phase margin $\phi_m = 60^\circ$.

(note: $k = \sqrt{\frac{\omega_p}{\omega_z}} = \tan\left(\frac{\phi_{\text{boost}}}{2} + \frac{\pi}{4}\right)$).

d) $H V_O = V_{\text{ref}} \Leftrightarrow H = \frac{1.2}{5} = 0.240$

e) $f_c = 50 \text{ kHz}$

$\phi_m = 60^\circ$

$\phi_b = \phi_m - \angle G_{oc}(j\omega_c) - 90^\circ = 65^\circ$

$K = \sqrt{\frac{\omega_p}{\omega_z}} = \tan\left(\frac{\phi_b}{2} + \frac{\pi}{4}\right) = 4.51$

$\omega_z = \frac{\omega_c}{K} = 2\pi \cdot \frac{50}{4.51} \text{ k} = 69.7 \text{ krad/s}$

$\omega_p = \omega_c K = 2\pi \cdot 50 \cdot 4.51 \text{ k} = 1.41 \text{ Mrad/s}$

$|G_c(j\omega_c)| = \frac{1}{|G_{oc}(j\omega_c)| H} = 27.23$

$K_c = \omega_c \cdot \frac{\sqrt{1+1/K^2}}{\sqrt{1+K^2}} \cdot |G_c(j\omega_c)| = 1.9 \text{ Mrad/s}$

$\angle G_{oc}(j\omega_c) = -2 \arctan\left(\frac{f_c}{f_0}\right) + \arctan\left(\frac{f_c}{f_{\text{ESR}}}\right) =$


$= -95.4^\circ$

$|G_{oc}(f_c)| = V_{\text{IN}} \cdot \left(\frac{f_0}{f_{\text{ESR}}}\right)^2 \cdot \frac{f_{\text{ESR}}}{f_c} = 0.153 = -16.3 \text{ dB}$

$G_c(s) = \frac{K_c}{s} \cdot \frac{1 + s/\omega_z}{1 + s/\omega_p}$

f) Design the error amplifier/compensator.

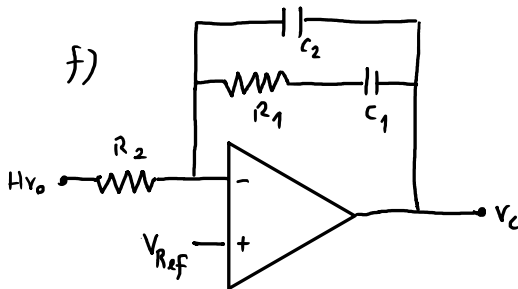g) The input voltage is varied between 36 and 72 V. What are the issues with system stability?



$G_c(s) = -\frac{1}{R_2} \cdot \frac{s C_1 R_1 + 1}{s C_2 (s C_1 R_1 + 1) + s C_1} =$

$= -\frac{1}{s R_2 C_1} \cdot \frac{1 + s C_1 R_1}{s C_2 R_1 + 1 + \frac{C_2}{C_1}}$

$\checkmark \approx 0 \text{ if } C_1 \gg C_2$

$R_1 C_1 = 1/\omega_z$

$R_1 C_2 = 1/\omega_p$

$R_2 C_1 = 1/K_c$

$R_1 = 27 \text{ k}\Omega$

$C_2 = 26 \text{ nF}$

$C_1 = 520 \text{ nF}$

$R_2 = 1 \text{ k}\Omega$

g) $V_{\text{IN}} \uparrow \Rightarrow |G_{oc}(s)| \uparrow$

Guarantee: worst $\Rightarrow$?

$f_c < \frac{1}{5} f_{\text{sw}}$ To be safe a factor of 10



stability is sometimes used

After $\frac{1}{5}$ of f_{sw} the model goes to shit

for both sides
decrease or increase will lose phase margin!

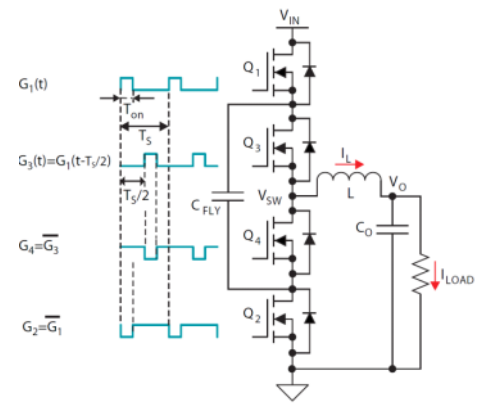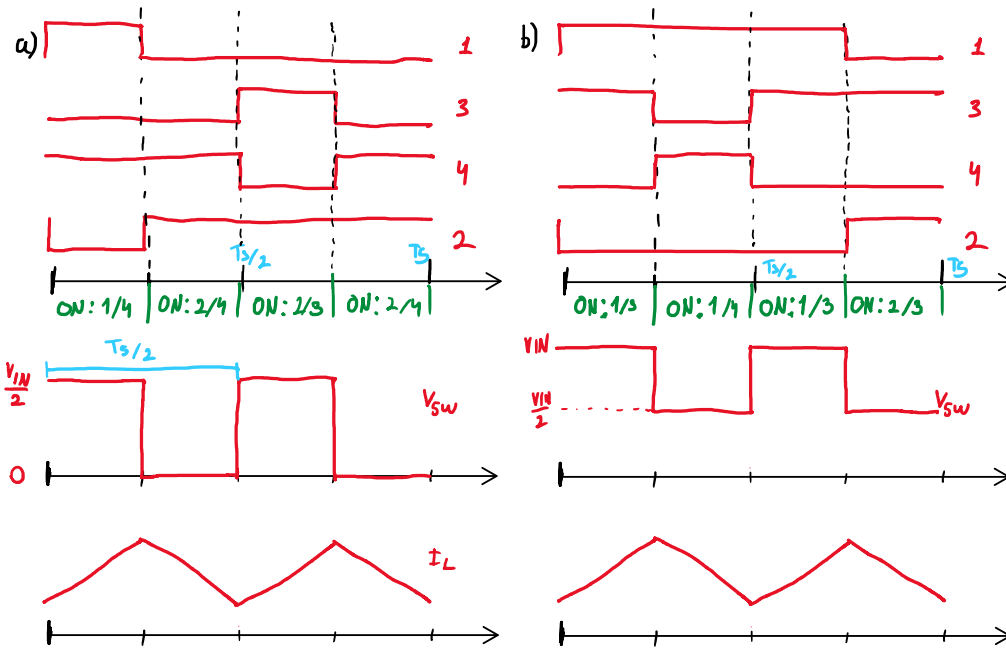2) The three-level buck converter shown in Fig. 2 operates in CCM at $f_{sw} = 1/T_s = 750$ kHz. The switch gate-driving waveforms are illustrated in Fig. 2 as well ($D = T_{on}/T_s$). Assume the converter is lossless.

- Sketch the plot of V_{SW} and I_L as a function of time, assuming $V_{CFLY} = V_{IN}/2$ and $D < 0.5$.
- Sketch the plot of V_{SW} and I_L as a function of time, assuming $V_{CFLY} = V_{IN}/2$ and $D > 0.5$.
- Derive the DC voltage transfer function V_O/V_{IN} as a function of D .
- Derive an expression for the peak-to-peak inductor current ripple, $\Delta i_{L, 3L}$, as a function of D .
- Sketch the plot of $\Delta i_{L, 3L}$ as a function of D , along with the plot of $\Delta i_{L, 2L}$ for a standard buck converter. What is the advantage of the three-level buck compared with the standard (two-level) buck converter?



$$c) (V_{SW} - V_O)D + (V_{SW} - V_O)(\frac{1}{2} - D) = 0$$

$$D < 0.5:$$

$$(\frac{V_{IN}}{2} - V_O)D + (0 - V_O)(\frac{1}{2} - D) = 0$$

$$V_{IN}D = V_O \Leftrightarrow \frac{V_O}{V_{IN}} = D$$

$$D > 0.5:$$

$$(V_{IN} - V_O)(D - \frac{1}{2}) + (\frac{V_{IN}}{2} - V_O)(1 - D) = 0$$

$$V_{IN}(D - \frac{1}{2} + \frac{1}{2} - \frac{D}{2}) - V_O(D - \frac{1}{2} + 1 - D) = 0$$

$$\frac{V_O}{V_{IN}} = D$$


$$d) V = L \frac{di}{dt} \Leftrightarrow \Delta i = \frac{V \Delta t}{L} = \frac{(\frac{V_{IN}}{2} - V_O)DT_s}{L} = \frac{V_{IN}(\frac{1}{2} - D) \cdot D}{L f_{sw}} \quad D < 0.5$$

$$D > 0.5 \quad \frac{(\frac{V_{IN}}{2} - V_O)(1 - D)}{L f_{sw}} = \frac{V_{IN}(\frac{1}{2} - D)(1 - D)}{L f_{sw}}$$

$$e) \Delta i_{L2} = \frac{(V_{IN} - V_O)D}{L f_{sw}} = \frac{V_{IN}(1 - D)D}{L f_{sw}}$$

$$\Delta i_{L \text{ norm}} = (1 - D)D$$
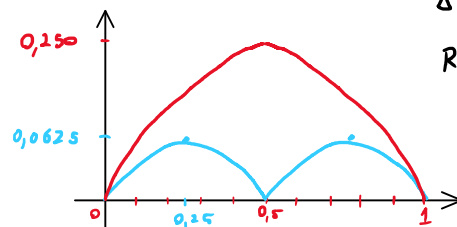
$$\Delta i_{L3 \text{ norm}} = \begin{cases} (\frac{1}{2} - D)D \\ (\frac{1}{2} - D)(1 - D) \end{cases}$$



$$\Delta i_{L2 \text{ Max}} = 4 \cdot \Delta i_{L3 \text{ Max}}$$

Ripple is 4 times smaller



Assuming $V_{IN} = 12V$, $V_O = 3.8V$, $P_O = 7.6 W$:

- Select the inductance L such that the peak-to-peak current ripple is less than 30% of the average current.
- Select a plot of the current flowing through C_{FLY} as a function of time.
- Select C_{FLY} to ensure that the peak-to-peak voltage ripple is less than 10% of the nominal voltage.
- Calculate the peak-to-peak output voltage ripple ($C_O = 22 \mu F$, $ESR = 5m\Omega$).

$$f) I_O = 2 A \Rightarrow \Delta I_L = 0.6 A$$

$$D = 0.317$$
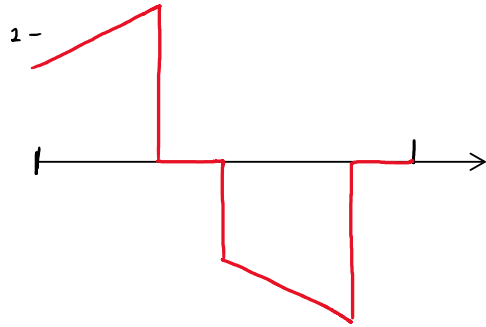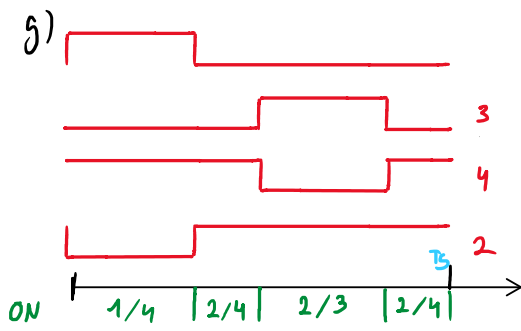
$$\Delta I_L < \frac{V_{IN}(\frac{1}{2} - D) \cdot D}{L f_{sw}} \Leftrightarrow L < \frac{V_{IN}(\frac{1}{2} - D) D}{\Delta I_L f_{sw}} \Leftrightarrow L < 1.55 \mu H$$



h)

Neglecting current ripple

$$i = C \frac{\Delta V}{\Delta t} \Leftrightarrow \Delta V = \frac{i \Delta t}{C}$$

$$0.1 \frac{V_{IN}}{2} < \frac{I_o D T_s}{C} \Rightarrow C < \frac{2 I_o D T_s}{0.1 V_{IN}}$$

$$C < 1.4 \mu F$$

i)

$$\Delta V = \frac{1}{2} \cdot \frac{\Delta T}{4} \cdot \frac{\Delta I_o}{2} \cdot C + ESR \cdot \Delta I_o =$$

$$\Delta I_o = 0,6 A$$

$$= \frac{\Delta I_o}{16 C f_{sw}} + ESR \Delta I_o \Rightarrow \Delta V = 2.27 mV + 3 mV$$

